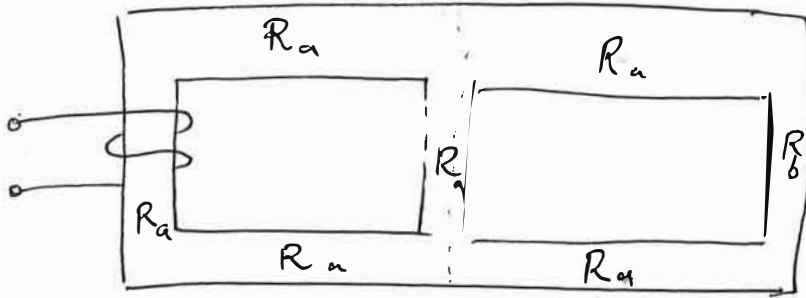


Homework Solution

①

(a) Draw magnetic ckt:



* All sections labeled R_a have identical reluctances

$$R_a = \frac{\text{length of Leg}}{\mu \text{ area}}$$

$$= \frac{l}{\mu_0 \mu_r A_a}$$

$$* \text{where } l = 3 \text{ cm} = \boxed{0.03 \text{ m} = l}$$

$$* A_a = 1 \text{ cm} \times 1 \text{ cm}$$

$$= (0.01 \text{ m})^2 = (10^{-2})^2 \text{ m}^2$$

$$= \boxed{10^{-4} \text{ m}^2 = A_a}$$

$$= \frac{(0.03 \text{ m})}{(4\pi \times 10^{-7} \text{ H/m}) 1000 (10^{-4} \text{ m}^2)}$$

$$\approx 238.7 \times 10^3 \text{ H}^{-1} = R_a$$

(2)

- The "narrow" leg has reluctance

$$R_b = \frac{l}{\mu_0 \mu_r A_b}$$

$$\text{where } A_b = 0.5 \text{ cm} \times 1 \text{ cm}$$

$$= (0.5 \times 10^{-2} \text{ m})(1 \times 10^{-2} \text{ m})$$

$$= 0.5 \times 10^{-4} \text{ m}^2$$

$$= 5 \times 10^{-5} \text{ m}^2$$

$$= \frac{0.03 \text{ m}}{(4\pi \times 10^{-7} \text{ H/m}) 1000 (5 \times 10^{-5} \text{ m}^2)}$$

$$\approx \underbrace{477.5 \times 10^3 \text{ H}^{-1}} = R_b$$

- The core has 3 branches


$$\text{Left branch total reluctance} = R_x = 3 R_a = 716.2 \times 10^3 \text{ H}^{-1}$$

$$\text{Center branch total reluctance} = R_y = R_a = 238.7 \times 10^3 \text{ H}^{-1}$$

$$\text{Right branch total reluctance} = R_z = 2 R_a + R_b = 954.9 \times 10^3 \text{ H}^{-1}$$

(3)

We can now redraw the circuit as

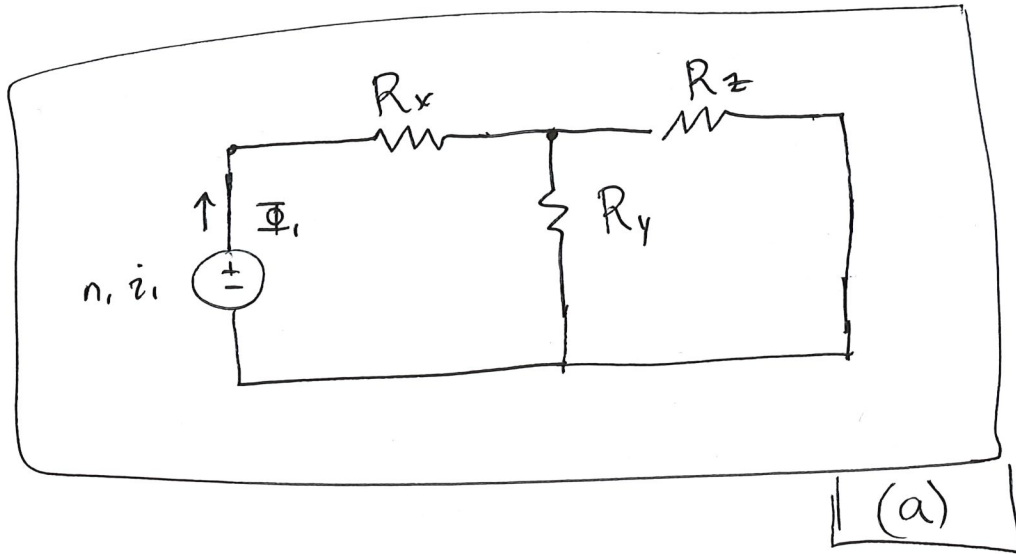

b) Determine the inductance

Compute "effective" reluctance from coil #1

$$\begin{aligned}
 R_{\text{eff}} &= R_x + R_y \parallel R_z \\
 &= R_x + \frac{R_y R_z}{R_y + R_z} \\
 &\approx 907.2 \text{ H}^{-1}
 \end{aligned}$$


$$\rightarrow \Phi_1 = \frac{n_1 i_1}{R_{\text{eff}}}$$

$$\mathcal{F} \quad v_1(t) = n_1 \frac{d\Phi_1}{dt} = \overbrace{\frac{n_1^2}{R_{\text{eff}}}}^L \frac{di_1(t)}{dt}$$

$$\Rightarrow L = \frac{\overset{n_1=10}{n_1^2}}{R_{\text{eff}}} \approx 110.2 \mu\text{H} = L \quad (b)$$

(4)

c) Modify ck + model w/ 2nd winding

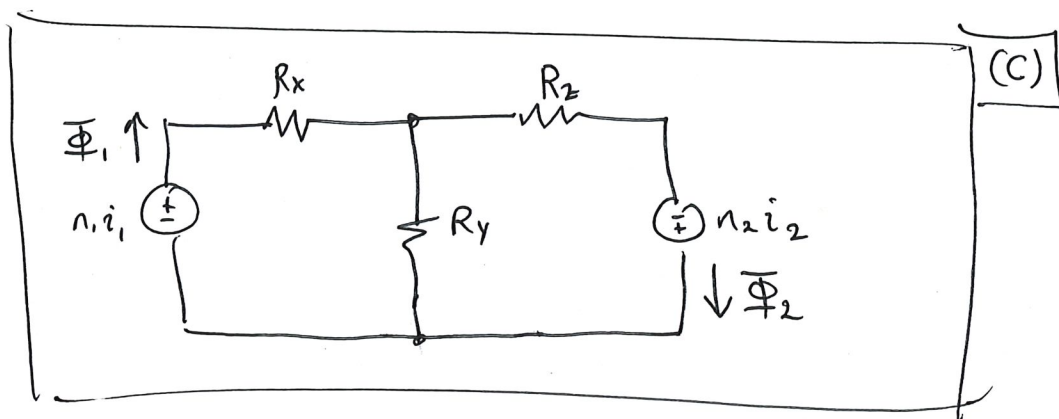

d) Solve via superposition to get

$$\begin{bmatrix} v_1(t) \\ v_2(t) \end{bmatrix} = \begin{bmatrix} L_{11} & L_{12} \\ L_{12} & L_{22} \end{bmatrix} \frac{d}{dt} \begin{bmatrix} i_1(t) \\ i_2(t) \end{bmatrix}$$


• Main Strategy:

- We need to solve for Φ_1 & Φ_2 in the diagram above. Once we obtain Φ_1 & Φ_2 , then Faraday's law gives

$$v_1(t) = n_1 \frac{d\Phi_1}{dt} \quad \& \quad v_2(t) = n_2 \frac{d\Phi_2}{dt} \quad \left. \vphantom{\frac{d\Phi_1}{dt}} \right\} \text{ gives us}$$

which we can put into the form needed.

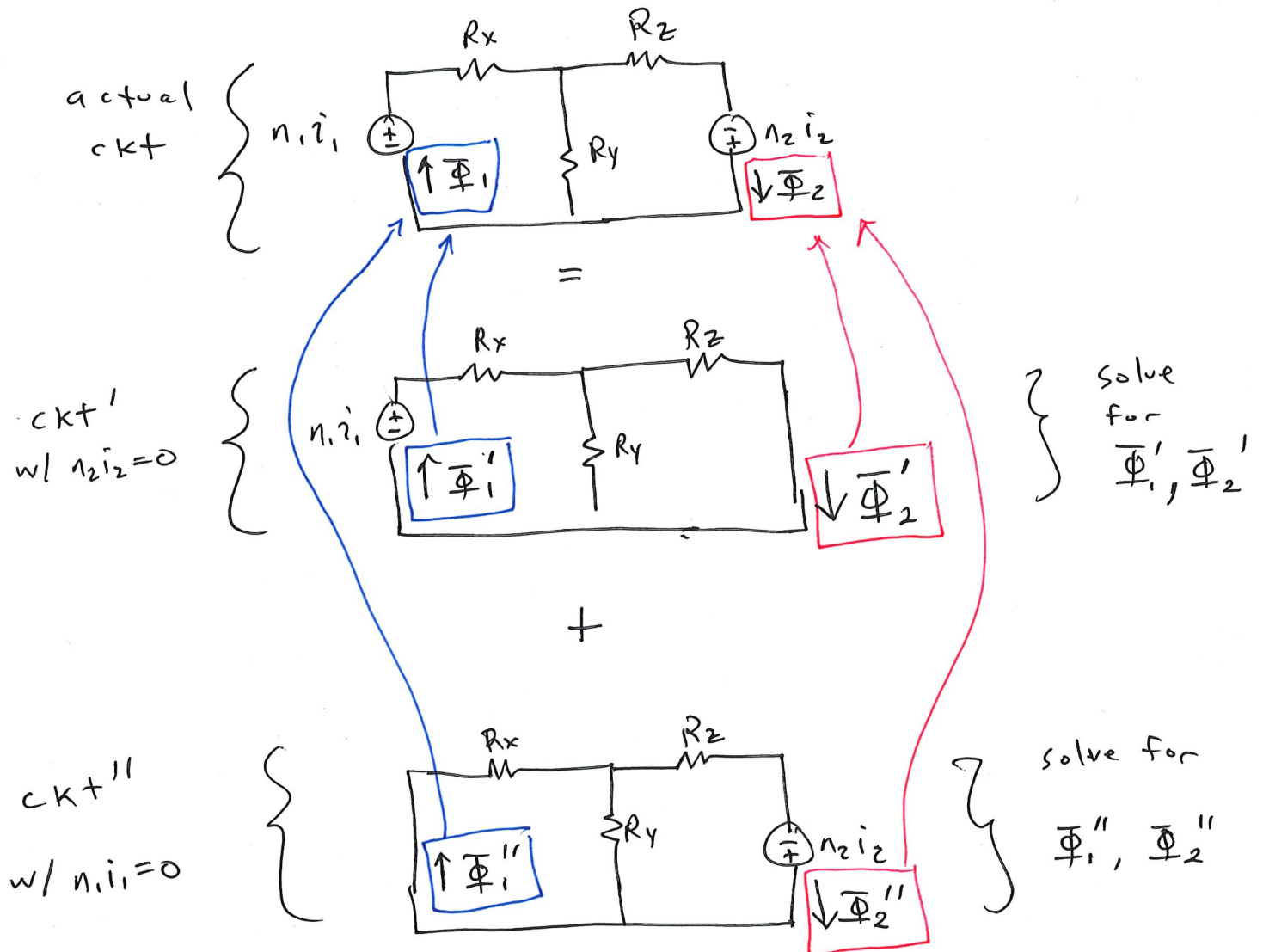- The main idea of superposition is that we will write the circuit above as the sum of two circuits:



where $\Phi_1 = \Phi_1' + \Phi_1''$ and $\Phi_2 = \Phi_2' + \Phi_2''$

- First set $n_2 i_2 = 0$ to get circuit 1... solve for Φ_1' and Φ_2' .

Looking above, KVL for circuit 1 gives

$$n_1 i_1 = \Phi_1' \left(R_x + \frac{R_y R_z}{R_y + R_z} \right)$$

$\underbrace{R_y + R_z}_{R_y \parallel R_z}$

$$\Rightarrow \Phi_1' = \frac{n_1 i_1}{R_x + \frac{R_y R_z}{R_y + R_z}} \quad (1)$$

6

Next solve for Φ_2'

KVL also says:

$$R_2 \Phi_2' = n_1 i_1 - \Phi_1' R_x$$

$$\Rightarrow \Phi_2' = \frac{n_1 i_1 - \Phi_1' R_x}{R_2}$$


* use (1) for Φ_1'

$$= \frac{n_1 i_1}{R_2} - \frac{R_x}{R_2} \frac{n_1 i_1}{R_x + \frac{R_y R_z}{R_y + R_z}}$$

$$= n_1 i_1 \left(\frac{1}{R_2} - \frac{R_x}{R_2} \frac{1}{\left(R_x + \frac{R_y R_z}{R_y + R_z} \right)} \right) \quad (2)$$

$$= \Phi_2'$$

• Next set $n_1 i_1 = 0$ & solve again

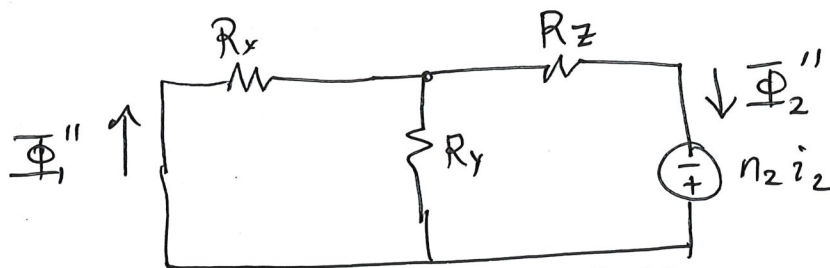

need to solve for Φ_1'' & Φ_2''

KVL gives

$$n_2 i_2 = \Phi_2'' \left(R_z + \frac{R_x R_y}{R_x + R_y} \right)$$

$$\Rightarrow \Phi_2'' = \frac{n_2 i_2}{R_z + \frac{R_x R_y}{R_x + R_y}} \quad (3)$$

• Do KVL again but include $\Phi_1'' R_x$ branch

$$0 = n_2 i_2 - \Phi_1'' R_x - \Phi_2'' R_z$$

→ solve for Φ_1''

$$\Rightarrow \Phi_1'' = \frac{n_2 i_2 - \Phi_2'' R_z}{R_x}$$

* substitute (3)

$$= \frac{n_2 i_2}{R_x} - \frac{R_z}{R_x} \left(\frac{n_2 i_2}{R_z + \frac{R_x R_y}{R_x + R_y}} \right)$$

$$= \left(n_2 i_2 \left(\frac{1}{R_x} - \frac{R_z}{R_x} \frac{1}{R_z + \frac{R_x R_y}{R_x + R_y}} \right) \right) = \Phi_1'' \quad (4)$$

• Now combine & apply superposition:

$$\Phi_1 = \underbrace{\Phi_1'}_{(1)} + \underbrace{\Phi_1''}_{(4)}$$

$$= n_1 i_1 \frac{1}{R_x + \frac{R_y R_z}{R_y + R_z}} + n_2 i_2 \left(\frac{1}{R_x} - \frac{R_z}{R_x} \frac{1}{R_z + \frac{R_x R_y}{R_x + R_y}} \right) \quad (5)$$

and voltage is

$$v_1(t) = n_1 \frac{d\Phi_1}{dt}$$

$$= \underbrace{n_1^2 \frac{1}{R_x + \frac{R_y R_z}{R_y + R_z}}}_{L_{11}} \frac{di_1}{dt} + \underbrace{n_1 n_2 \left(\frac{1}{R_x} - \frac{R_z}{R_x} \frac{1}{R_z + \frac{R_x R_y}{R_x + R_y}} \right)}_{L_{12}} \frac{di_2}{dt} \quad (6)$$

and

$$\Phi_2 = \overset{(2)}{\Phi_2'} + \overset{(3)}{\Phi_2''}$$

$$= n_1 i_1 \left(\frac{1}{R_z} - \frac{R_x}{R_z} \frac{1}{\left(R_x + \frac{R_y R_z}{R_y + R_z} \right)} \right) + n_2 i_2 \frac{1}{R_z + \frac{R_x R_y}{R_x + R_y}} \quad (7)$$

where v_2 is

$$v_2(t) = n_2 \frac{d\Phi_2}{dt}$$

$$= \underbrace{n_1 n_2 \left(\frac{1}{R_z} - \frac{R_x}{R_z} \frac{1}{\left(R_x + \frac{R_y R_z}{R_y + R_z} \right)} \right)}_{L_{12}} \frac{di_1}{dt} + \underbrace{n_2^2 \left(\frac{1}{R_z + \frac{R_x R_y}{R_x + R_y}} \right)}_{L_{22}} \frac{di_2}{dt}$$

- L_{12} in (8) & (6) "look" different but are in fact equal once you plug in the numbers. You can also show they are equivalent by doing a bunch of algebra. Plugging in numbers on a computer we get.

$$\begin{bmatrix} v_1(t) \\ v_2(t) \end{bmatrix} = \underbrace{\begin{bmatrix} 110.2 \mu\text{H} & 44.1 \mu\text{H} \\ 44.1 \mu\text{H} & 352.7 \mu\text{H} \end{bmatrix}}_{\begin{bmatrix} L_{11} & L_{12} \\ L_{12} & L_{22} \end{bmatrix}} \frac{d}{dt} \begin{bmatrix} i_1(t) \\ i_2(t) \end{bmatrix}$$

[d]