

Lecture # 5 10/8/2021

- HW 1 due Monday 11:59 pm PT.

Last time

-> General procedure to compute S.S. values in a converter

↳ Using balance eqns.

Today



↳ Finish last set of blank pages

↳ Switch realization




Tip


↳ HW doesn't require a sim., but you can simulate it anyway.

Boost Example

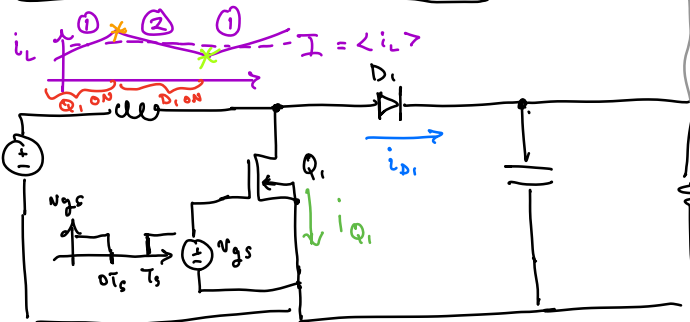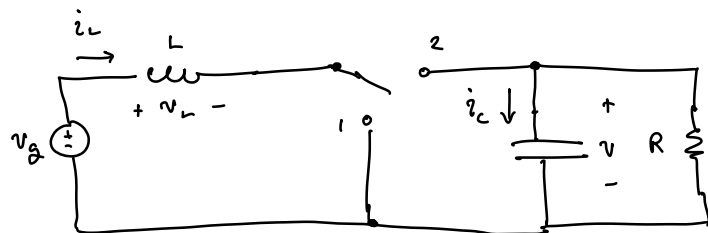

discontinuous currents

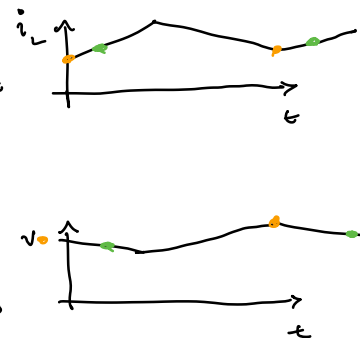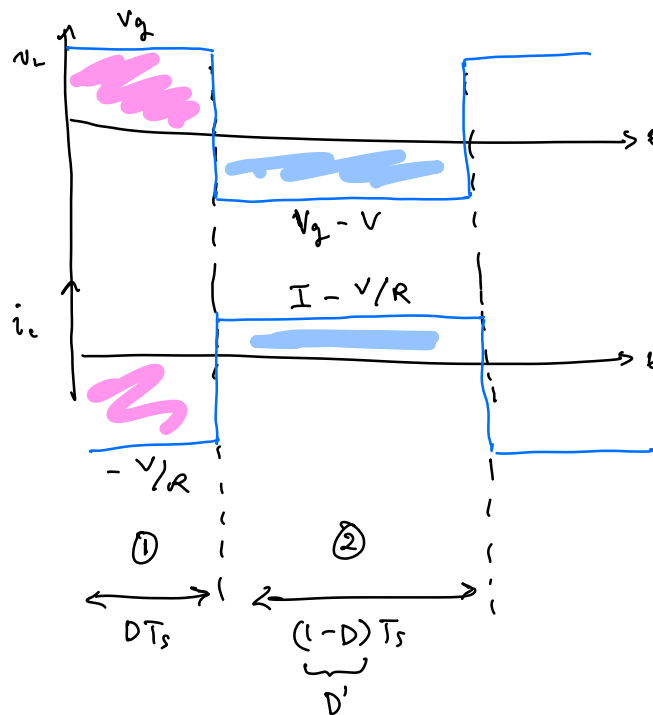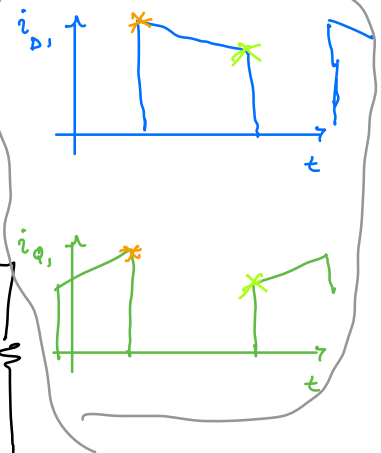

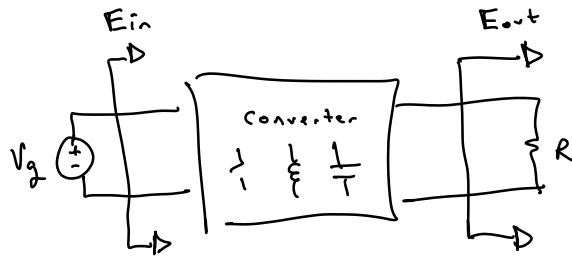

Cap & Inductor Behavior

$$v_L = L \frac{di_L}{dt}$$

small current ripple \approx

$$i_C = C \frac{dv}{dt}$$

small voltage ripple \approx


- Computing Ripple Amplitude

• For L in boost

generally $\frac{di_L}{dt} = \frac{v_L}{L}$

use linear approximation ... rewrite derivative
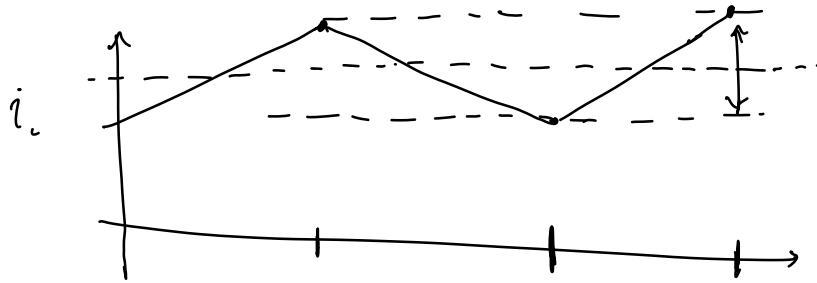
$$\begin{aligned} \textcircled{1} & \rightarrow \frac{2 \Delta i_L}{\Delta t_{\textcircled{1}}} = \\ \textcircled{2} & \rightarrow \frac{2 \Delta i_L}{\Delta t_{\textcircled{2}}} = \end{aligned}$$



... similar story for cap

• For C

$$\frac{dv}{dt} = \frac{i_c}{C}$$

↓ use approx for derivative

$$\frac{2 \Delta v}{\Delta t_1} =$$


OR

$$\frac{2 \Delta v}{\Delta t_2} =$$

— Discontinuous waveforms through switches

• Look @ boost again

- Cuk Converter Example

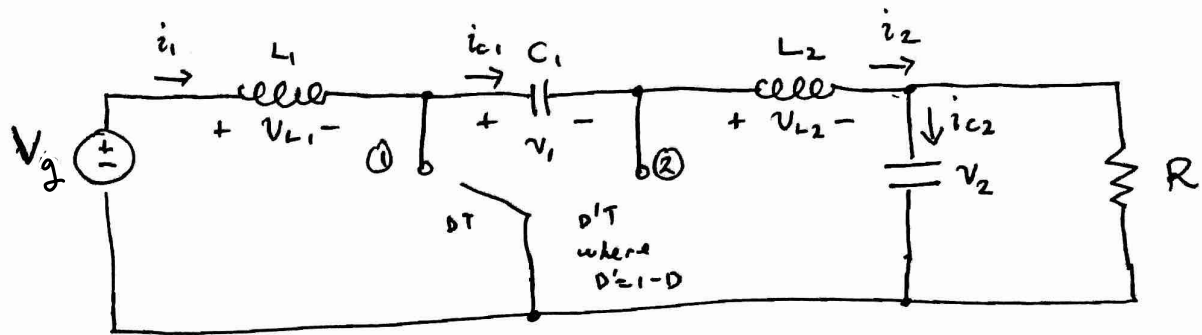

Objective :


Solve for V_{ss} , inductor currents & cap voltages
(dc component of)

Approach

1) Compute balance eqns

2) Do a bunch of algebra

- Cuk: State # 1

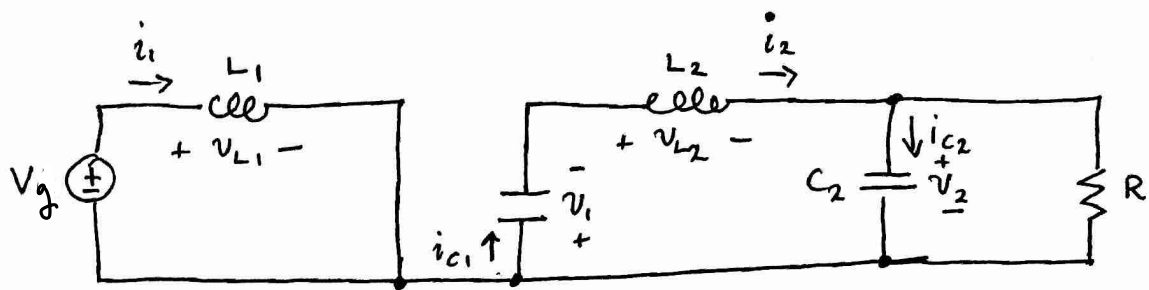

$$v_{L1} =$$

$$v_{L2} =$$

$$i_{C1} =$$

$$i_{C2} =$$

$\xrightarrow{\text{small}}$
 ripple
 approx
 "SRA"


$$v_{L1} =$$

$$v_{L2} =$$

$$i_{C1} =$$

$$i_{C2} =$$

• Cuk State #2

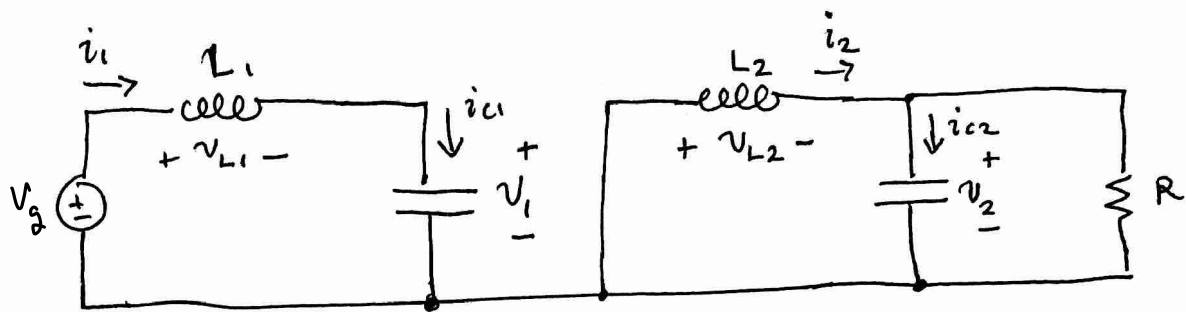

$$v_{L1} =$$

$$v_{L2} =$$

$$i_{c1} =$$

$$i_{c2} =$$

SRA


→

$$v_{L1} =$$

$$v_{L2} =$$

$$i_{c1} =$$

$$i_{c2} =$$

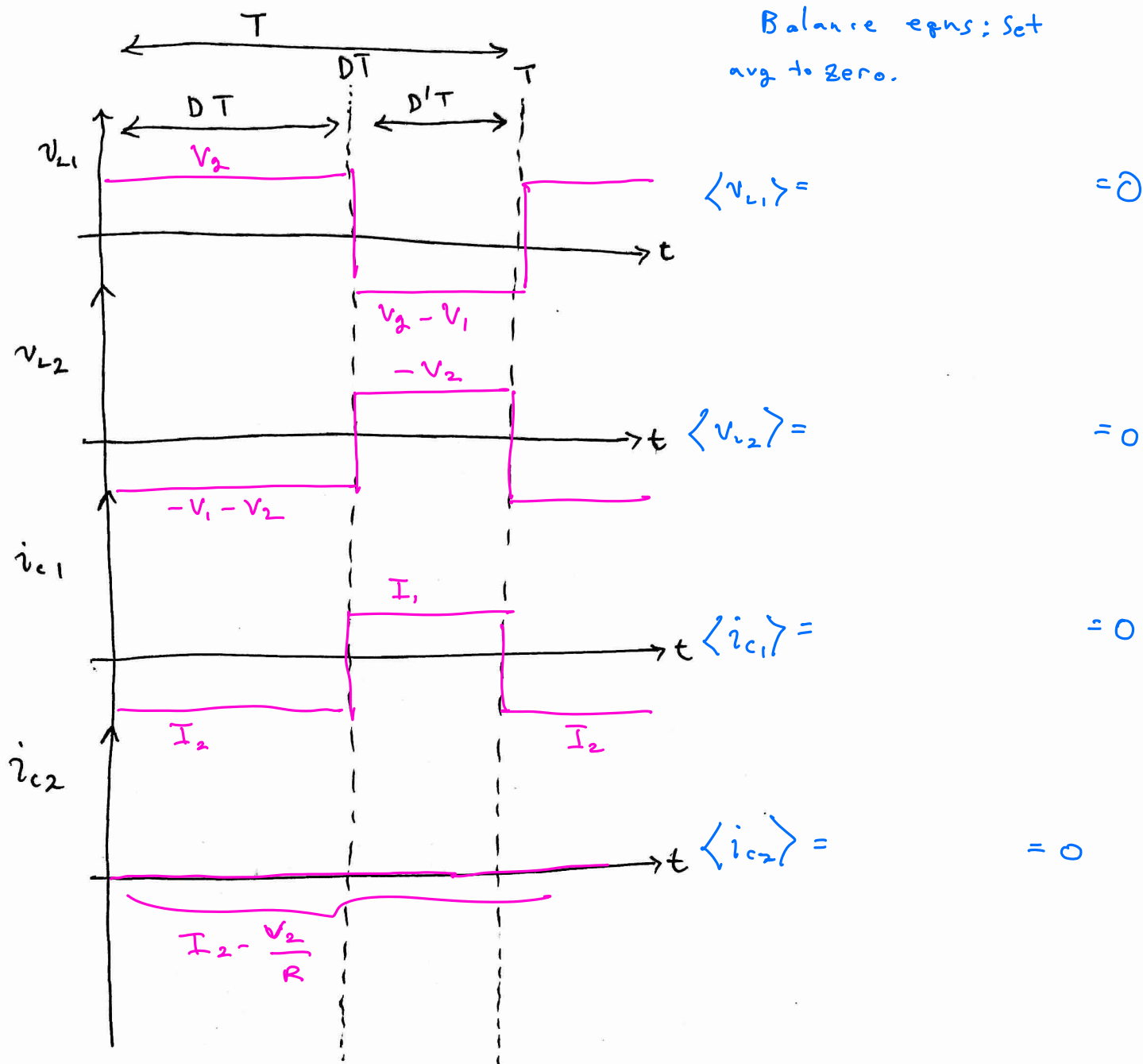

Take stock:

Unknowns:

of equations =

- Recap of some basic converters

