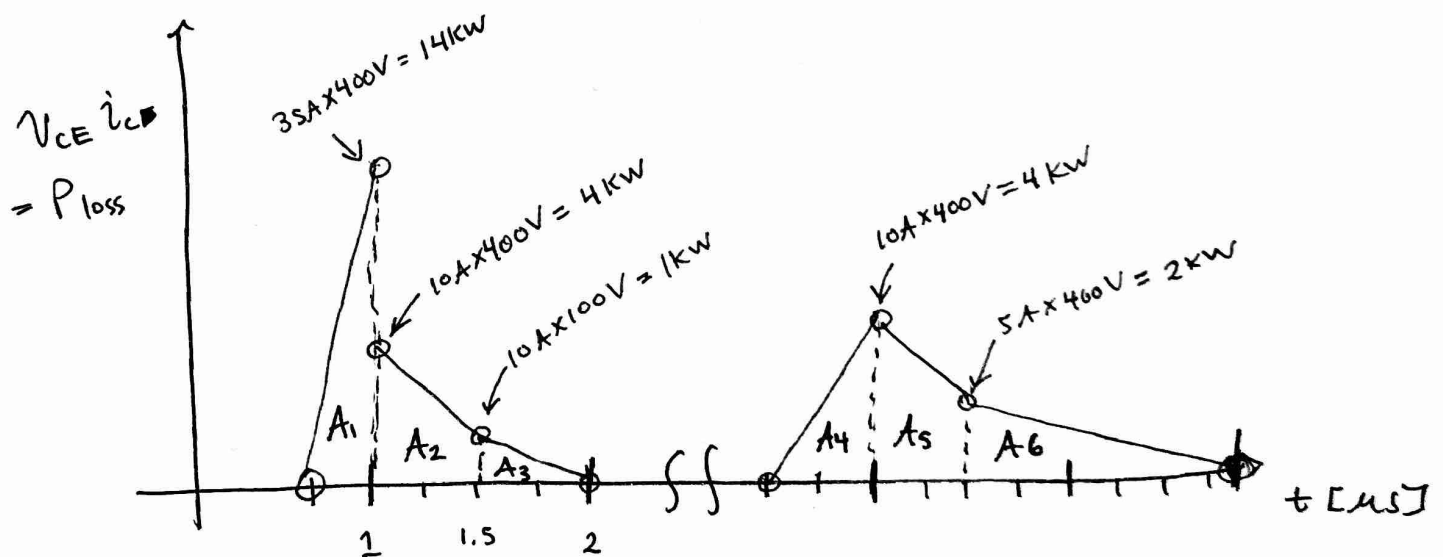


## Home work #4 Solutions

### Problem # 1

- 1 a) - Look @  $V_{CE}(t)$  &  $i_c(t)$  waveforms to compute power loss.
- Multiply  $V_{CE}(t)$  &  $i_c(t)$  @ transition points on waveforms, then connect the dots using straight line approximations where needed.



- Slice up into 6 regions & calculate areas.  $\frac{1}{2}$  base  $\times$  height works for  $A_1, A_3, A_4, A_6$  directly. For  $A_2$  &  $A_5$ , it's convenient to break those up into a rectangle on the bottom + triangle sitting on top.

$$E_{loss} = A_1 + A_2 + A_3 + A_4 + A_5 + A_6$$

$$A_1 = \frac{1}{2} \times 0.25 \mu s \times 14 kW$$

$$A_2 = \underbrace{0.5 \mu s \times 1 kW}_{\square \text{ on bottom}} + \underbrace{\frac{1}{2} 0.5 \mu s \times 3 kW}_{\Delta \text{ on top}}$$

$$A_3 = \frac{1}{2} \times 0.5 \mu s \times 1 kW$$

$$A_4 = \frac{1}{2} 0.5 \mu s \times 4 kW$$

$$A_5 = \underbrace{0.5 \mu s \times 2 kW}_{\square \text{ on bottom}} + \underbrace{\frac{1}{2} \times 0.5 \mu s \times 2 kW}_{\Delta \text{ on top}}$$

$$A_6 = \frac{1}{2} \times 1.5 \mu s \times 2 kW$$


---


↳ Crunch numbers & total up

$$E_{loss} = 7.2 \text{ mJ} \quad | a$$

& average power loss due to switching is

$$P_{sw} = f_s E_{loss}$$

(b) Draw ckt:

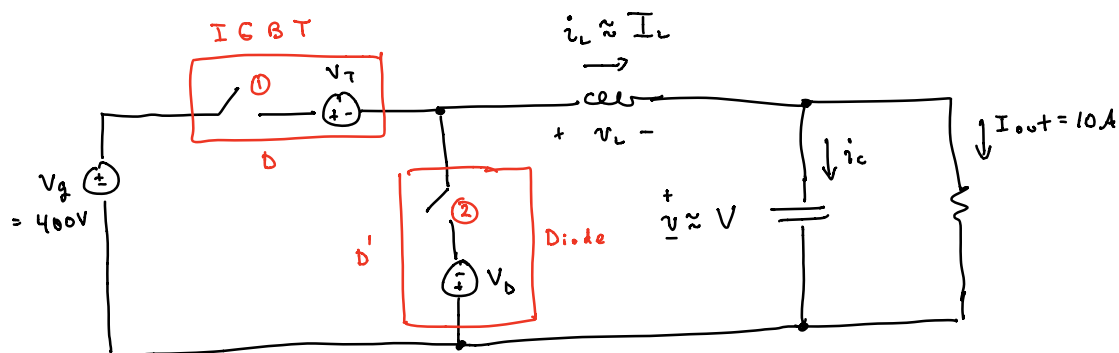

Where  $V_T = 2.5V$ ,  $V_b = 1.5V$ .

Conduction loss from diodes only is given by

$$P_{cond} = D \overbrace{(V_T I_L)}^{IGBT} + D' \overbrace{(V_b I_L)}^{diode} \quad (1)$$

?      ✓      ✓      ?      ✓      ✓

$I_L = 10A$  from plot

$D$  is only unknown. Obtain it from balance eqn.

$$\langle v_L \rangle = 0 = D(V_g - V_T - V) + D'(-V_b - V) \quad (2)$$

$$\langle i_c \rangle = 0 = D(I_L - I_{out}) + D'(I_L - I_{out}) \quad (3)$$

config ①      config ②

(2) confirms that  $I_L = I_{out} = 10A$ .

Use (1) to solve for  $D$

$$\Rightarrow 0 = D(V_g - V_T - V) + D'(-V_b - V)$$

$$= D(V_g - V_T) - \cancel{DV} - V_b - V + DV_b + \cancel{DV}$$

\* collect terms w/  $D$  factor

$$= D (V_g - V_T + V_D) - V_D - V$$

$$= 0$$

$$\Rightarrow D = \frac{V_D + V}{V_g - V_T + V_D} \quad (4)$$

$$= \frac{1.5V + 200V}{400V - 2.5V + 1.5} = 0.505$$

$$= D$$

(4)  $\rightarrow$  (1) gives:

$P_{\text{cond loss}}$  = all conduction loss in forward drops

$$= \underbrace{0.505}_D (V_T I_L) + \underbrace{(1 - 0.505)}_{1-D} (V_D I_L)$$

$\approx 20.05 \text{ W}$  1 (b)

1c) Look @ efficiency

Know

$$P_{\text{out}} = V I = (200V)(10A) = 2 \text{ kW}$$

Efficiency definition is

$$\eta = \frac{P_{\text{out}}}{P_{\text{in}}}$$

\* recall  $P_{\text{out}} = P_{\text{in}} - \overbrace{P_{\text{sw loss}} + P_{\text{cond loss}}}^{\text{losses}} \Rightarrow P_{\text{in}} = P_{\text{out}} + P_{\text{sw}} + P_{\text{cond}}$

$$= \frac{P_{\text{out}}}{P_{\text{out}} + \underbrace{f_s E_{\text{loss}}}_{\substack{\text{from} \\ \text{part a}}} + P_{\text{cond loss}}}$$

$$\eta = \frac{2 \text{ kW}}{2 \text{ kW} + f_s (7.2 \text{ mJ}) + 20.05 \text{ W}}$$

(c)

$$= \eta$$

↑ easy to plot on computer