
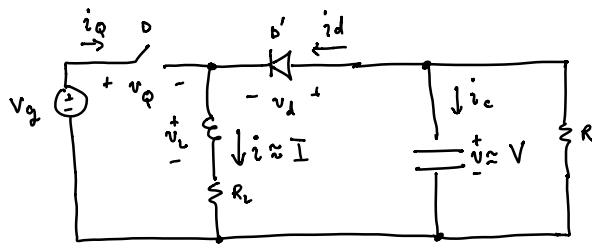


Homework # 5

Problem 1

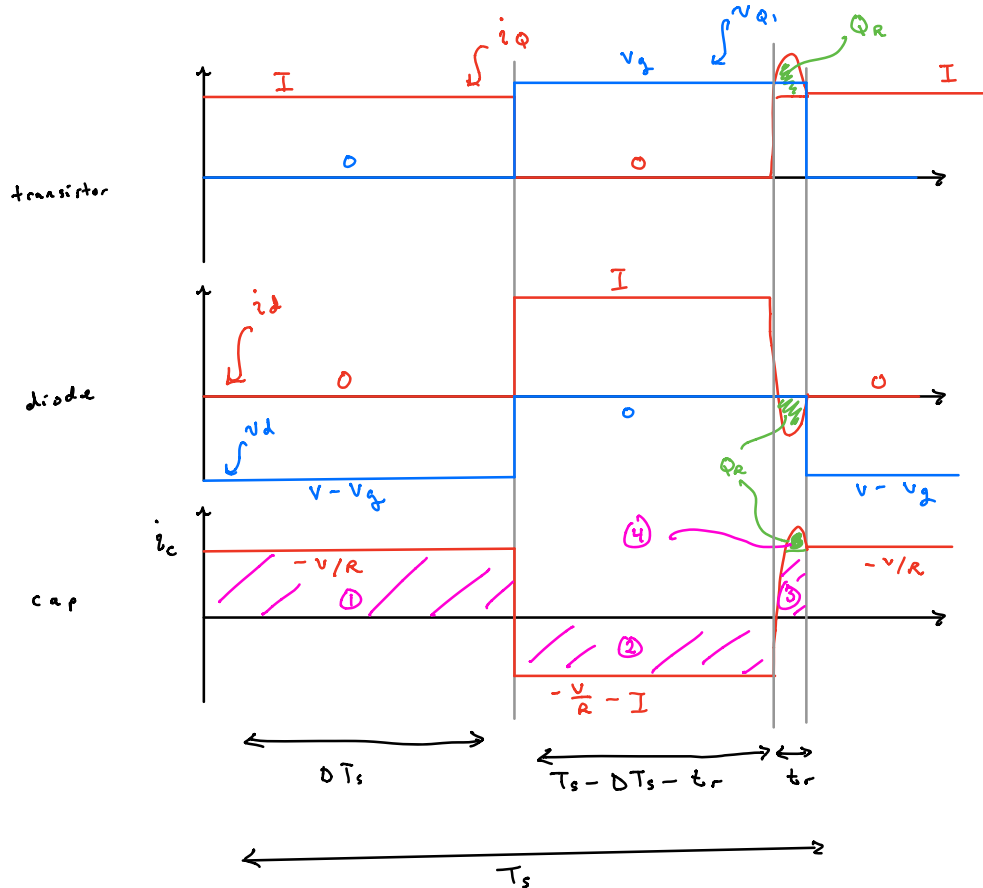

Draw waveforms like in lecture



where $i_c = -(\frac{V}{R} + i_d)$

- Volt - sec balance

$$\langle V_L \rangle = 0 = D(V_g - IR_L) + D'(V - IR_L)$$

$$= DV_g - IR_L + D'V = 0 \quad \leftarrow \text{KVL loop eqn.}$$

- Charge balance



$$\langle i_o \rangle = \frac{\text{sum of areas}}{T_s}$$

$$= \frac{\overset{\textcircled{1}}{DT_s \left(-\frac{V}{R}\right)} + \overset{\textcircled{2}}{\left(T_s - DT_s - t_r\right) \left(-\frac{V}{R} - I\right)} + \overset{\textcircled{3}}{t_r \left(-\frac{V}{R}\right)} + \overset{\textcircled{4}}{Q_R}}{T_s}$$


$$= \frac{-DT_s \frac{V}{R} + \left(-T_s \frac{V}{R} - IT_s + DT_s \frac{V}{R} + I DT_s + t_r \frac{V}{R} + I t_r\right) - t_r \frac{V}{R} + Q_R}{T_s}$$

$$= -\frac{V}{R} - D'I + I \frac{t_r}{T_s} + \frac{Q_R}{T_s} = 0 \quad \leftarrow \text{KCL eqn}$$

Draw equiv ckt

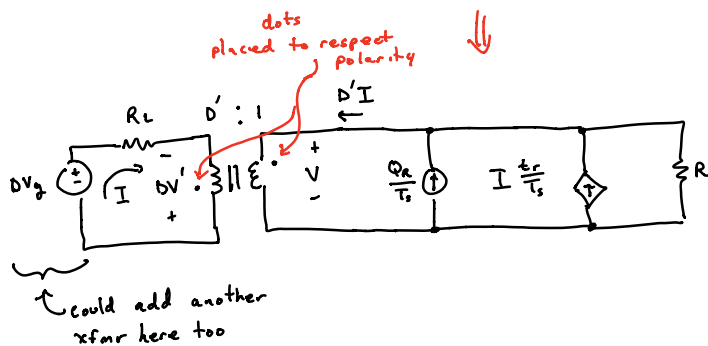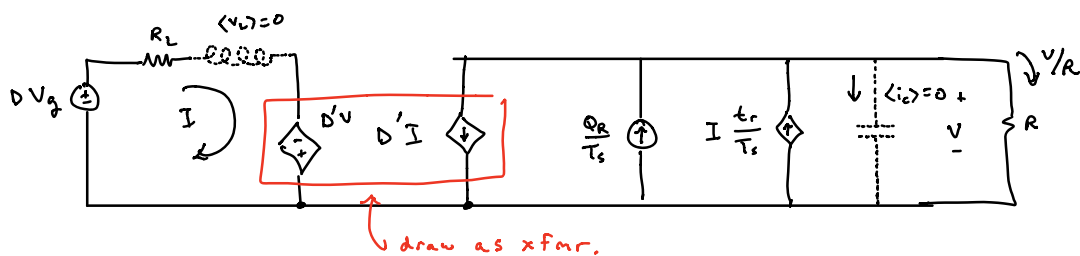


Final form with ideal x fms:

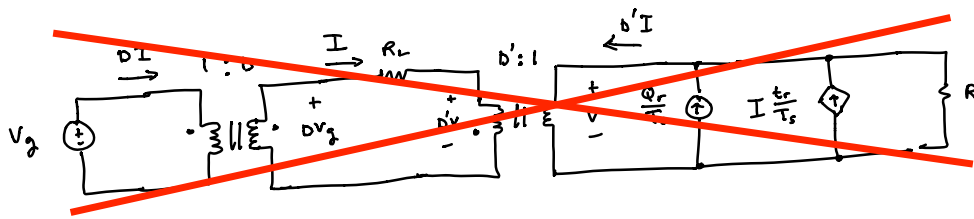

* correction


$$\langle P_{in} \rangle = V_g \langle i_T \rangle \neq V_g D I$$
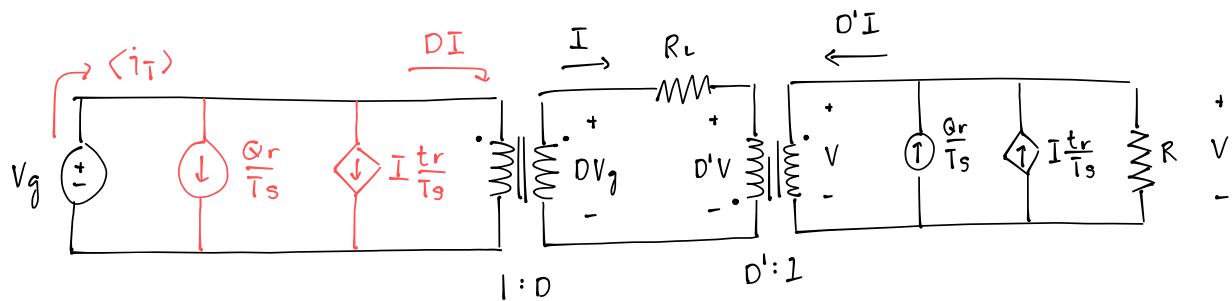
$$\langle i_T \rangle = D I + I_{tr}/T_s + Q_r/T_s$$




Problem # 2

a) Show DCM happens when $K < K_{crit}$.

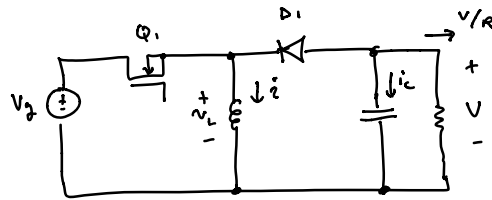

• Look @ ripple amplitude in CCM

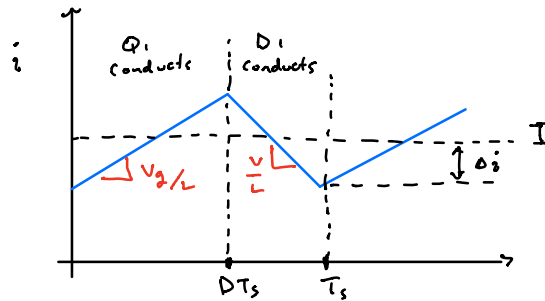

$$V_L = L \frac{2\Delta i}{\Delta t}$$

↳ look @ config when Q_1 conducts

$$\Rightarrow V_g = L \frac{2\Delta i}{DT_s}$$

$$\Rightarrow \Delta i = \frac{DT_s}{2L} V_g \quad (1)$$

In steady-state, it is well known that

$$M = \frac{V}{V_g} = \frac{-D}{1-D} \quad (2)$$

• Now look @ dc component of i using charge balance

$$\langle i_c \rangle = 0 = D \left(-\frac{V}{R} \right) + D' (-I - V/R)$$

(solve for I

$$\Rightarrow 0 = -\frac{V}{R} + D' (-I)$$

$$I = -\frac{V}{R D'}$$

* use (2)

$$= \cancel{\frac{1}{R(1-D)}} \left(\cancel{V_g} \underbrace{\frac{D}{1-D}}_V \right)$$

$$= \frac{V_g D}{R(1-D)^2} \quad (3)$$

$$= I$$

Using (1) & (3), CCM occurs if


$$\underbrace{\Delta i}_{\cancel{\frac{D T_s}{2L}} \cancel{V_g}} > \underbrace{I}_{\cancel{\frac{V_g D}{R(1-D)^2}}} \quad (4)$$

Put (4) into $\underbrace{K}_{\text{physics}} < \underbrace{K_{\text{crit}}}_{\text{control}}$ form

$$\rightarrow \boxed{\underbrace{(1-D)^2}_{K_{\text{crit}}} > \underbrace{\frac{2L}{R T_s}}_K} \quad \boxed{2a}$$

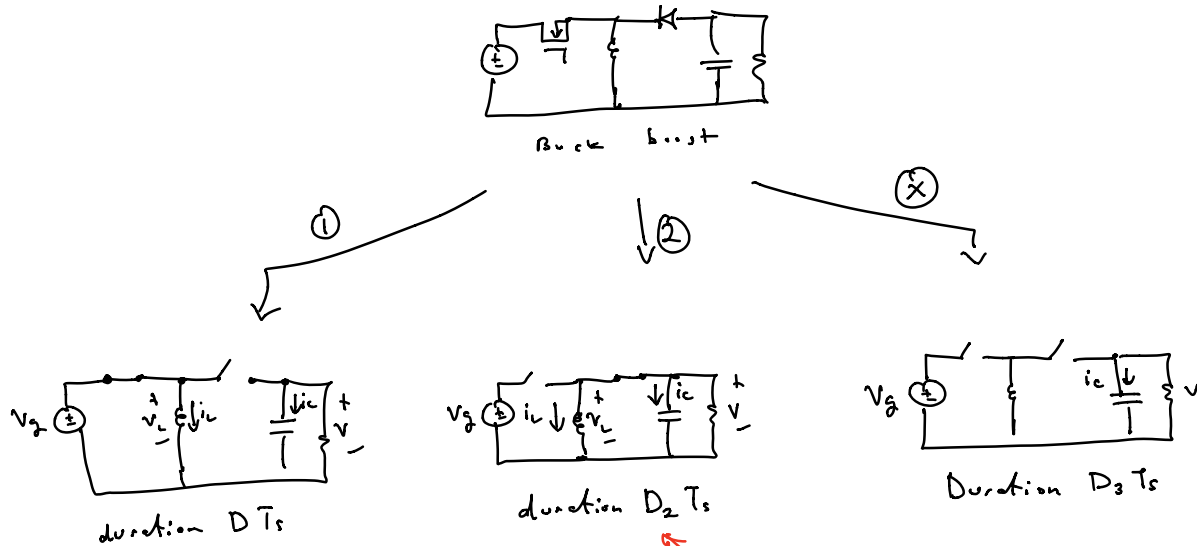2. b) Compute V/V_g .

First need to analyze 3 ckt configurations:



Need three golden equations to relate V , I , D_2


• Volt-sec balance gives:

$$\langle v_L \rangle = 0 = D(V_g) + D_2(\overset{\text{set okay for cap voltage.}}{V}) + D_3(0)$$

$$\begin{aligned} &= DV_g + D_2 V \\ &= 0 \end{aligned} \quad (5)$$

← key eqn for later

• Look @ KCL on load side

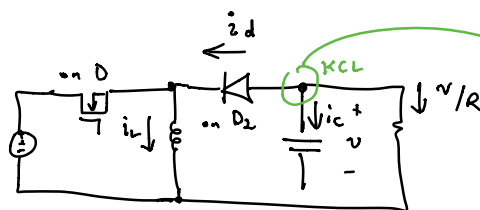

KCL gives pulsed diode current

$$i_c = -V/R - i_d \quad (6)$$

Take avg of both sides of (6)


$$\Rightarrow \langle i_c \rangle = -\frac{V}{R} - \langle i_d \rangle \quad (7)$$

↑ must be zero in s.s.

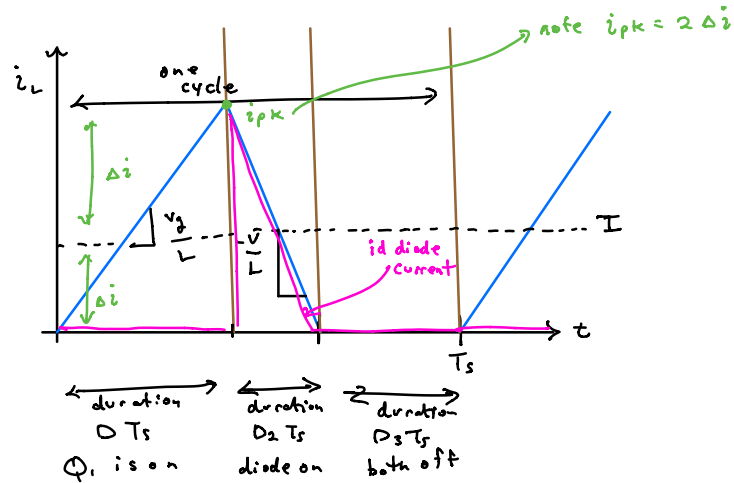(7) implies

$$\langle i_d \rangle = -\frac{V}{R} \quad (8)$$

• And now analyze i_L and i_d waveforms to get I and $\langle i_d \rangle$



Before computing $\langle i_L \rangle$ & $\langle i_d \rangle$, first compute i_{pk} . When Q_1 is on for duration $D T_s$ in config ①, we know $2 \Delta i = i_{pk}$. Hence,

$$\begin{aligned} v_L &= L \frac{2 \Delta i}{\Delta t} \\ \text{config ①} \rightarrow V_g &= L \frac{2 \Delta i}{D T_s} = L \frac{i_{pk}}{D T_s} \\ \Rightarrow i_{pk} &= V_g \frac{D T_s}{L} \quad (9) \end{aligned}$$

Integrate/average over 1 cycle to get $\langle i_L \rangle = I$ value:

$$\begin{aligned} \langle i_L \rangle &= I = \frac{1}{T_s} \underbrace{\int_0^{T_s} i_L(t) dt}_{\text{area}} \\ &= \frac{1}{T_s} \cdot \frac{1}{2} i_{pk} (D + D_2) T_s \\ &= \frac{i_{pk} (D + D_2)}{2} \\ &\quad \text{* use (9) for } i_{pk} \end{aligned}$$

$$\left. \begin{aligned} &= \frac{V_g D T_s}{L} \frac{(D + D_2)}{2} \\ &= I \end{aligned} \right\} (10)$$

And diode avg current is

$$\begin{aligned} \langle i_d \rangle &= \frac{1}{T_s} \int_0^{T_s} i_d(t) dt \\ &= \frac{1}{T_s} \frac{1}{2} i_{pk} D_2 T_s \\ &= \frac{i_{pk} D_2}{2} \\ &\quad * \text{use (9) again} \end{aligned}$$

$$\left. \begin{aligned} &= \frac{V_g D T_s}{L} \frac{D_2}{2} \\ &= \langle i_d \rangle \end{aligned} \right\} (11)$$

• 4 green boxes above are our key eqns. Rest is algebra to isolate V/V_g .

Use (5) to get D_2

$$D_2 = -D \frac{V_g}{V} \quad (12)$$

Now equate (8) & (11) for $\langle i_d \rangle$

$$\underbrace{-\frac{V}{R}}_{(8)} = \underbrace{\frac{V_g D T_s}{L} \frac{D_2}{2}}_{(11)}$$

* plug in (12) for D_2

$$\begin{aligned} &= \frac{V_g D T_s}{2L} \overbrace{\left(-D \frac{V_g}{V} \right)}^{D_2} \\ &= - \frac{V_g^2 D^2 T_s}{2VL} \end{aligned}$$

$$\Rightarrow \frac{v^2}{v_g^2} = \left(\frac{v}{v_g} \right)^2 = \underbrace{\frac{RT_s}{2L}}_{K^{-1}} D^2$$

$$= \frac{D^2}{K}$$

$$\left[\begin{array}{l} \text{recall} \\ K = \frac{2L}{RT_s} \end{array} \right.$$

$$\Rightarrow M = \left(\frac{v}{v_g} \right) = \sqrt{\frac{D^2}{K}}$$

$$= \frac{D}{\sqrt{K}}$$

$$= \frac{v}{v_g}$$

2b

3c) Plot v/v_g for $K = 0.1$ for $0 \leq D \leq 1$.

$$\frac{v}{v_g} = \frac{D}{\sqrt{0.1}} \approx 3.16 D$$

