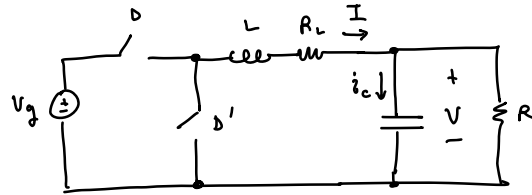


Solution



where

$$V_g = 40V$$

$$V = 20V$$

$$f_s = 50kHz$$

$$R \geq R_{min} = 4\Omega$$

a) Find L such that $\Delta i / I = 0.1$

- Ignore R_L effect for now since it is very small and has minimal impact on result.
- Volt-second balance gives

$$\begin{aligned} 0 &= (V_g - V)D + (-V)D' \\ &= DV_g - V \\ \Rightarrow D &= \frac{V}{V_g} \end{aligned}$$

- Charge balance gives

$$\begin{aligned} 0 &= (I - V/R)D + (I - V/R)D' \\ &= I - V/R \\ \Rightarrow I &= V/R \end{aligned}$$

* look @ heaviest load when $R = R_{min} = 4\Omega$

$$\begin{aligned} &= \frac{V}{R_{min}} \\ &= I \end{aligned} \quad (1)$$

- Look @ ripple:

$$V_L = L \frac{2\Delta i}{\Delta t}$$

* see config ①

$$\Rightarrow (V_g - V) = L \frac{2\Delta i}{DT_s} \quad (2)$$

$$\begin{array}{l}
 \text{need } \frac{\Delta i}{I} = 0.1 \Rightarrow \Delta i = 0.1 I \\
 \& \tau_s = \frac{1}{f_s} \\
 \& (1) \text{ gives us } I.
 \end{array}
 \left. \vphantom{\begin{array}{l} \text{need } \frac{\Delta i}{I} = 0.1 \Rightarrow \Delta i = 0.1 I \\ \& \tau_s = \frac{1}{f_s} \\ \& (1) \text{ gives us } I. \end{array}} \right\} \text{ plug into (2)}$$

Substituting into (2) gives


$$\begin{aligned}
 V_g - V &= L \frac{2 \overbrace{\frac{1}{10} I}^{\Delta i}}{D/f_s} \\
 &= L \frac{f_s I}{5D} \quad \text{--- } V/R_{\min} \\
 &= L \frac{V f_s}{5 R_{\min} D}
 \end{aligned}$$

solve for L $D = \frac{V}{V_g} = \frac{20V}{40V} = 0.5$

$$\begin{aligned}
 L &= \frac{(V_g - V) 5 R_{\min} D}{V f_s} \\
 &= \frac{(40V - 20V) 5 \times 4\Omega \times 0.5}{20V \times 50 \text{ kHz}}
 \end{aligned}$$

$$= \boxed{200 \mu\text{H} = L}$$

b) Determine I_{\max}

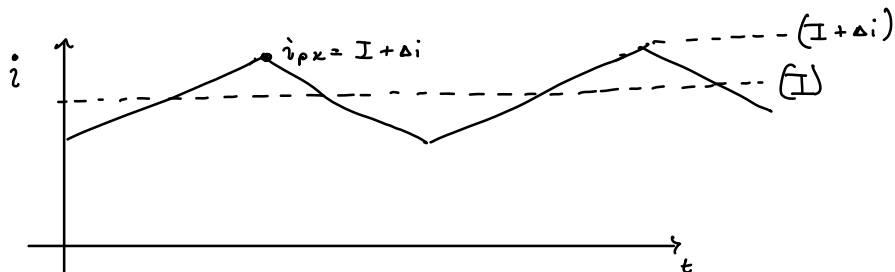

$$i_{pk} = I + \Delta i$$

$$= I + 0.1I$$

$$= 1.1I$$

use (c)

$$= 1.1 \underbrace{\frac{V}{R_{min}}}_{= i_{pk}}$$

↳ i_{pk} is the theoretical exact peak of the current.

• In real applications, need to deal with transients and other cases where i might exceed i_{pk} momentarily.

• A more practical choice is

$$\rightarrow \text{Pick } I_{max} = 1.25 \underbrace{i_{pk}}_{\substack{\text{gives 25\%} \\ \text{"safety" margin}}}$$

$$\boxed{\begin{aligned} &= 1.25 \times 1.1 \frac{V}{R_{min}} \\ &= I_{max} \end{aligned}}$$

↑ this solution uses engineering judgement and is not unique.

c) Design inductor via K_L method.

$$\text{Goal: Need } I^2 R_L \leq P_{loss, max} = 1W$$

$$\hookrightarrow R_L \leq \frac{P_{loss, max}}{I^2}$$

$$\text{let } R := \frac{P_{loss, max}}{I^2} = \text{max allowable resistance}$$

Step 1) Pick core big enough

$$K_g = \frac{\rho L^2 I_{max}^2}{B_{max}^2 R K_u} 10^8$$
$$= \frac{\rho L^2 \left(1.25 \times 1.1 \times \frac{V}{R_{min}}\right)^2}{B_{max}^2 R K_u} 10^8$$

* evaluate at

$$\rho = 2.3 \times 10^{-6} \Omega \cdot \text{cm} @ 100^\circ\text{C}$$

$$L = 200 \mu\text{m}$$

$$V = 20 \text{ V}, R_{min} = 4 \Omega$$

$$B_{max} = 0.25 \text{ T}$$

$$K_u = 0.5 \leftarrow \text{realistic utilization factor}$$

$$\approx 347.9 \times 10^{-3} \text{ cm}^5$$

Look @ table. Smallest available core which exceeds K_{gmin} above is

$$\rightarrow K_g = 0.909 \text{ cm}^5 \text{ for "EES0" geometry}$$

core size chosen

Step #2) Pick air gap

$$l_g = \frac{\mu_0 L I_{max}^2}{B_{max}^2 A_c} 10^4$$

$$* \text{ where } A_c = 2.26 \text{ cm}^2 \text{ for EES0}$$

$$\approx 841 \mu\text{m} = l_g$$

Step # 3) Pick Turns

$$n = \text{round} \left(\frac{L I_{\max}}{B_{\max} A_c} 10^4 \right)$$

* where $A_c = 2.26 \text{ cm}^2$ for EES0

$$= 25 \text{ turns} = n$$

Step 4) Check wire size

$$A_w \leq \frac{k_u W_A}{n} [\text{cm}^2]$$

$$* W_A = 1.78 \text{ cm}^2$$

$$\approx 35.6 \times 10^{-3} \text{ cm}^2$$

\Rightarrow implies need AWG # 12 or above (smaller wire)

$$\bullet \text{ AWG \# 12 } A_w = 33.1 \times 10^{-3} \text{ cm}^2.$$

Sanity check

$$\text{Check } R_{\text{actual}} = \frac{\rho n (\text{MLT})}{A_w}$$

$$* (\text{MLT}) = 10 \text{ cm for EES0}$$

$$= \frac{(2.3 \times 10^{-6} \Omega\text{-cm}) (25) (10 \text{ cm})}{33.1 \times 10^{-3} \text{ cm}^2} \approx 17 \text{ m}\Omega$$

$\underbrace{\text{R @ dc}}_{\text{"actual"}}$
 $\underbrace{R = 40 \text{ m}\Omega}_{\text{max R value we targeted}}$

$\swarrow \searrow$
 success! we hit our target.