

Lecture # 4, 10/6/2021

Last time:

- 1st  $\frac{1}{2}$  of motor modeling doc.

→ Finish 2nd  $\frac{1}{2}$  on Friday.

Today


- Ch 2, "balance equations"

- HW1 due next Monday 11:59 pm PT.

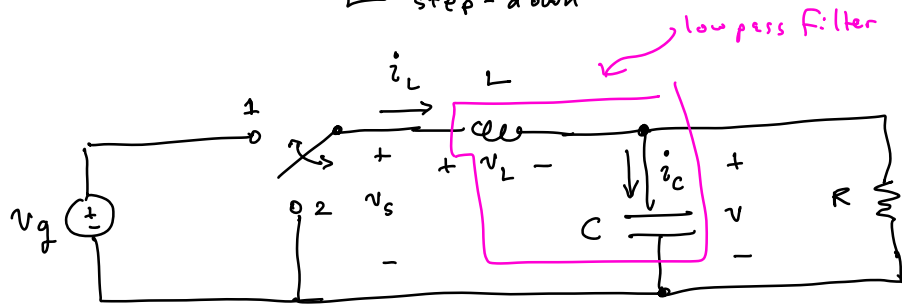
# Chapter 2 → Steady-state Analysis

periodic steady state due to switching

Consider the "Buck" converter  
 ↓ step-down



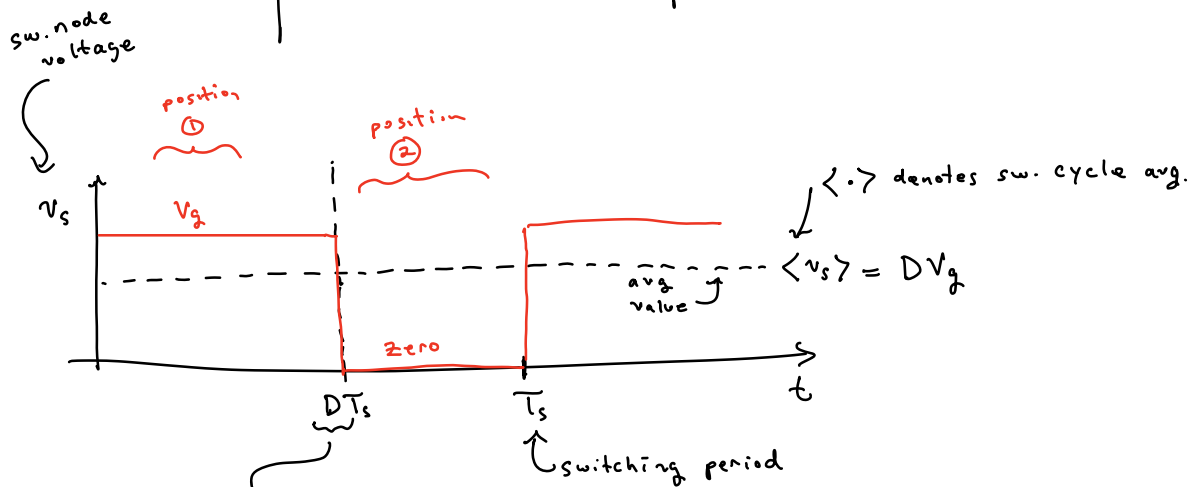A comment on polarity / sign conventions for analysis



D is "duty ratio"

$$0 < D < 1$$

$$D = \frac{\text{time on}}{T_s}$$

$$f_s = T_s^{-1}, \text{ typically kHz to MHz range}$$

Avg value = dc component

$$\begin{aligned}\langle v_s \rangle &= \frac{1}{T_s} \int_0^{T_s} v_s(t) dt \\&= \frac{1}{T_s} \left( \int_0^{DT_s} v_g dt + \int_{DT_s}^{T_s} \cancel{\text{zero}} dt \right) \\&= \frac{1}{T_s} v_g \underbrace{\int_0^{DT_s} 1 dt}_{DT_s} \\&= \frac{DT_s}{T_s} v_g \\&= D v_g\end{aligned}$$

Q: What about the output voltage?

A: LC is a lowpass filter. Dc component <sup>of sw. terminal voltage</sup> appears @ output.




$$\Rightarrow v = D v_g$$

$$\rightarrow \underbrace{\frac{v}{v_g} = \frac{\text{output}}{\text{input}} = D}_{\text{ratio called "M" in book}} \rightarrow \text{s.s. voltage conversion ratio}$$

specific to buck

\* Need a more generalized method to derive  $\frac{v}{v_g} = M$   
for any converter

## Overview of 3 common converters

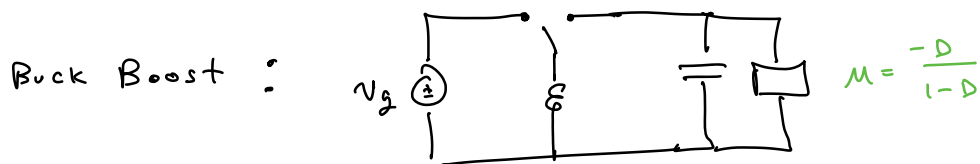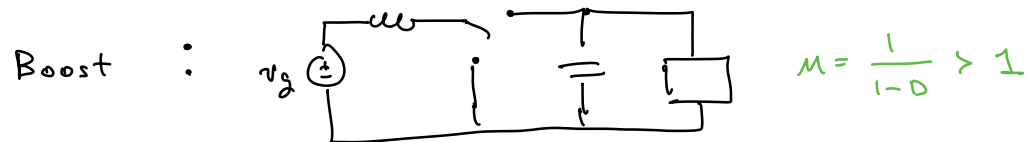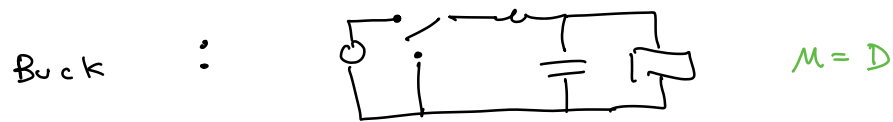

General method to derive  $M$  hinges on


→ volt-second balance for  $L$ 's

→ charge (AKA amps-seconds) balance for  $C$ 's

Intuition:

Energy doesn't build up in  $L$ 's &  $C$ 's of the converter. Input energy goes to output.

## Buck converter wave forms

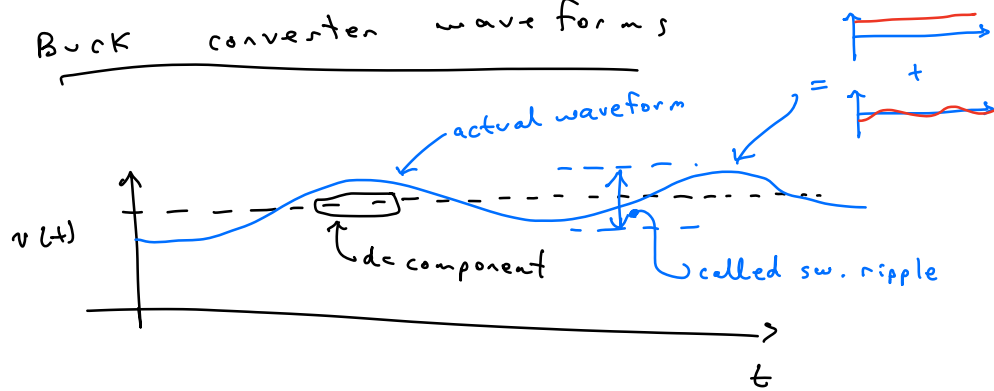


$$v(t) = \underset{\substack{\uparrow \\ \text{dc comp.}}}{V} + v_{\text{ripple}}(t)$$

In most designs  $\|v_{\text{ripple}}\| < V$

and  $v(t) \approx V$

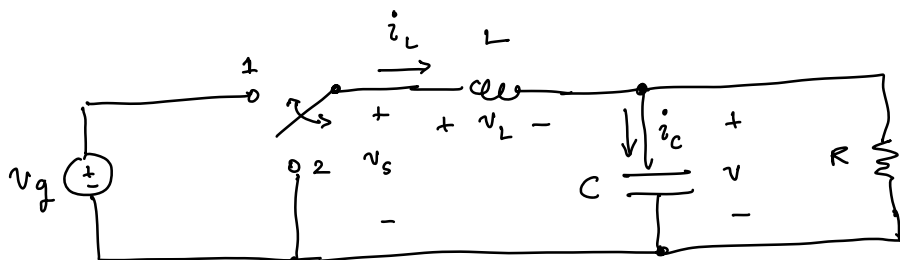
## General Method to Derive S.S. Input-Output Relations

- Start w/ a given converter ckt.
  - Draw diagram for each sw. config. & compute ckt voltages & currents
- and get all S.S. I's & V's in ckt



config

①

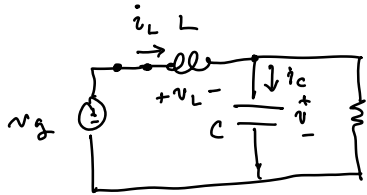

• Look @ L voltage

$$v_L = v_g - v \quad (1)$$

b/c small ripple @ output

$$v \approx V = \text{dc component}$$

Hence, (1) becomes

$$v_L = v_g - V \quad (2a)$$

$$L \frac{di_L}{dt} = v_L \quad (3a)$$


$$= \underbrace{v_g - V}_{\text{constant}}$$

$$\Rightarrow \frac{di_L}{dt} = \frac{v_g - V}{L}$$

⊕ slope

config

②

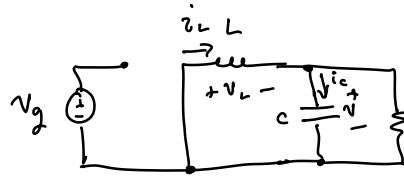

• Inductor voltage

$$v_L = -v$$

... small ripple ...

$$v_L = -V \quad (2b)$$


$$L \frac{di_L}{dt} = v_L \quad (3b)$$

$$= -V$$

$$\frac{di_L}{dt} = \frac{-V}{L}$$

⊖ slope

Look @  $V_L$  wave for  $n$  s

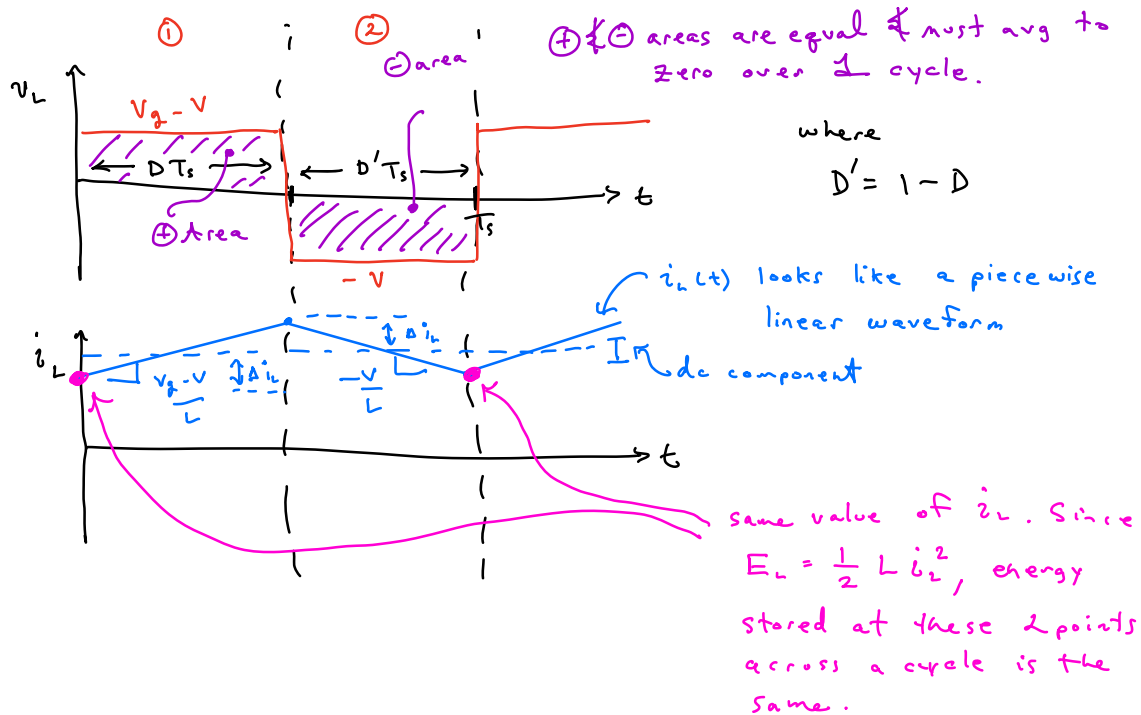

Principle of volt-second balance

know  $V_L = L \frac{di_L}{dt} \rightarrow \frac{di_L}{dt} = \frac{V_L}{L}$

in integral form  $\rightarrow \overbrace{i_L(T_s) - i_L(0)}^{\text{zero}} = \frac{1}{L} \int_0^{T_s} V_L(t) dt$

init.      final

b/c final & initial values same in steady state

$$\Rightarrow 0 = \frac{1}{L} \int_0^{T_s} V_L(t) dt$$

÷ by  $L$  &  $\times$  by  $\frac{1}{T_s}$

rewrite as  $0 = \frac{1}{T_s} \int_0^{T_s} V_L(t) dt = \langle V_L \rangle$

area under curve

Area above & below in rectangles must be equal

area under  $v_L$  curve

$$\lambda = \int_0^{T_s} v_L(t) dt = (V_g - V) \cancel{(DT_s)} + (-V) \cancel{(D'T_s)} = 0$$

zero in s.s.

volt-sec balance eqn.

Solve for  $V$

$$0 = (V_g - V) D - V \overbrace{(1-D)}^{D'}$$

$$= DV_g - V$$

$$\Rightarrow V = DV_g$$

$$\rightarrow M = \frac{V}{V_g} = \frac{DV_g}{V_g} = D$$

• What about Cap? ↴

• Principle of cap charge balance

$$i_c(t) = C \frac{dv(t)}{dt} \rightarrow \frac{dv}{dt} = \frac{i_c}{C}$$

integral form

$$\underbrace{v(T_s) - v(0)}_{\text{zero}} = \frac{1}{C} \int_0^{T_s} i_c(t) dt$$

same


$$0 = \frac{1}{C} \int_0^{T_s} i_c(t) dt \quad \times \text{ by } C, \div \text{ by } T_s$$

$$0 = \frac{1}{T_s} \underbrace{\int_0^{T_s} i_c(t) dt}_{\text{charge}} = \langle i_c \rangle \quad \text{Avg value}$$




$$\text{charge} = \int_0^{T_s} i_c(t) dt$$

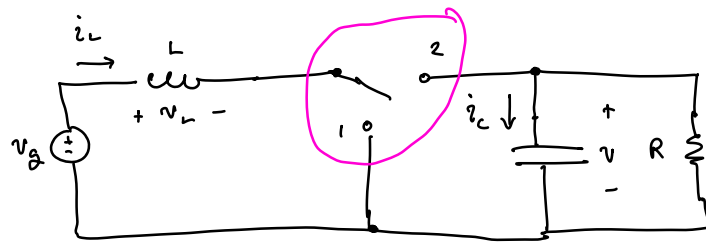- Boost Example to see both balance equations




↓ realization

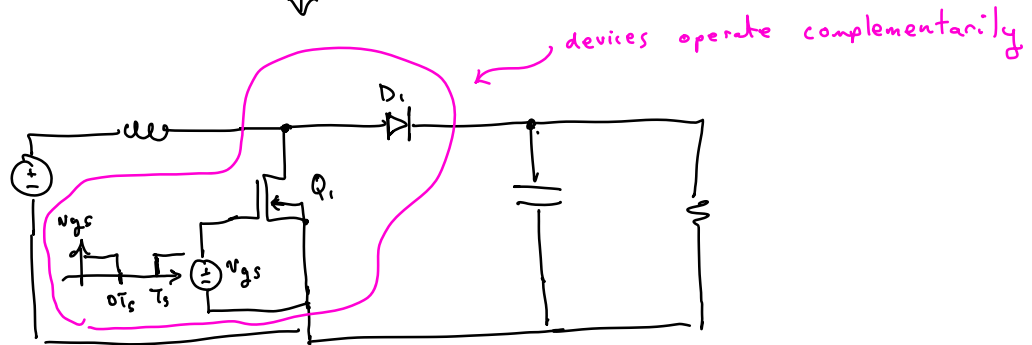


Back to analysis

config ①

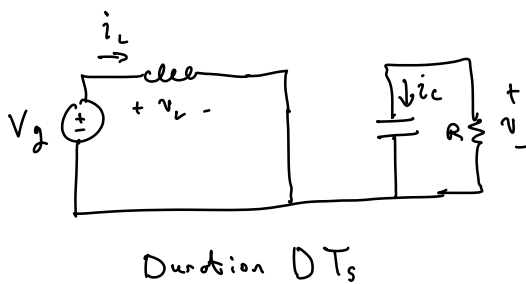

config ②

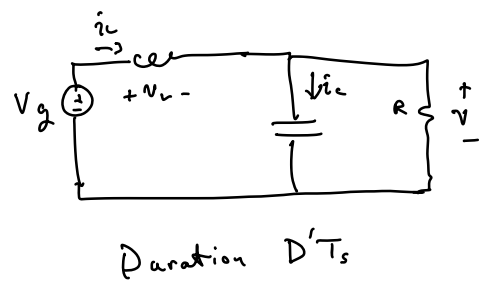

inductor  $v_L \neq$  cap  $i_c$

$$v_L = V_g$$

$$i_c = -v/R$$

inductor  $v_L \neq$  cap  $i_c$

$$v_L = V_g - v$$

$$i_c = i_L - v/R$$

apply small  
ripple approx

$$v_L = V_g$$


$$i_c = -V/R$$

$$v_L = V_g - V$$

$$i_c = I - \frac{V}{R}$$

$$\rightarrow v \approx V, i_L = I$$

Look @ waveforms

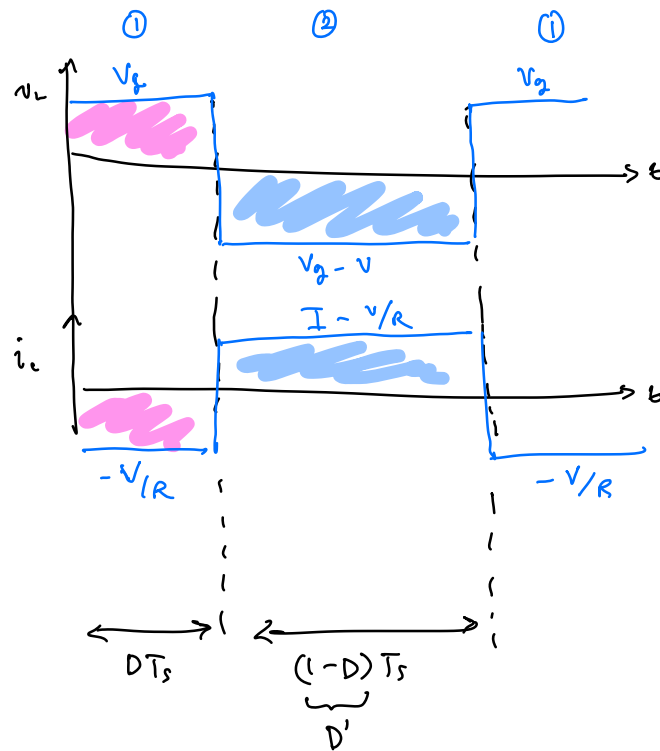

write balance equations

volt second:

$$0 = \underline{(V_g)(DT_s)} + \underline{(V_g - V)(1-D)T_s}$$

solve for V

$$0 = V_g (\cancel{D} + \cancel{1-D}) - V(1-D)$$

$$\rightarrow V = \frac{V_g}{1-D} (*)$$

$$\rightarrow \boxed{M(D) = \frac{V}{V_g} = \frac{1}{1-D}}$$

Boost conversion

Charge balance ... needed to set I

$$0 = \underline{(-V/R)(DT_s)} + \underline{(I - V/R)(1-D)T_s}$$

solve for I

$$0 = -\frac{V}{R} (\cancel{D} + \cancel{1-D}) + I(1-D)$$

$$I = \frac{V}{(1-D)R}$$

substitute expression of V ... use (\*)

$$\Rightarrow \boxed{I = \frac{V_g}{(1-D)^2 R}}$$