



Logistics:

- Lab 1B deadline question
see announcement
- Lab 1 report due 2 weeks
after lab 1C

Lab 2A: current sensing and overvoltage protection.

1. Layout all components. Do not need to solder.

Full ckt:

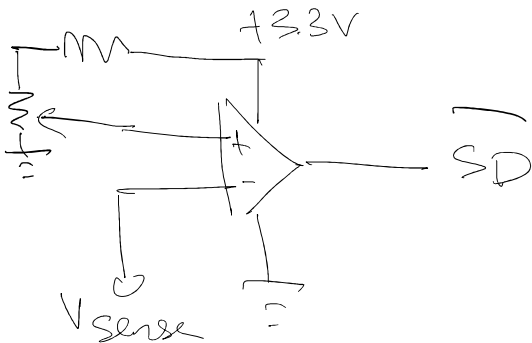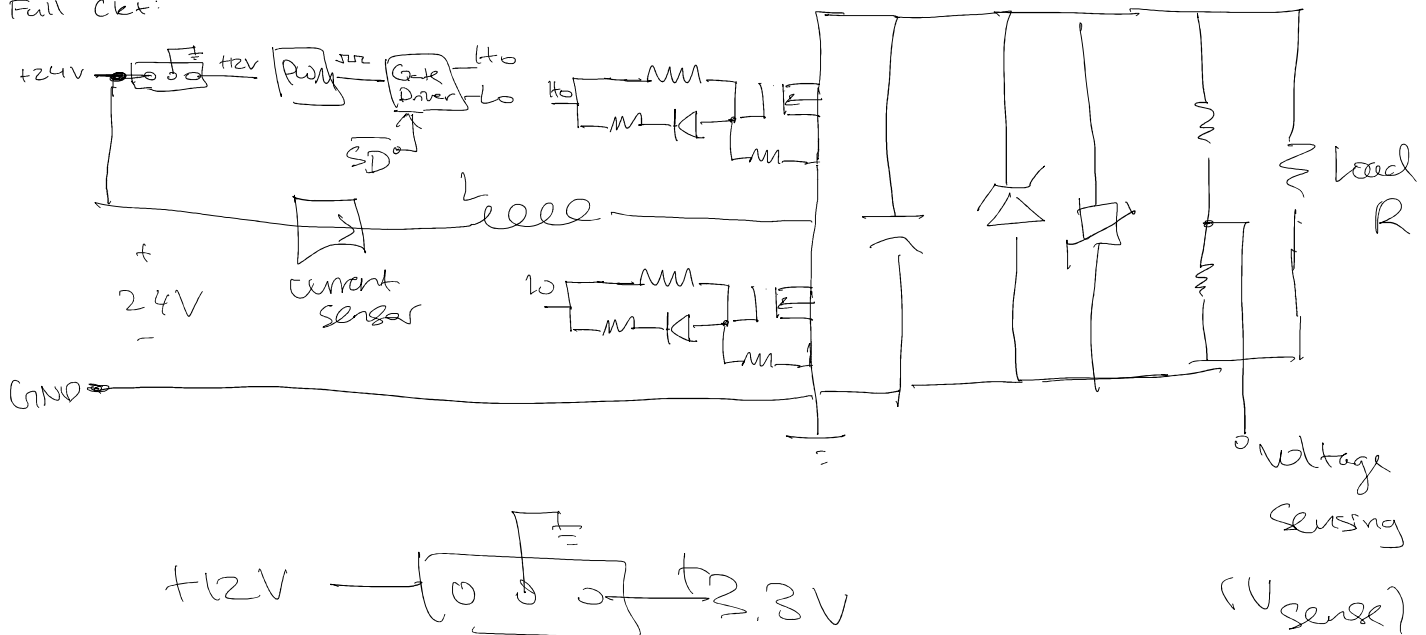


overvoltage protection

Chef

For Lab 2A:

do NOT connect gate driver to MOSFETS or output capacitor, diode, MOV to load.

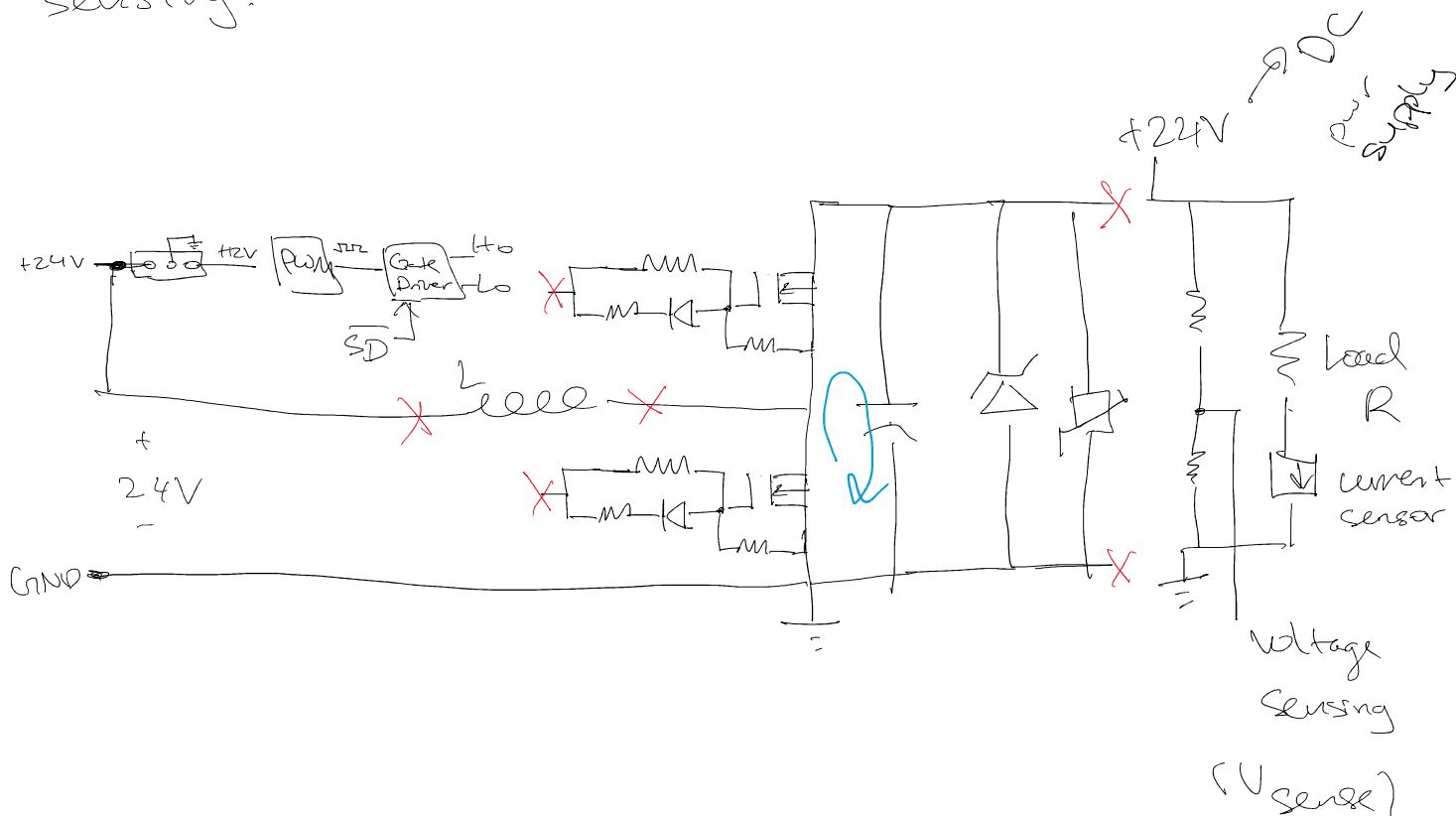Jump power supply to load to test sensing.



size output voltage divider


to handle 0-60V. $V_{\text{sense}} [0, 3.3V]$

So at 60V, output $\geq 3V$. Test with $[20-30]V$.

Note: current sensor on load just to test it. will move to L later.

Note: Load $[100-400] \Omega$. Can change to test different currents.

Comparator Review:

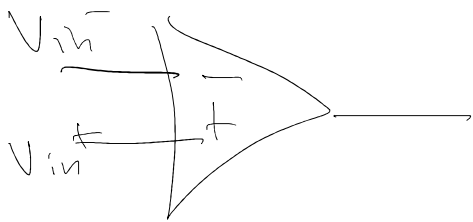

$V_{in}^- > V_{in}^+$ Low


$V_{in}^- < V_{in}^+$ HIGH

Layout considerations:

- keep switching nodes SMALL
- Switch node drawn in blue

Note: load resistors may get hot

current sensor sensitivity:

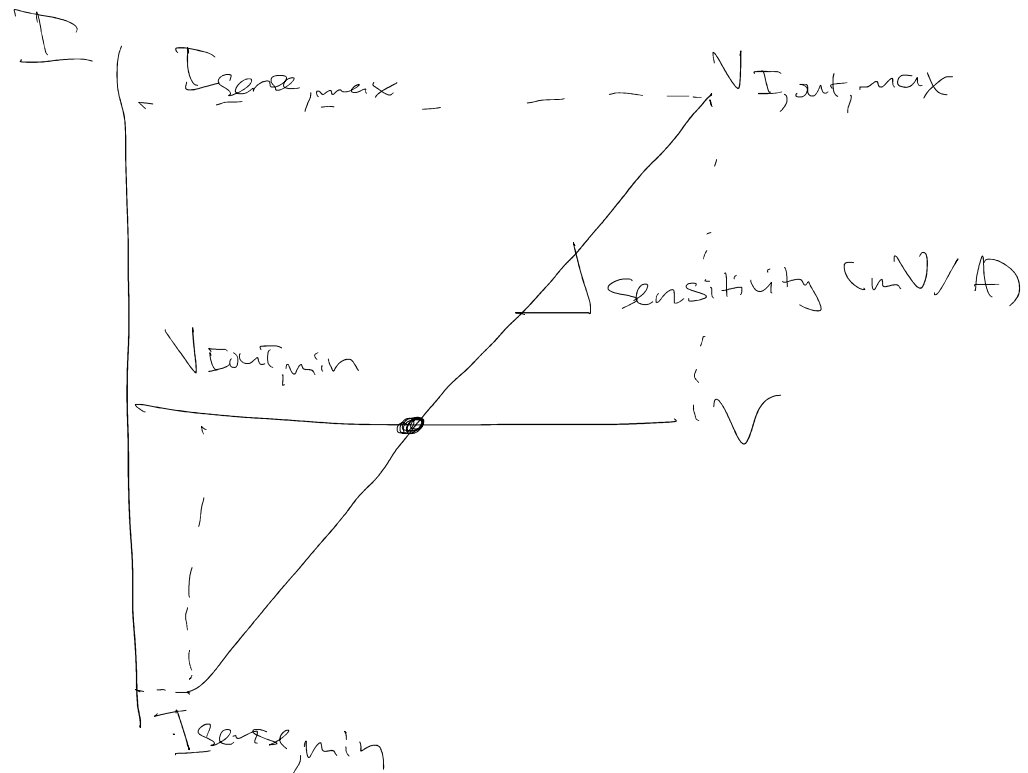

find in datasheet