

## Lecture # 28, 12/8/21


- Final exam = next Monday, 4:30-6:20 pm } • do a review on Friday. See Canvas for guiding documents.
- HW 8 due Friday
- Closed notes, eqn sheet provided (on Canvas now)

• Final Report for lab due Weds 12/15 @ Noon.

- Last time: Flyback converter (isolated converters)
- Today: Ch 6, voltage source inverters  
    ↑ dc-ac converters


### - Differential Connections

\* Enables generation of ac waveforms.

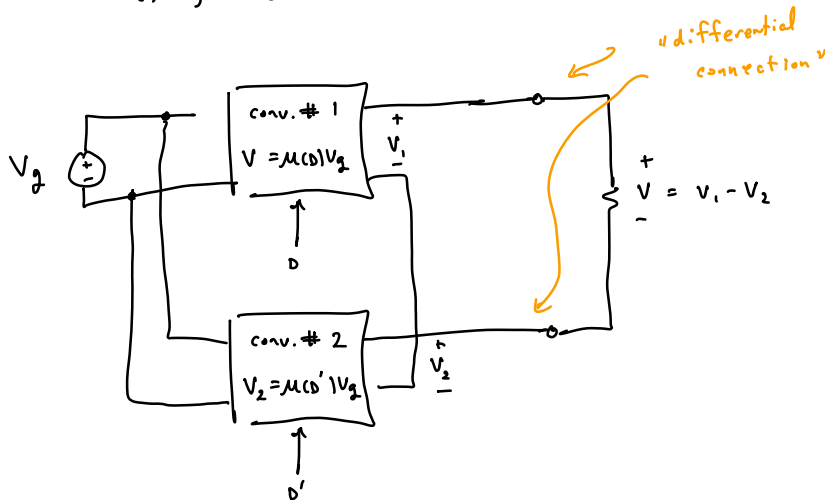


Even if  $V_1$  &  $V_2$  are  $\oplus$ , the diff  $V_1 - V_2$  can be manipulated to produce an ac waveform.

- 2 differential Bucks

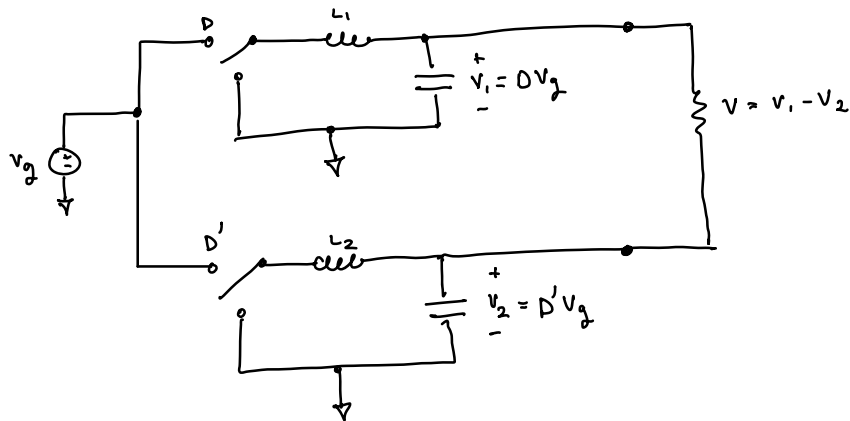
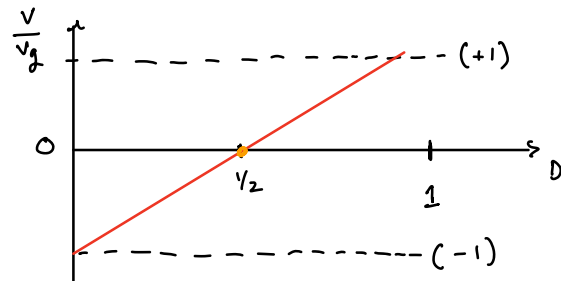
$$\begin{aligned}
 V &= V_1 - V_2 \\
 &= DV_g - (1-D)V_g \\
 &= V_g (2D - 1) \quad (1)
 \end{aligned}$$




to get ac waveform, pick duty

$$D(t) = \frac{1 + m \sin(\omega t)}{2} \quad (2)$$

often called "modulation depth"  
 $0 < m < 1$


(2)  $\rightarrow$  (1) to get

$$V = V_g m \sin(\omega t)$$

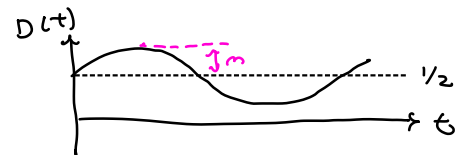


• Modify cnt to get "practical" realization

step #1: move filter caps across load

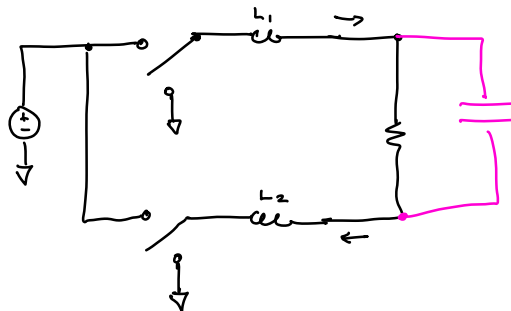

step #2: Lump  $L_1$  &  $L_2$  together

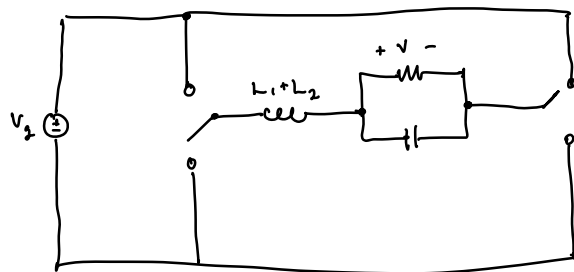

Known a  
"H-bridge"  
or  
"Full-bridge"

↳ gives an ac waveform @  $V$


↳ called a "single-phase" inverter

\* key idea:

$|V| < V_g \rightarrow$  preserves "step-down/buck" behavior.

- 3 phase ac

• start w/ 3 bucks

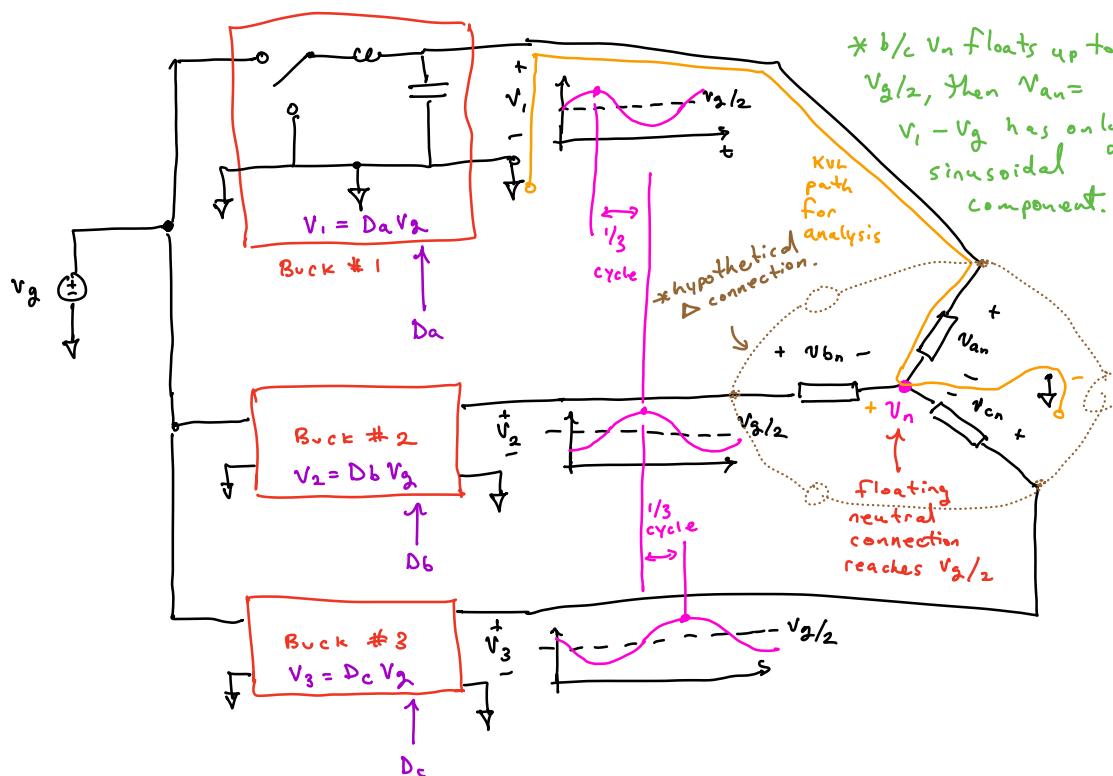

For balanced 3 $\phi$  ac, pick duties

$$D_a = \frac{1 + m \sin(\omega t)}{2} \longrightarrow v_1 = V_g D_a = \frac{V_g}{2} (1 + m \sin(\omega t))$$

$$D_b = \frac{1 + m \sin(\omega t - \frac{2\pi}{3})}{2} \longrightarrow v_2 = \text{"} = \text{"} - - - (\omega t - \frac{2\pi}{3})$$

$$D_c = \frac{1 + m \sin(\omega t + \frac{2\pi}{3})}{2} \longrightarrow v_3 = \text{"} = \text{"} - - - (\omega t + \frac{2\pi}{3})$$

• Look @ KVL for each phase loop

KVL for A gives  $v_1 - v_{an} = v_n$

" B  $v_2 - v_{bn} = v_n$

" C  $v_3 - v_{cn} = v_n$

$$\xrightarrow{\text{sum eqns}} v_1 + v_2 + v_3 - (v_{an} + v_{bn} + v_{cn}) = 3v_n$$

↓  
0 b/c balanced load

$$\Rightarrow v_n = \frac{1}{3} (v_1 + v_2 + v_3) = \text{avg of 3 buck voltages}$$

$$= \frac{V_g}{2}$$