

Lecture #2 10/1/2021

Logistics

- PLECS → Install using license codes
 Brian sent today
 └→ tailored for switching converters

Today

- └→ Motor modeling handout } for lab # 1
 OR
└→ Power Electronics Ch 1, basics


- Energy & Power, physics recap



diff between P & E ?


$$P = \frac{dE}{dt} = \text{rate at which energy flows}$$
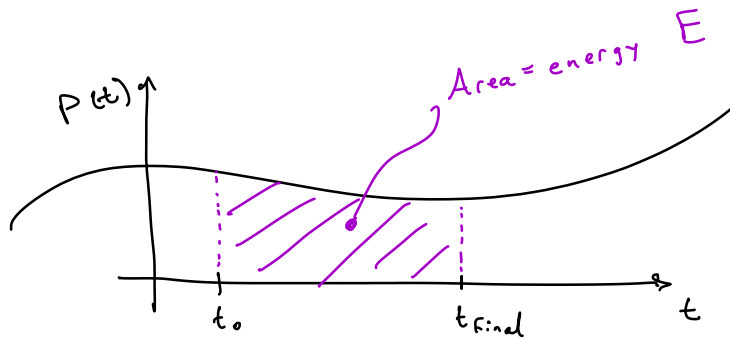
$$E(t) = \int_{\tau=t_0}^{\tau=t_{\text{final}}} P(\tau) d\tau$$




Forms of Energy

• Kinetic Energy

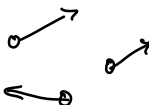


$$E = \frac{1}{2} m v^2$$

• Electric Field

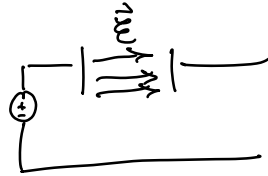


$$E = \frac{1}{2} \epsilon \vec{E}^2 \times \text{volume}$$

• Magnetic Field

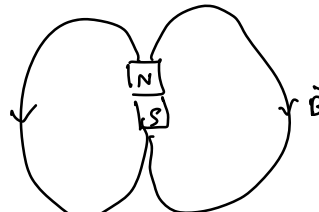

$$E = \frac{1}{2} \frac{\vec{B}^2}{\mu} \times \text{volume}$$


Lossy Elements



$$P_{\text{loss}} = i^2 R$$


lossy

Capacitor

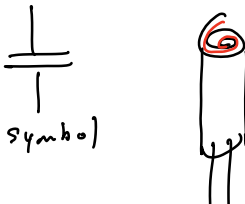

$$E = \frac{1}{2} C v^2$$

Inductors

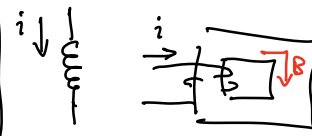


$$E = \frac{1}{2} L i^2$$

Transferring Power / Energy w/ ckt's


store energy

• Naive approach to power transfer

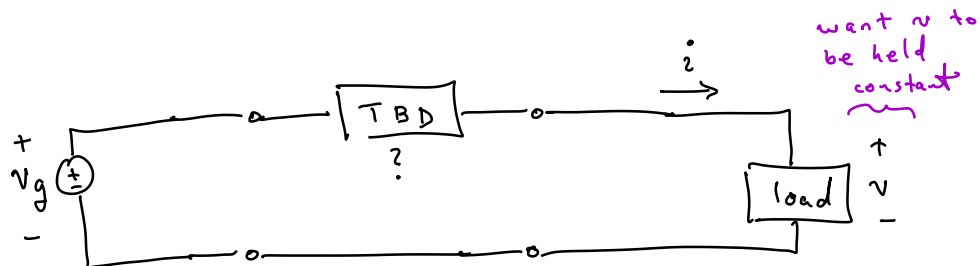

Goal: Regulate v to a target/desired value
 where $v < v_g$ v_{ref}


Options. 1) Resistive divider

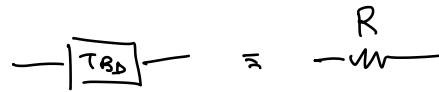

X Only works if load resistance is known & fixed

X $P_{loss} = i^2 R$ ← very lossy!

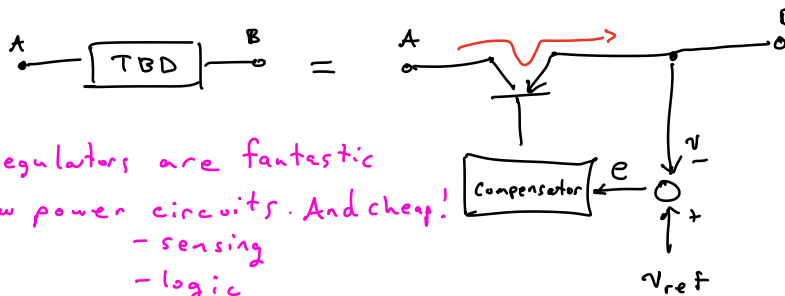2) Linear regulators (not power electronics)




∴ linear regulators are fantastic
for low power circuits. And cheap!
- sensing
- logic

✓ Solves problem of load resistance being unknown.
Behaves as a self-tuning resistor


X $P_{loss} = (V_g - V)i$ ← still lossy!

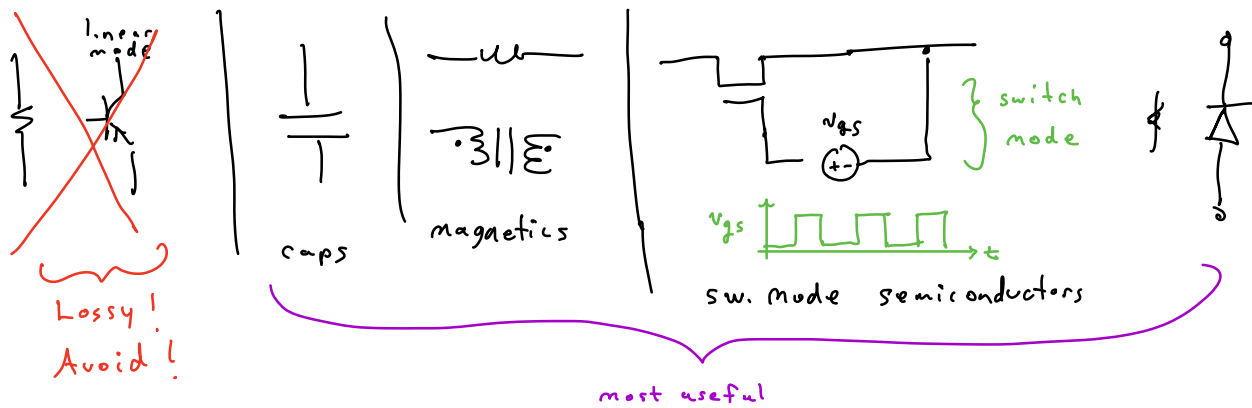— What are sw. power converters built from



Why are these items "useful"?

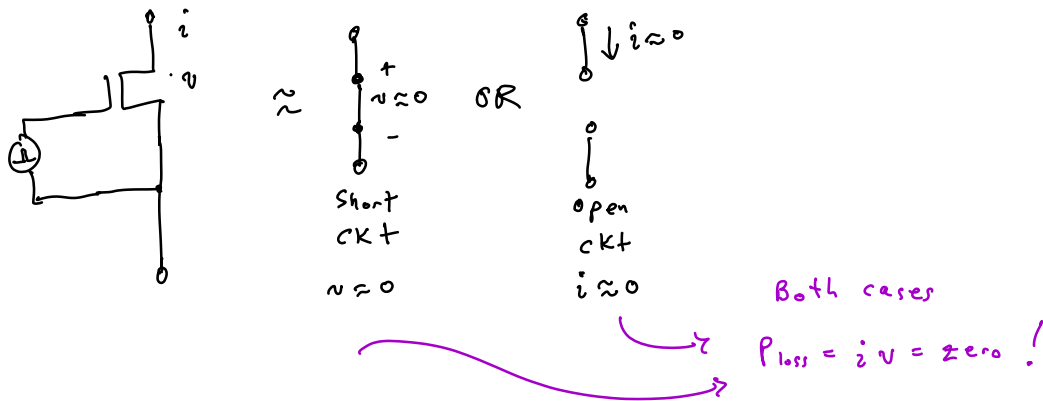$\frac{1}{s}, \frac{1}{s^2}$ store/release energy, ideally don't dissipate energy.



Main idea:

- Switches, which are (ideally) lossless, route power to L's & C's which store energy.
- Periodic switching action passes energy from input to output.

$\uparrow \uparrow \uparrow$ Ch 1

Look Ahead:


- Spend a few lectures on ch 2

\rightarrow Steady state analysis


* To do: Read Ch 2 over next 1 week.

Chapter 2

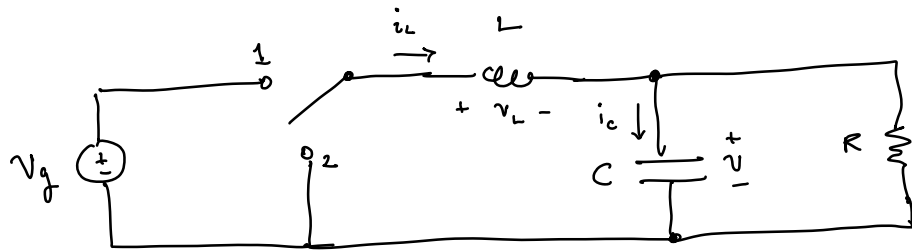Consider the "Buck" converter
└ step-down



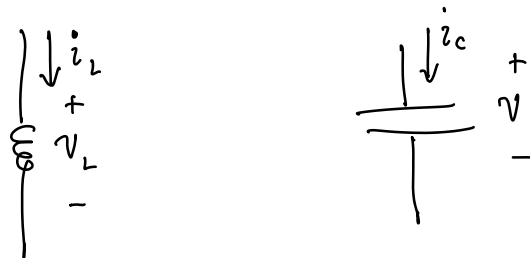A comment on polarity / sign conventions for analysis



... will continue in Lect #3