

### Problem 1: Conceptual Questions [20 Points Total]

#### Converters and devices.

- (a) [5 Points] Why is the flyback converter useful in applications where large voltage conversion ratios are needed?

The conversion ratio is  $v/v_s = n \frac{D}{1-D}$ , where  $n$  can be chosen to give a large (or very small) conversion ratio. This allows you to keep  $D$  in a range where efficiency is high.

- (b) [5 Points] In converters with half-bridges, dead-time is necessary. What is dead-time and why is it needed?

- Deadtime is the interval where both devices have a low gate-source voltage & should not conduct.
- This avoids a potential short circuit which is caused by devices having a non-zero turn-on & turn-off transition times.

#### Magnetics.

- (a) [5 Points] A ferromagnetic material is exposed to an external magnetic field  $B_{\text{vac}}$ . Why is the magnetic field inside the material larger than  $B_{\text{vac}}$  and how does this relate to the material permeability  $\mu$ ? Describe what is happening at the atomic level inside the material.

- Field in material is higher b/c dipoles in material align w/  $\tilde{B}_{\text{vac}}$  & contribute additional flux density.
- $\mu$  is proportional to how easily dipoles in material align with an external field  $\tilde{B}_{\text{vac}}$ .

- (b) [5 Points] What is saturation and what is the effective permeability of a material during saturation? Describe what is happening at the atomic level inside the material.

- All dipoles are fully aligned w/  $\tilde{B}_{\text{vac}}$  during saturation.
- effective permeability is  $\mu_0$  (free space permeability).

**Problem 2: Magnetics [30 Points Total]** Consider the magnetic core in Fig. 1. Assume that the core geometry was designed such that the reluctance through path a, path b, and path c are identical with value  $\mathcal{R}$ . Winding #1 has  $n_1$  turns.


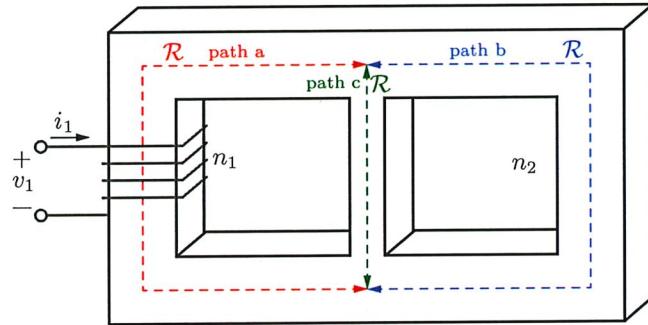


Figure 1: A magnetic core with one coil.

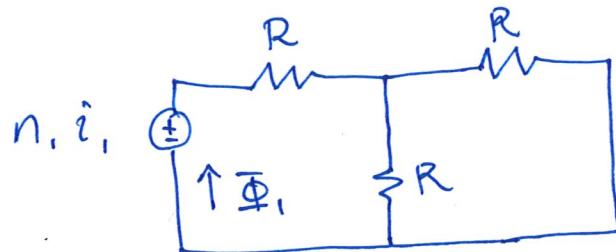(a) [5 Points] Draw the magnetic circuit model of this device.



(b) [5 Points] Compute the inductance,  $L$ , for coil #1 in terms of  $\mathcal{R}$  and  $n_1$ .

- Ampere's Law:  $n_1 i_1 = \Phi_1 (R + \underbrace{R/2}_{R_{II}R})$

$$= \frac{3}{2} \Phi_1 R$$

$$\Rightarrow \Phi_1 = \frac{2}{3} n_1 i_1 \frac{1}{R}$$

- Faraday's Law:  $v_1(t) = n_1 \frac{d\Phi_1}{dt} = \underbrace{\frac{2 n_1^2}{3R}}_L \frac{di_1}{dt}$

$$\Rightarrow L = \frac{2 n_1^2}{3R}$$


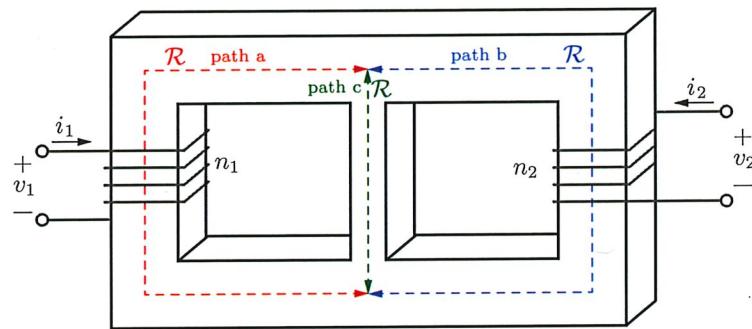


Figure 2: A magnetic core with two coils.

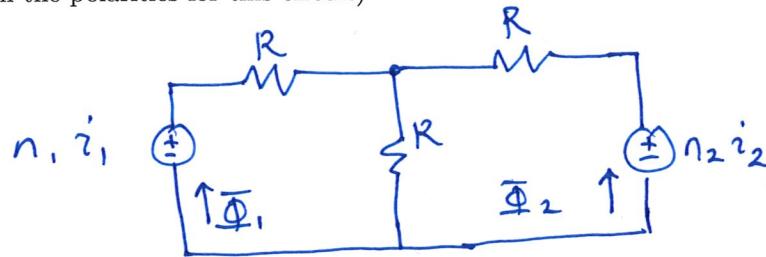- (c) [5 Points] A second winding is added to the same core, as shown in Fig. 2. Modify your magnetic circuit model in part (a) to include this winding. (Hint: Be careful with the polarities for this circuit)



- (d) [15 Points] Determine analytical expressions of  $L_{11}$ ,  $L_{12}$ , and  $L_{22}$  in terms of  $\mathcal{R}$ ,  $n_1$  and  $n_2$ , where

$$\begin{bmatrix} v_1(t) \\ v_2(t) \end{bmatrix} = \begin{bmatrix} L_{11} & L_{12} \\ L_{12} & L_{22} \end{bmatrix} \frac{d}{dt} \begin{bmatrix} i_1(t) \\ i_2(t) \end{bmatrix}.$$

• As done in HW7, apply superposition.

→ First set  $n_2 i_2 = 0$

$$n_1 i_1 = \Phi'_1 (R + \frac{R}{2})$$

$$= \frac{3\Phi'_1}{2} R$$

$$\Rightarrow (\Phi'_1 = \frac{2n_1 i_1}{3R}) \quad (1)$$

and outer KVL loop gives:

$$n_1 i_1 - \Phi'_1 R + \Phi'_2 R = 0$$


$$\Rightarrow \overline{\Phi}'_2 = \frac{1}{R} (\underbrace{\Phi'_1 R - n_1 i_1}_{\text{*sub (1)}})$$

$$= \frac{1}{R} \left( \frac{2n_1 i_1}{3R} R - n_1 i_1 \right) \quad \begin{matrix} \nearrow \\ -1/3 \end{matrix}$$

$$= \frac{1}{R} n_1 i_1 \left( \underbrace{\frac{2}{3} - 1}_{-1/3} \right)$$

$$= \left| \begin{array}{l} \frac{n_1 i_1}{3R} = \overline{\Phi}'_2 \\ \hline \end{array} \right. \quad (2) \quad \left| \begin{array}{c} \vdots \\ \hline \end{array} \right.$$
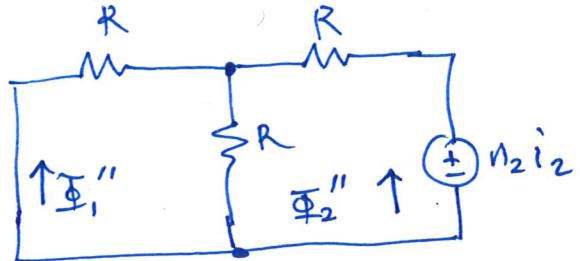
$$\Rightarrow \text{Next set } n_1 i_1 = 0$$



$$n_2 i_2 = \overline{\Phi}''_2 \left( R + \frac{R}{2} \right) = \frac{3R}{2} \overline{\Phi}''_2$$

$$\Rightarrow \left| \begin{array}{l} \overline{\Phi}''_2 = \frac{2n_2 i_2}{3R} \\ \hline \end{array} \right. \quad (3) \quad \left| \begin{array}{c} \vdots \\ \hline \end{array} \right.$$

and outer KVL loop again

$$\begin{aligned}
 0 &= n_2 i_2 - \Phi_2'' R + \Phi_1'' R \\
 \Rightarrow \Phi_1'' &= \frac{\Phi_2'' R - n_2 i_2}{R} \\
 &\quad * \text{sub (3)} \\
 &= \frac{1}{R} \left( \frac{2n_2 i_2}{3R} R - n_2 i_2 \right) \\
 &= \frac{1}{R} n_2 i_2 \left( \frac{2}{3} - 1 \right) \\
 &= \left\{ \frac{-n_2 i_2}{3R} = \Phi_1'' \right\} \quad (4)
 \end{aligned}$$

• Apply Superposition:

$$\left\{
 \begin{array}{l}
 \Phi_1 = \Phi_1' + \Phi_1'' = \frac{2}{3} \frac{n_1 i_1}{R} - \frac{n_2 i_2}{3R} \\
 \Phi_2 = \Phi_2' + \Phi_2'' = -\frac{n_1 i_1}{3R} + \frac{2}{3} \frac{n_2 i_2}{R}
 \end{array}
 \right.$$

Apply Faraday's Law:

$$V_1 = n_1 \frac{d\Phi_1}{dt} = \frac{2n_1^2}{3R} \frac{di_1}{dt} - \frac{n_1 n_2}{3R} \frac{di_2}{dt}$$

$$V_2 = n_2 \frac{d\Phi_2}{dt} = -\frac{n_1 n_2}{3R} \frac{di_1}{dt} + \frac{2n_2^2}{3R} \frac{di_2}{dt}$$

$$\rightarrow \begin{bmatrix} V_1 (+) \\ V_2 (+) \end{bmatrix} = \begin{bmatrix} \frac{2n_1^2}{3R} & -\frac{n_1 n_2}{3R} \\ -\frac{n_1 n_2}{3R} & \frac{2n_2^2}{3R} \end{bmatrix} \frac{d}{dt} \begin{bmatrix} i_1 (+) \\ i_2 (+) \end{bmatrix}$$

**Problem 3: Inductor Design [25 Points Total]** Consider the toroidal core with permeability  $\mu$ , mean path radius  $r$ , air gap  $\ell_g$ , and cross-sectional area  $A_c$ .

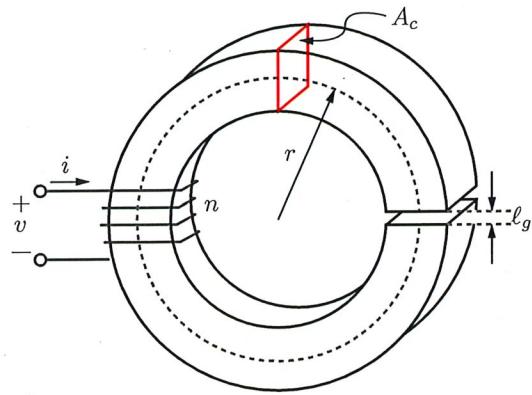


Figure 3: A gapped inductor.

- (a) [5 Points] Draw the magnetic circuit model of this device and derive the total reluctance,  $\mathcal{R}_{\text{net}}$ , around the flux path in terms of  $\mu, \mu_0, r, \ell_g$ , and  $A_c$ .

$$\begin{aligned}
 & \text{Magnetic Circuit Model:} \\
 & \text{Circuit Diagram: } n i \text{ (current source)} - R_c \text{ (core reluctance)} - R_g \text{ (air gap reluctance)} \\
 & \text{Reluctance Sum: } \mathcal{R}_{\text{net}} = R_c + R_g \\
 & = \frac{2\pi r}{\mu A_c} + \frac{\ell_g}{\mu_0 A_c} \\
 & = \frac{2\pi r}{\mu A_c} + \frac{\ell_g}{A_c} \left( \frac{1}{\mu_0} - \frac{1}{\mu} \right) \\
 & = \mathcal{R}_{\text{net}}
 \end{aligned}$$

- (b) [5 Points] Compute an analytical expression for the coil inductance in terms of  $\mu, \mu_0, n, r, l_g$ , and  $A_c$ .

- Ampere's Law gives:

$$ni = \Phi R_{\text{net}}$$

$$\rightarrow \Phi = \frac{ni}{R_{\text{net}}} = \frac{ni}{\frac{2\pi r}{\mu A_c} + \frac{l_g}{A_c} \left( \frac{1}{\mu_0} - \frac{1}{\mu} \right)}$$

- And Faraday says

$$V = n \frac{d\Phi}{dt} = n \frac{d}{dt} \left( \frac{ni}{\frac{2\pi r}{\mu A_c} + \frac{l_g}{A_c} \left( \frac{1}{\mu_0} - \frac{1}{\mu} \right)} \right)$$

$$= \underbrace{\frac{n^2}{\frac{2\pi r}{\mu A_c} + \frac{l_g}{A_c} \left( \frac{1}{\mu_0} - \frac{1}{\mu} \right)}}_{L} \frac{di}{dt}$$

$$\Rightarrow L = \boxed{\frac{n^2 A_c}{\frac{2\pi r}{\mu} + l_g \left( \frac{1}{\mu_0} - \frac{1}{\mu} \right)}}$$

- (c) [5 Points] Suppose you are given a maximum expected current  $I_{\text{sat}}$  and a material with saturation flux density of  $B_{\text{sat}}$ . Compute the air gap,  $\ell_g$ , which gives saturation when  $i \geq I_{\text{sat}}$ . In other words,  $B = B_{\text{sat}}$  when  $i = I_{\text{sat}}$ . Write your expression of  $\ell_g$  in terms of  $I_{\text{sat}}$ ,  $B_{\text{sat}}$ ,  $\mu$ ,  $\mu_0$ ,  $n$ , and  $r$ .

- In general, Ampere's Law says

$$n i = \oint R_{\text{net}}$$

$$\times \oint = BA_c$$

$$= \underbrace{BA_c}_{\oint} \left( \frac{2\pi r}{\mu A_c} + \frac{\ell_g}{A_c} \left( \frac{1}{\mu_0} - \frac{1}{\mu} \right) \right)$$

- Evaluate @  $i = I_{\text{sat}} \neq B = B_{\text{sat}}$

$$n I_{\text{sat}} = B_{\text{sat}} \left( \frac{2\pi r}{\mu} + \ell_g \left( \frac{1}{\mu_0} - \frac{1}{\mu} \right) \right)$$

solve for  $\ell_g$

$$\rightarrow \frac{n I_{\text{sat}}}{B_{\text{sat}}} - \frac{2\pi r}{\mu} = \ell_g \left( \frac{1}{\mu_0} - \frac{1}{\mu} \right)$$

$$\rightarrow \boxed{\ell_g = \frac{1}{\frac{1}{\mu_0} - \frac{1}{\mu}} \left( \frac{n I_{\text{sat}}}{B_{\text{sat}}} - \frac{2\pi r}{\mu} \right)}$$

- (d) [5 Points] Substitute your expression for  $\ell_g$  in part (c) into your inductance expression in part (b). Simplify your inductance expression such that the inductance is written purely in terms of  $n, I_{sat}, B_{sat}$ , and  $A_c$ .

Substitute results

$$L = \frac{n^2 A_c}{\frac{2\pi r}{\mu} + \left( \frac{1}{\left( \frac{1}{\mu_0} - \frac{1}{\mu} \right)} \left( \frac{n I_{sat}}{B_{sat}} - \frac{2\pi r}{\mu} \right) \right) \left( \frac{1}{\mu_0} - \frac{1}{\mu} \right)}$$

~~$\ell_g$~~

$$= \frac{n^2 A_c}{\cancel{\frac{2\pi r}{\mu}} + \frac{n I_{sat}}{B_{sat}} - \cancel{\frac{2\pi r}{\mu}}}$$

$$= \frac{n^2 A_c}{\frac{n I_{sat}}{B_{sat}}} = \boxed{\frac{n^2 A_c B_{sat}}{I_{sat}} = L}$$

(e) [2.5 Points] Fill in the blank: As the maximum expected current  $I_{\text{sat}}$  increases, the necessary air gap  $\ell_g$  increases.

(f) [2.5 Points] Fill in the blank: Suppose you fix the number of turns  $n$  and design the air gap according to your solution in part d. As the saturation field  $B_{\text{sat}}$  increases, the inductance  $L$  increases.

**Problem 4: Discontinuous Conduction Mode [25 Points Total]** Consider the converter in Fig. 4. The input voltage is  $V_g$ , and output voltage is  $V$ . The MOSFET has duty ratio of  $D$  for configuration ①. All losses in the converter can be neglected and the switching frequency is denoted as  $f_s = 1/T_s$ . The inductor current and diode current are denote  $i$  and  $i_d$ .


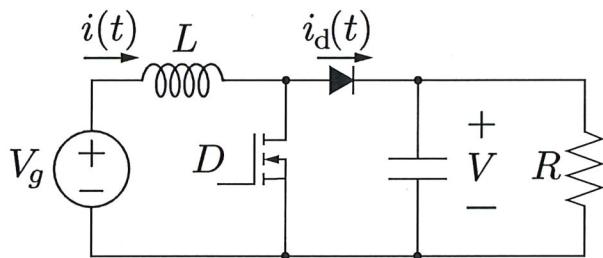


Figure 4: Ideal boost converter for DCM analysis.

- (a) [5 Points] From here forward, consider the converter operating in discontinuous conduction mode (DCM). Draw the 3 possible circuit configurations and specify which devices are conducting. Denote configurations ①, ②, and ③ as having duty ratios  $D$ ,  $D_2$ , and  $D_3$ , respectively.


- Config ①

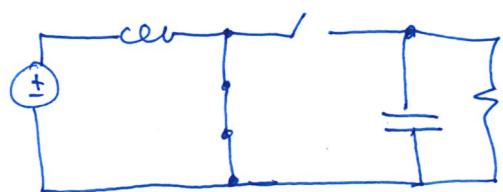

MOSFET conducts

$D T_s$  duration


- Config ②

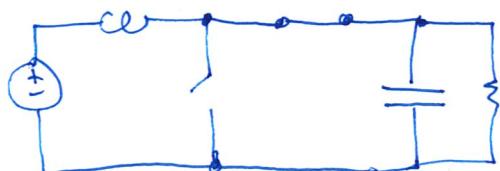

Diode conducts

$D_2 T_s$  duration

- Config ③

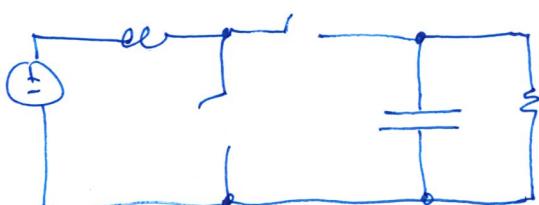

No devices conduct

$D_3 T_s$


- (b) [5 Points] Write down the volt-second balance equation and compute  $D_2$  in terms of  $V$ ,  $V_g$ , and  $D$ .

$$\langle v_L \rangle = 0 = D(V_g) + D_2(V_g - V) + \cancel{D_3(C_o)}$$

$$\Rightarrow D_2 = \frac{-D V_g}{V_g - V}$$

$$= \boxed{\frac{D V_g}{V - V_g} = D_2}$$

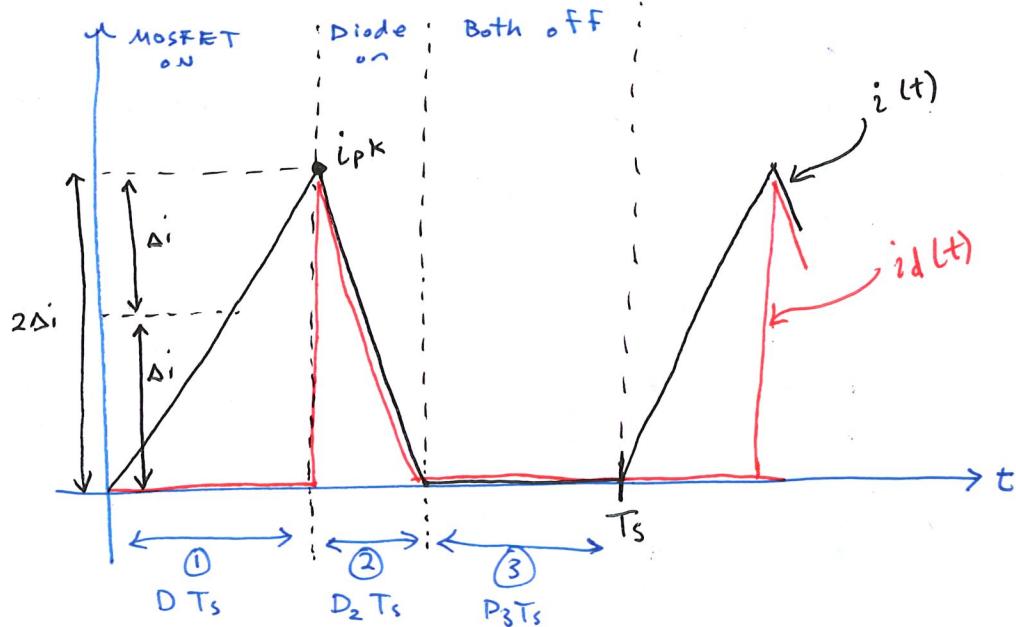- (c) [5 Points] Draw the DCM waveforms for the inductor current,  $i$ , and diode current,  $i_d$ , on the same plot. Clearly label the inductor current peak value as  $i_{pk}$  and label  $\Delta i$  in your plot.



(d) [5 Points] Obtain an expression for the averaged diode current,  $\langle i_d \rangle$  in terms of  $V_g$ ,  $V$ ,  $D$ ,  $T_s$ , and  $L$ . (Hint: First compute  $i_{pk}$  and also apply your result from part (b))

- Look @  $V_L = L \frac{i_{pk}}{DT_s}$  to get  $i_{pk}$

$$\Rightarrow V_g = L \frac{i_{pk}}{DT_s} \Rightarrow i_{pk} = V_g \frac{DT_s}{L} \quad (1)$$

- Take avg of  $i_d$  waveform

$$\langle i_d \rangle = \frac{1}{T_s} \int_0^{T_s} i_d dt = \frac{1}{T_s} \left( \frac{1}{2} i_{pk} D_2 T_s \right)$$

\* use (1)

$$= \frac{1}{2} \underbrace{V_g \frac{DT_s}{L}}_{i_{pk}} D_2$$

\* use result for  $D_2$  in (b)

$$= \frac{1}{2} V_g \frac{DT_s}{L} \underbrace{\frac{D V_g}{(V - V_g)}}_{D_2}$$

$$= \boxed{\frac{T_s}{2L} \frac{D^2 V_g^2}{(V - V_g)} = \langle i_d \rangle}$$

- (e) [5 Points] Compute the charge-balance equation at the capacitor. Apply your result from part (d) solve for  $V/V_g$  in terms of  $D$  and  $K$  where  $K := 2L/(RT_s)$ . You will need so to solve a quadratic expression to obtain your final result.

KCL @ cap node gives

$$i_c = i_d - \frac{v}{R}$$

Average both sides

$$\begin{aligned} \Rightarrow \langle i_c \rangle = 0 &= \langle i_d \rangle - \frac{\langle v \rangle}{R} \\ &= \langle i_d \rangle - \frac{V}{R} \\ &\quad * \text{use (3) from part (d)} \\ &= \frac{T_s}{2L} \frac{D^2 V_g^2}{V - V_g} - \frac{V}{R} = 0 \end{aligned}$$

Multiply by  $R$

$$\rightarrow 0 = \underbrace{\frac{R T_s}{2L}}_{1/K} \frac{D^2 V_g^2}{V - V_g} - V = \frac{D^2}{K} \frac{V_g^2}{(V - V_g)} - V$$

Multiply by  $V - V_2$

$$\rightarrow 0 = \frac{D^2}{K} V_g^2 - V(V - V_2) = \frac{D^2}{K} V_g^2 - V^2 + VV_2 \quad (4)$$

$\div$  by  $-V_g^2$  and rearrange into quadratic form

$$\begin{aligned} \rightarrow 0 &= +\left(\frac{V}{V_g}\right)^2 - \left(\frac{V}{V_2}\right) - \frac{D^2}{K} \\ &= ax^2 + bx + c \quad \text{where} \quad x = \frac{V}{V_g}, \quad a = 1, \quad b = -1, \quad c = -\frac{D^2}{K} \end{aligned}$$

Solve for  $x = V/V_g$  & keep  $\oplus$  solution

$\rightarrow$

$$\begin{aligned} \frac{V}{V_g} &= \frac{-b + \sqrt{b^2 - 4ac}}{2a} = \frac{1 + \sqrt{1 - 4(1)(-\frac{D^2}{K})}}{2} \\ &= \frac{1 + \sqrt{1 + 4D^2/K}}{2} = \frac{V}{V_g} \end{aligned}$$