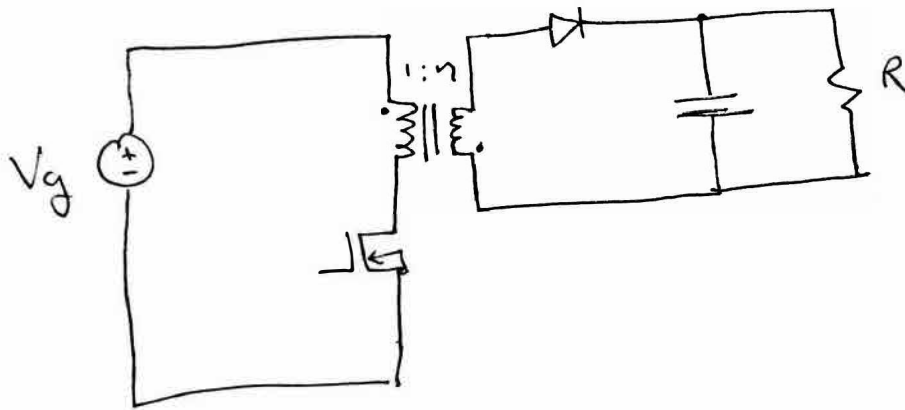


# Homework solution

1

Problem #1 Begin w/ the flyback schematic




Now redraw with  $\rightarrow$  transformer model w/  $R_p$  &  $R_s$

$\rightarrow$  MOSFET lossy model  $\circ - \text{switch} - R_{on} - \circ$

$\rightarrow$  Diode lossy model  $\circ - \text{diode} - V_D - \circ$

we get  $\downarrow$

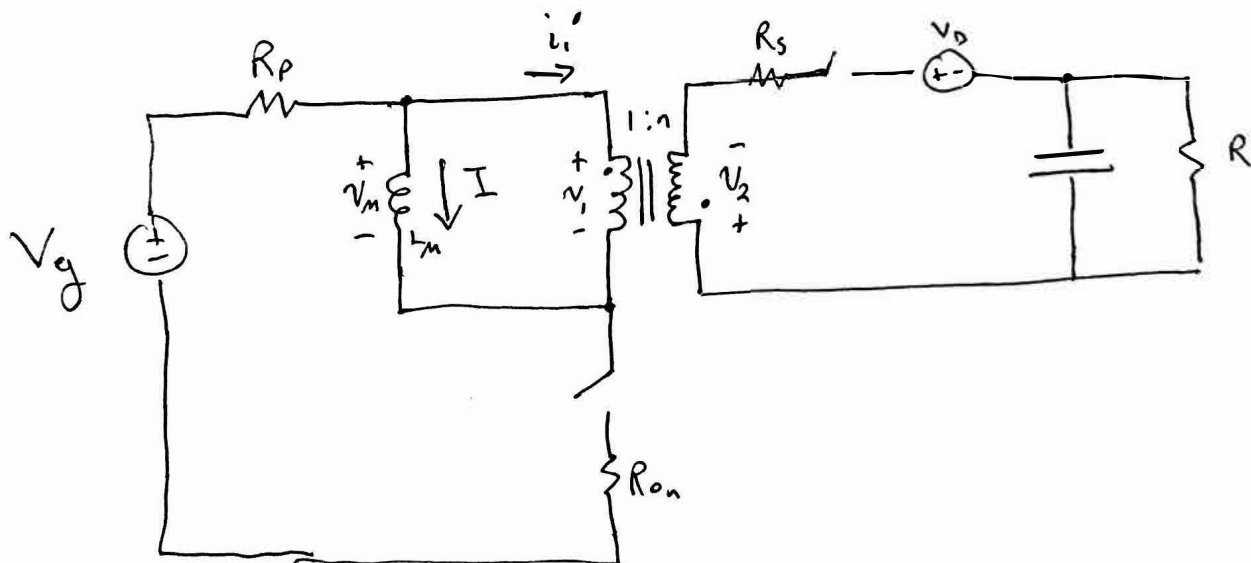


(a) Derive the equiv s-r. ckt:


2

- Following my notes / guidelines we obtain the following circuits for both configurations

— Configuration (1) duration  $DT_s$ :

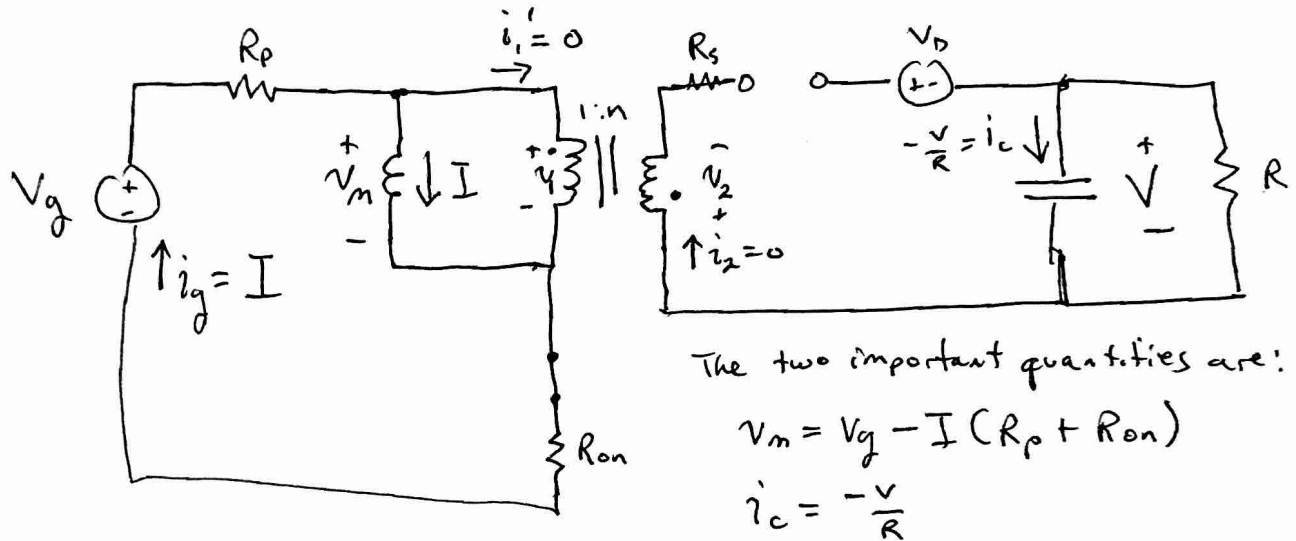

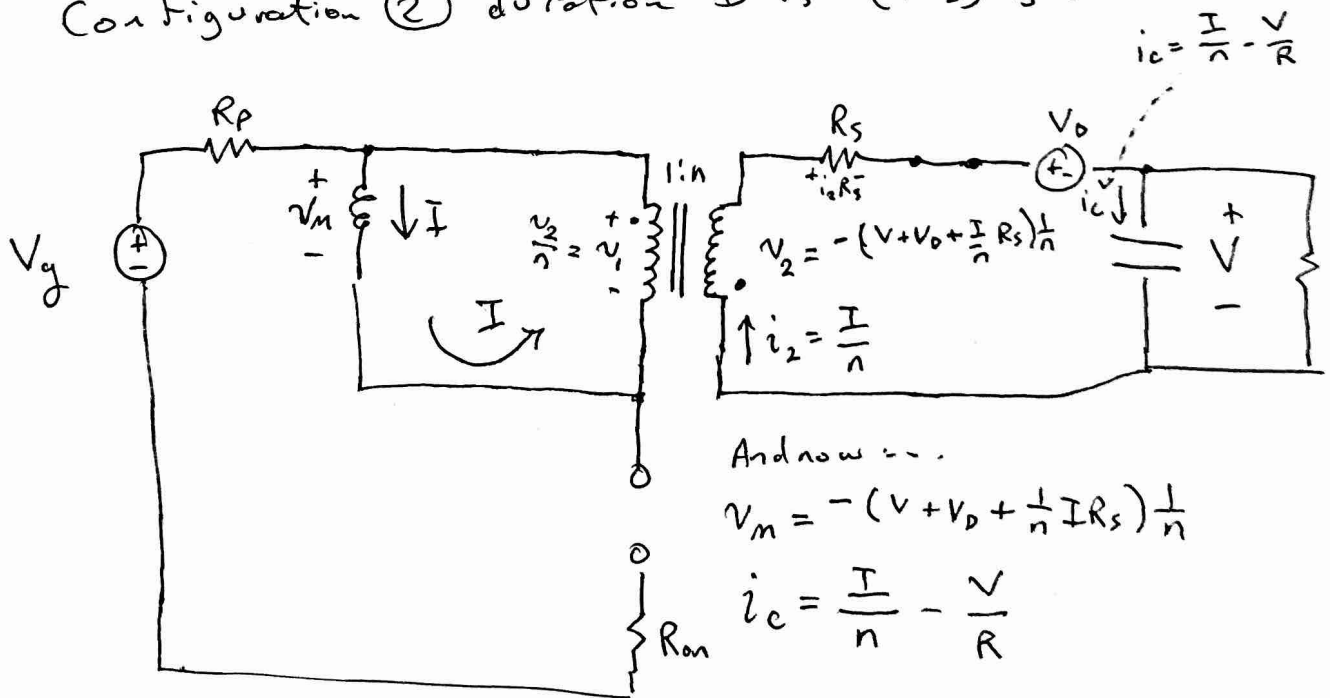— Configuration (2) duration  $D'T_s = (1-D)T_s$ :



• Now apply the balance equations:


3

$$\langle V_m \rangle = 0 = D(V_g - I(R_p + R_{on})) - D'(V + V_b + \frac{1}{n}IR_s) \frac{1}{n} = 0 \quad (1)$$


and

$$\begin{aligned} \langle i_c \rangle = 0 &= D\left(-\frac{V}{R}\right) + D'\left(\frac{I}{n} - \frac{V}{R}\right) \\ &= -\frac{V}{R} + D'\frac{I}{n} = 0 \quad (2) \end{aligned}$$

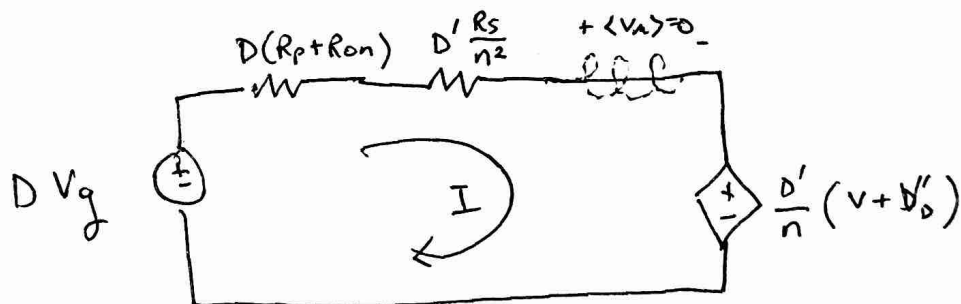
• (1) looks like a KVL loop equation for  $\langle V_m \rangle = 0$



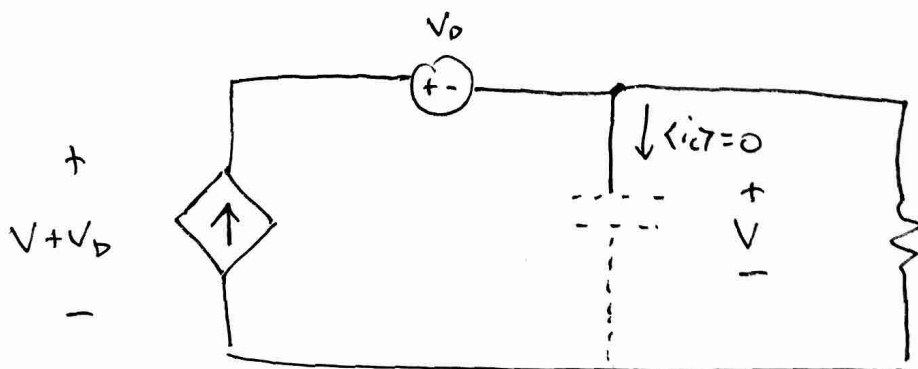• (2) looks like a KCL equation for  $\langle i_c \rangle = 0$




Now combine to get:

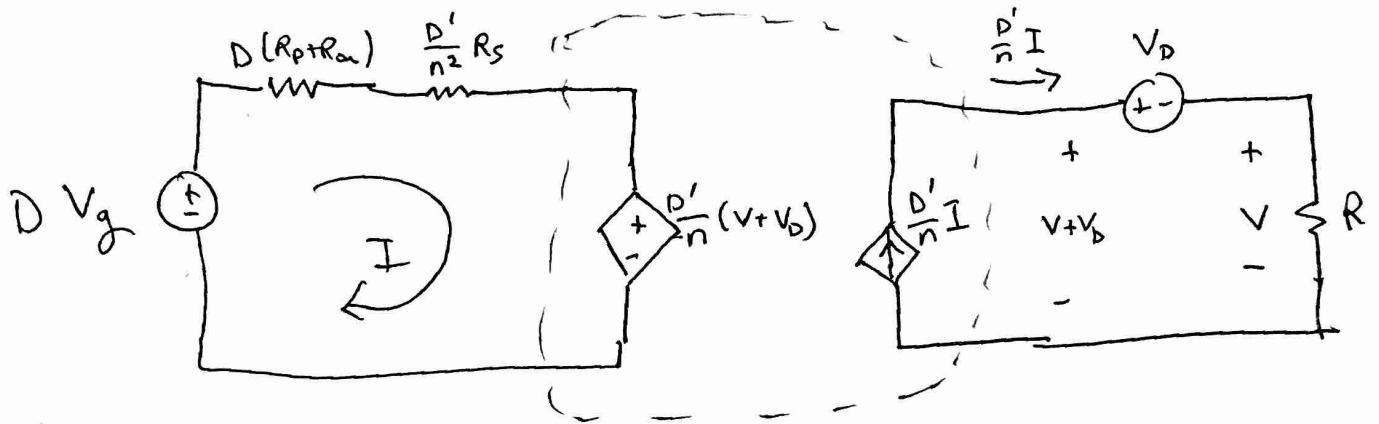

redraw as equiv  
ideal XFmr

1a

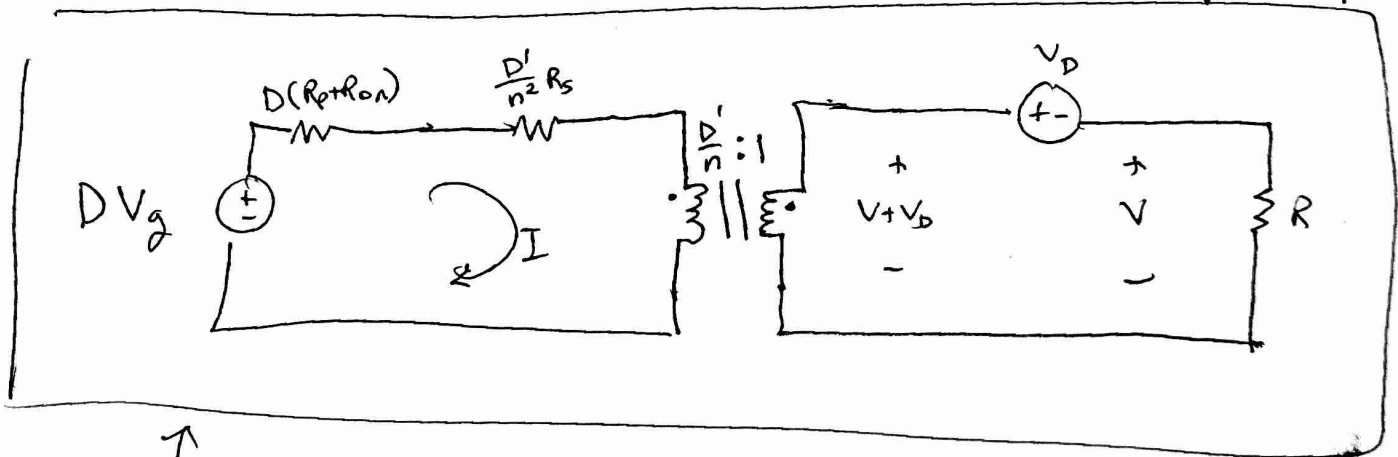

↑ Equiv ckt model in S.S.

b) Compute efficiency  $\eta$  in terms of  $V_g, R_{on}, R_p, R_s, V_D, D, D'$ .

5

- Revisit (1)-(2) balance equations, follow same procedure from past HW assignments  $\rightarrow$  compute/solve for  $I$  first  $\rightarrow$  Eliminate  $I$  &  $V$  from equations

$\rightarrow$  look @  $P_{in}$  &  $P_{out}$ , take ratio, and do algebra.

- Calculate  $I$  from (2)

$$I = \frac{nV}{D'R} \quad (3)$$

- Substitute (3)  $\rightarrow$  (1) & solve for  $V$  since we need to eliminate it.

$$0 = D \left( V_g - \frac{nV}{D'R} (R_p + R_{on}) \right) - \frac{D'}{n} \left( V + V_D + \frac{R_s}{R} \left( \frac{nV}{D'R} \right) \right)$$

$$= DV_g - V \frac{nD}{D'R} (R_p + R_{on}) - \frac{D'}{n} V - \frac{D'}{n} V_D - V R_s \frac{D'}{D'nR}$$

\* collect terms

$$= DV_g - V \left( \frac{nD}{D'R} (R_p + R_{on}) + \frac{D'}{n} + \frac{R_s}{nR} \right) - \frac{D'}{n} V_D = 0 \quad (4)$$

$$\rightarrow V = \frac{DV_g - \frac{D'}{n} V_D}{\frac{nD}{D'R} (R_p + R_{on}) + \frac{D'}{n} + \frac{R_s}{nR}} \quad (5)$$

[6]

- Now look @  $P_{in}$  &  $P_{out}$  avg values  
 \* look @ equiv ckt from pt (a) to see more clearly

$$P_{in} = \underbrace{I}_{\substack{\text{input} \\ i}} \underbrace{DV_g}_{\substack{\text{input} \\ v}} = \underbrace{\frac{nV}{D'R}}_I DV_g = \frac{nDV_g V_g}{D'R}$$

and

$$P_{out} = \frac{V^2}{R}$$

and

$$\eta = \frac{P_{out}}{P_{in}} = \frac{V^2}{R} \frac{D'R}{nDV_g V_g} = \frac{\textcircled{V} D'}{V_g nD}$$

\* plug in (5) for  $V$

$$\left[ \frac{D'}{V_g nD} \frac{DV_g - \frac{D'}{n} V_D}{\frac{nD}{D'R} (R_p + R_{on}) + \frac{D'}{n} + \frac{R_s}{nR}} \right] = \eta$$

This is the solution. With some work, we can probably put it into a more clean/elegant form

\* sanity check

$$\lim_{R_s, R_p, R_{on}, V_D \rightarrow 0} \eta = \frac{D'}{V_g nD} \frac{DV_g - 0}{\cancel{\frac{nD}{D'R}} (0) + \frac{D'}{n} + 0}$$

$$= \frac{\cancel{D'}}{\cancel{V_g nD} \cancel{D'}} \frac{DV_g}{D'} = 1 \quad \checkmark$$

↑ If all lossy elements disappear  $\eta \rightarrow 1$  !