

# EE 452 – Power Electronics Design, Fall 2021

## Homework 5

**Due Date:** Monday November 15th 2021, 11:59 pm Pacific Time

**Instructions.** You must scan your completed homework assignment into a pdf file, and upload your file to the Canvas Assignment page by the due date/time above. All pages must be gathered into a single file of moderate size, with the pages in the correct order. Set your phone or scanner for basic black and white scanning. You should obtain a file size of hundreds of kB, rather than tens of MB. I recommend using the "Tiny Scanner" app. Please note that the grader will not be obligated to grade your assignment if the file is unreadable or very large.

**Problem 1:** The buck-boost converter of Fig. 1 is implemented with a MOSFET and a p-n diode. The MOSFET can be modeled as ideal, but the diode exhibits a substantial reverse-recovery process, with reverse recovery time  $t_r$  and recovered charge  $Q_r$ . In addition, the inductor has winding resistance  $R_L$ . The converter operates in the continuous conduction mode (the small ripple approximation can be used). Derive an equivalent circuit that models the dc components of the converter waveforms and that accounts for the loss elements described above.


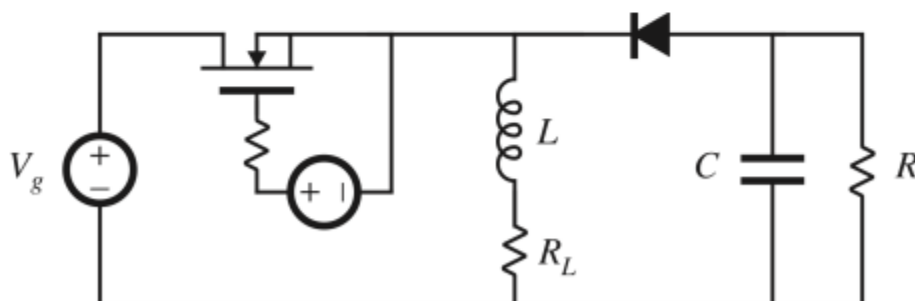


Figure 1: Buck-boost converter of Problem 1.

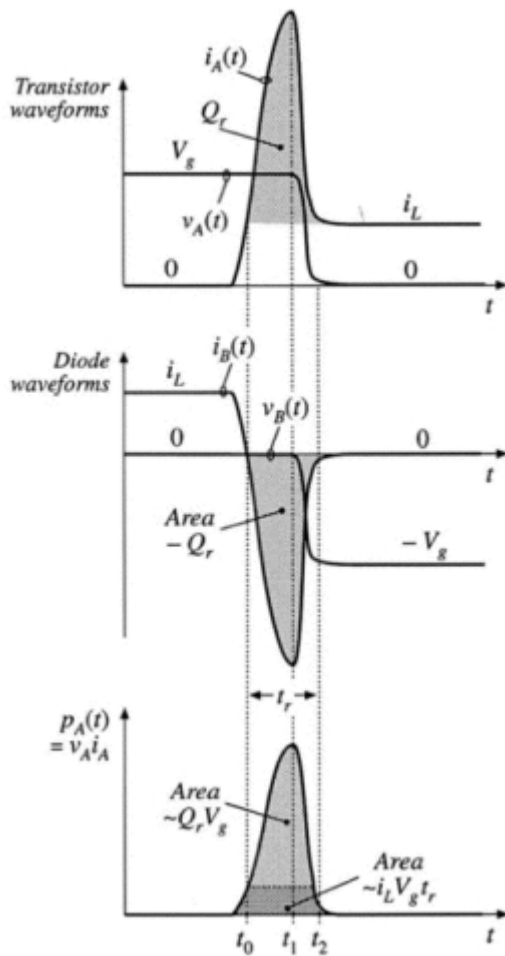

\*This waveform is from a buck. Wanted just for visual

Switch  $[0 < t < DT_s]$

$$0 = V_g - v_L - IR_L$$

$$v_L = V_g - IR_L$$

Switch  $[DT_s < t < T_s]$

$$0 = IR_L + v_L - v$$

$$v_L = v - IR_L$$

Total Volt Seconds over 1 period for Inductor Voltage

$$\int_0^{T_s} v_L(t) dt$$

$$0 = D(V_g - IR_L) + D'(V - IR_L)$$

$$0 = DV_g - IR_L + D'V \quad [\text{Equivalent Voltage Circuit}]$$

Switch  $[0 < t < DT_s]$

$$i_C = -\frac{V}{R}$$

$$i_D = 0$$

---

Switch  $[DT_s < t < T_s]$

$$i_C = -i_D - \frac{V}{R}$$

$$i_D = I_L + \text{Recovery Loss}$$

---

Recovery Loss

$$i_D = -\frac{Q_R}{T_s} - \frac{t_r I_L}{T_s}$$

---

Total Charge Balance over 1 period for Capacitor Current  $I$

$$\int_0^{T_s} i_C(t) dt$$

$$0 = D\left(\frac{-V}{R}\right) + D'(-i_D - \frac{V}{R})$$

$$0 = \frac{-V}{R} - D' i_D$$

$$0 = \frac{-V}{R} - D' I_L - \text{Recovery Loss}$$

$$0 = \frac{-V}{R} - D' I_L - \left(-\frac{Q_R}{T_s} - \frac{t_r I_L}{T_s}\right)$$

$$0 = -D' I_L + \frac{Q_R}{T_s} + \frac{t_r I_L}{T_s} - \frac{V}{R}$$

$$0 = D' I_L - \frac{Q_R}{T_s} - \frac{t_r I_L}{T_s} + \frac{V}{R} \quad [\text{Equivalent Current Circuit}]$$

**Problem 2:** The elements of the buck-boost converter of Fig. 2 are ideal: all losses may be ignored. Your results for parts (a) and (b) should agree with Table 5.2 in the book.

1. Show that the converter operates in discontinuous conduction mode when  $K < K_{\text{crit}}$  and derive expressions for  $K$  and  $K_{\text{crit}}$ .
2. Derive an expression for the dc conversion ratio  $V/V_g$  of the buck-boost converter operating in discontinuous conduction mode.
3. For  $K = 0.1$ , plot  $V/V_g$  over the entire range  $0 \leq D \leq 1$ .
4. ~~Sketch the inductor voltage and current waveforms for  $K = 0.1$  and  $D = 0.3$ . Label salient features.~~
5. ~~What happens to  $V$  at no load ( $R \rightarrow \infty$ )? Explain why, physically.~~

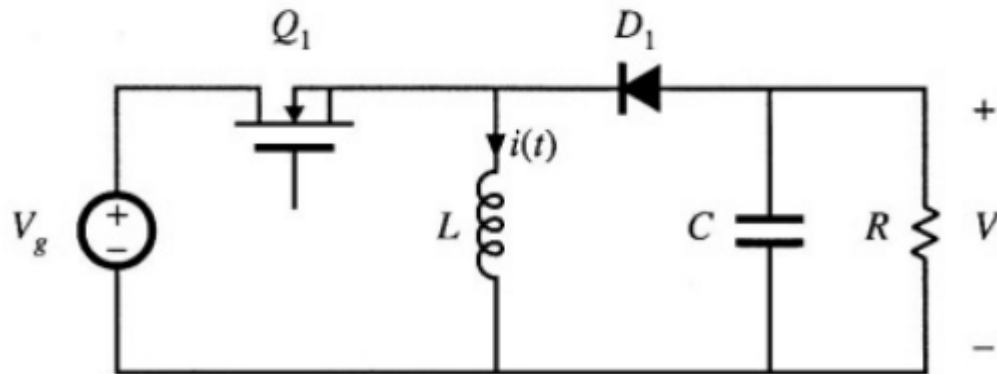


Figure 2: Buck-boost converter of Problem 2.

1.

Switch  $[0 < t < DT_s]$

$$\frac{di_L}{dt} = \frac{V_g}{L} \quad [i_L \text{ slope}]$$

Switch  $[0 < t < DT_s]$

$$i_C = -\frac{V}{R}$$

Switch  $[DT_s < t < T_s]$

$$\frac{di_L}{dt} = \frac{V}{L} \quad [i_L \text{ slope}]$$

Switch  $[DT_s < t < T_s]$

$$i_C = -I - \frac{V}{R}$$

Total Charge Balance over 1 period for Capacitor Current  $I$

$$I = V_g \frac{D}{D' D' R} \quad [\text{Inductor Current } I]$$

### Ripple

$$2\Delta i = (i_L \text{ slope}) \cdot DT_s$$

$$\Delta i = \frac{V_g}{2L} \cdot DT_s$$

### DCM

$$I_L < \Delta i$$

$$V_g \frac{D}{D' D' R} < \frac{V_g}{2L} \cdot DT_s$$

$$\frac{1}{D' D' R} < \frac{1}{2L} \cdot T_s$$

$$\frac{2L}{RT_s} < D' D'$$

$$K = \frac{2L}{RT_s}$$

$$K_{crit} = D' D'$$

2. Switch  $[0 < t < D_1 T_s]$

$$0 = V_g - v_L$$

$$v_L = V_g$$


---

Switch  $[D_1 T_s < t < (D_1 + D_2) T_s]$

$$0 = v_L - v$$

$$v_L = v$$


---

Switch  $[(D_1 + D_2) T_s < t < T_s]$

$$v_L = 0$$


---

Total Volt Seconds over 1 period for Inductor Voltage

$$\langle v_L \rangle = \int_0^{T_s} v_L(t) dt$$

$$0 = D_1(V_g) + D_2(V) + D_3(0)$$

$$V = \frac{-D_1 V_g}{D_2} \quad [\text{Output Voltage}]$$


---

Solve in terms of  $D_1$

$$V = \frac{-D_1 V_g}{D_2}$$

$$D_2 = \frac{-D_1 V_g}{V}$$


---

Thus

$$\langle i_D \rangle = \frac{V_g}{2L} D_1 D_2 T_s$$

$$\frac{V}{R} = \frac{V_g}{2L} D_1 \left( \frac{-D_1 V_g}{V} \right) T_s$$

$$\left[ \frac{V}{R} \right] \cdot \frac{2L \cdot V}{T_s} = \left[ -\frac{D_1^2 V_g^2}{2L \cdot V} T_s \right] \frac{2L \cdot V}{T_s}$$

$$V^2 \frac{2L}{RT_s} = -D_1^2 V_g^2$$

$$V^2 K = -D_1^2 V_g^2$$

$$\frac{V^2}{V_g^2} = -\frac{D_1^2}{K}$$

$$\frac{V}{V_g} = -\frac{D_1}{\sqrt{K}}$$

$$\frac{V}{V_g} = -D_1 \cdot \sqrt{\frac{RT_s}{2L}}$$

**Capacitor Charge Balance**

$$i_D = i_C + \frac{v}{R} \Big|_{i_C=0}$$

$$i_D = \frac{V}{R}$$


---

Peak Current:

$$i_D(D_1 T_s) = i_{pk} = \frac{V_g}{L} D_1 T_s$$


---

Average Current:

$$\begin{aligned} \langle i_D \rangle &= \frac{1}{T_s} \int_0^{T_s} i_D(t) dt \\ &= \frac{1}{T_s} \cdot \frac{1}{2} i_{pk} D_2 T_s \\ &= \frac{1}{T_s} \frac{1}{2} \left( \frac{V_g}{L} D_1 T_s \right) D_2 T_s \\ &= \frac{V_g}{2L} D_1 D_2 T_s \end{aligned}$$

3.

