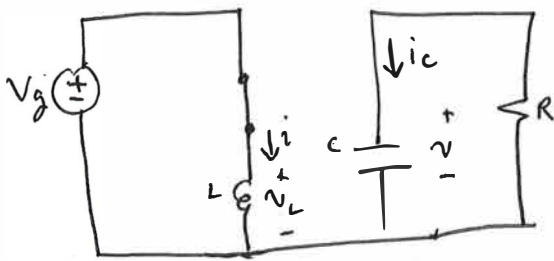
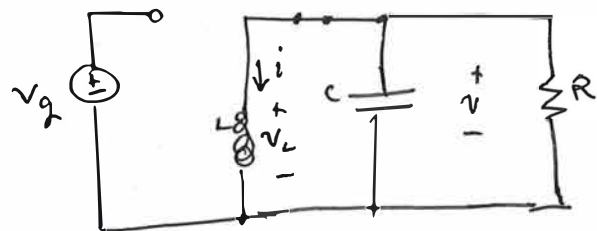


## HW # 1 solution

Problem # 11(a) Express  $V$  and  $I$  in terms of  $D, V_g, \& R$ Position ① Duration  $DT$ Position ② Duration  $D'T = (1-D)T$ 

volt second balance

$$\langle v_L \rangle = D V_g + \overbrace{(1-D)}^{D'} V = 0 \quad (1)$$

charge balance

$$\langle i_c \rangle = \left(-\frac{V}{R}\right) D + \left(-I - \frac{V}{R}\right) (1-D) = 0 \quad (2)$$

Rearrange (1)

$$\boxed{V = -V_g \frac{D}{1-D}} \quad (1a) \quad (3)$$

Rearrange (2)


$$-\frac{V}{R} D = (1-D) \left(I + \frac{V}{R}\right) \Rightarrow I = -\frac{V}{R} \frac{D}{1-D} - \frac{V}{R} \quad (4)$$

\* use (3) in (4)

$$\Rightarrow I = -\frac{V}{R} \left(\frac{D}{1-D} + 1\right) = \boxed{\frac{V_g}{R} \frac{D}{1-D} \left(\frac{D}{1-D} + 1\right) = I} \quad (1a) \quad (5)$$

(2)

1 (b) Plot  $V$  &  $I$  versus  $D$

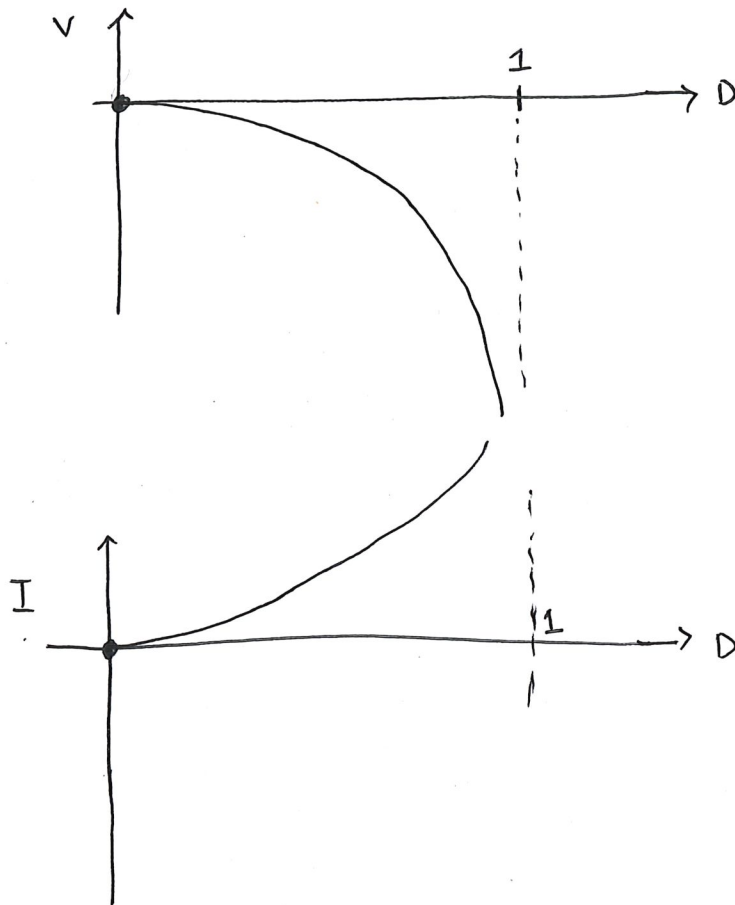

only shape  
≠ ~~data~~ zero values  
@  $D=0$  matter.

1 c) Design problem:

(1) Find  $D$  &  $I$

Rearrange (1)

$$0 = DV_g - DV + V$$

$$= D(V_g - V) + V$$

$$\Rightarrow D = \frac{-V}{V_g - V}$$

$$= \frac{V}{V - V_g}$$

$$= \frac{(-12V)}{(-12V) - 15V}$$

$$= \frac{12}{27} = \frac{4.3}{9.3}$$

$$= \frac{4}{9} \approx 0.44 \approx D \quad \text{1 c) ci)}$$

and (5) g.v.s.

$$I = \frac{15V}{4\Omega} \frac{\frac{4}{9}}{1 - \frac{4}{9}} \left( \frac{\frac{4}{9}}{1 - \frac{4}{9}} + 1 \right) \approx 5.4A \quad \text{1 c) (i)}$$

- (ii) for IC

• Find  $L$  s.t.  $\Delta i = 0.1 I$

• for position ① we get

$$L \frac{2\Delta i}{DT} = V_g \Rightarrow L = \frac{DTV_g}{2\Delta i}$$

\* where  $\Delta i = 0.1 I$  &  $I$  comes from before

$\Rightarrow$

$$L = \frac{DTV_g}{2 \times 0.1 \times I}$$

$$\begin{aligned} &= \frac{DTV_g}{2 \times 0.1 I f_s} \approx 30.9 \mu H \\ &= L \end{aligned}$$

- (iii) Find  $C$  s.t.  $\Delta v = 0.1 V$

• For position ①

$$C \frac{2\Delta v}{DT} = \frac{|V|}{R}$$


$$\rightarrow C = \frac{DT|V|}{2R\Delta v}$$

$$\begin{aligned} &= \frac{D|V|}{2R \times 0.1 V} \approx 33.3 \mu F \\ &= C \end{aligned}$$

(ii)  
1c) (iii)


(5)

1 (cd)

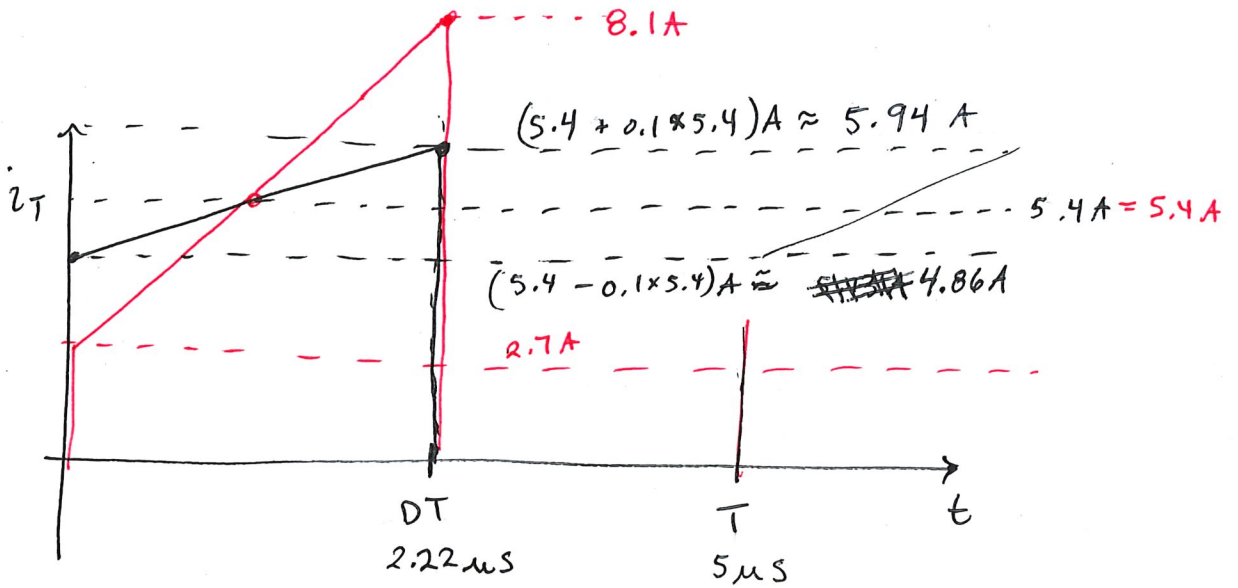

— case for  $\Delta i = 0.1 I$   
 — case for  $\Delta i = 0.5 I$

1 (e)

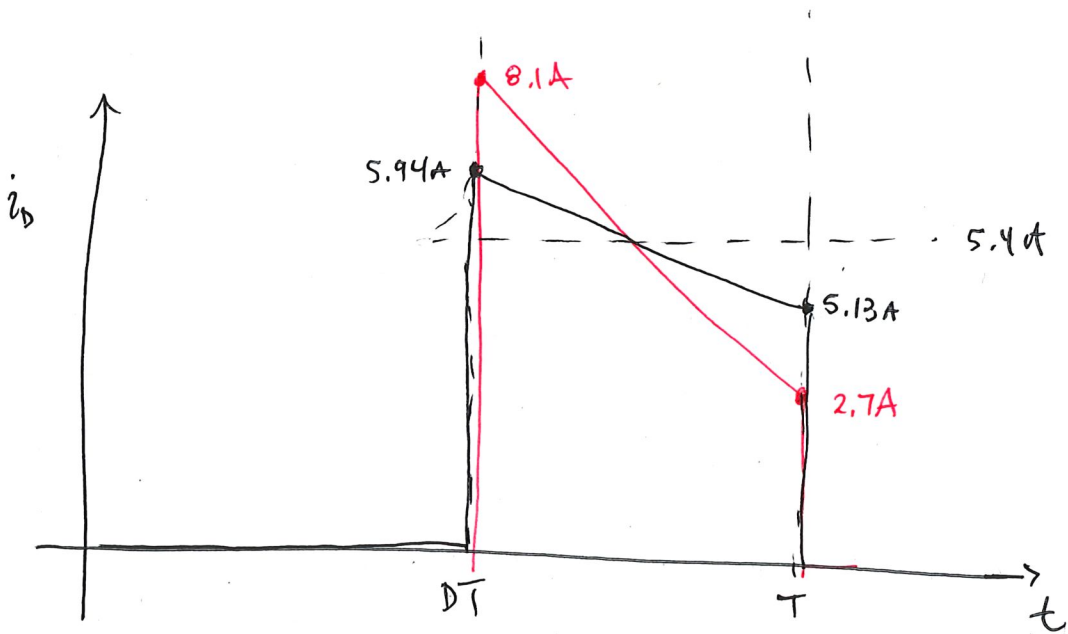

## Problem #2

2(a) Volt second balance gives

$$\langle v_L \rangle = V_g D + (V_g - V)(1-D) = 0$$


$$\rightarrow \cancel{V_g D} + V_g - \cancel{V_g D} - V(1-D) = 0$$

$$\rightarrow \frac{V_g}{V} = 1-D$$

$$\rightarrow D = 1 - \frac{V_g}{V}$$

$$\boxed{\begin{aligned} &= 1 - \frac{3.3V}{5V} = D \\ &\approx 0.34 \end{aligned}} \quad \boxed{2(a)}$$

2(b)  $V_{DS}$  looks like

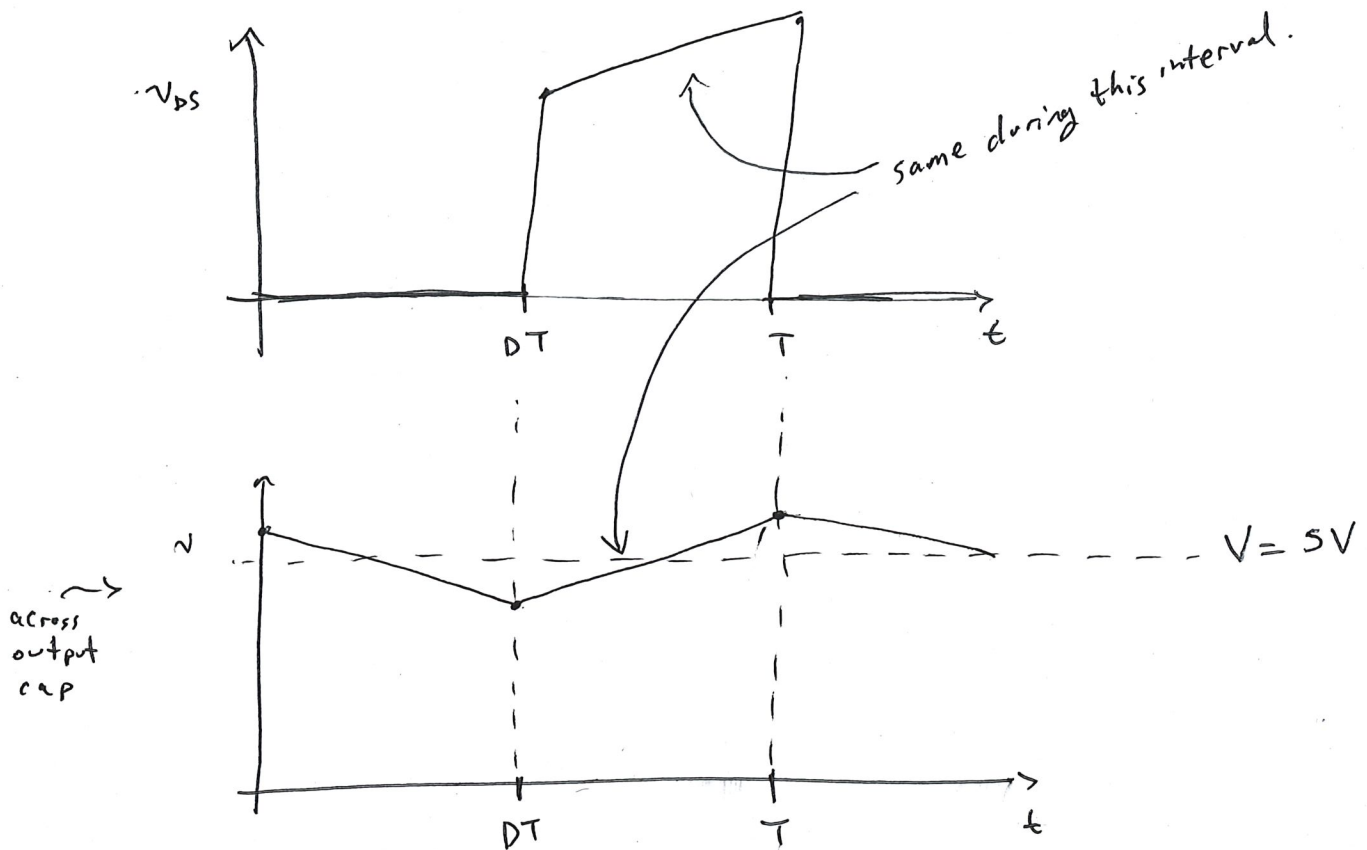

2(c) DC component of  $V_{DS}$  is same as average  $V_{DS}$  over 1 cycle

$$\langle V_{DS} \rangle = \frac{1}{T} \int_0^T V_{DS}(\tau) d\tau = \frac{1}{T} \left( \int_0^{DT} 0 d\tau + \int_{DT}^T V(\tau) d\tau \right)$$

$\nwarrow$  output cap voltage  
 Same as area of square equal to  $V(1-D)T$

$$= \frac{1}{T} V(1-D)T$$

$$= V(1-D) = \langle V_{DS} \rangle \quad \text{2(c)}$$

$$\approx 5V(1-0.34) = 3.3V$$