


Homework #3 Solutions

Problem #1

A Redraw w/ SPST's & define polarities of voltages & currents.

"Small ripple approximation" (SRA) applied here

called a
"Watkins-Johnson"
converter

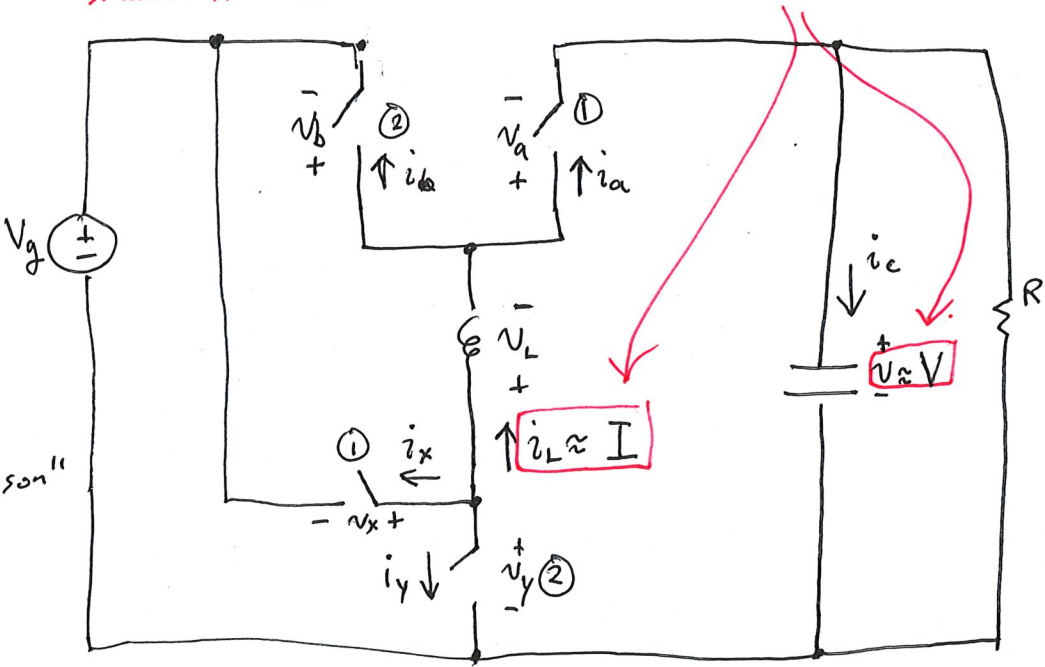

B Express ~~polarities~~ of $v_a, v_b, v_x, v_y, i_a, i_b, i_x, i_y$ in terms of V_g, I, V .

off state sw voltages

$$v_a = V_g - V$$

$$v_b = V_g - V$$

$$v_x = V_g$$

$$v_y = V_g$$

on-state sw currents

$$i_a = I$$

$$i_b = I$$

$$i_x = -I$$

$$i_y = -I$$

- C** • Solve ckt using Ch 2 approach. I suggest you draw ckt for configurations ① & ②, then use KVL to find V_L & KCL to find i_c in both settings.


- Apply volt-second & charge balance equations:

$$\begin{aligned} \langle V_L \rangle = 0 &= \overbrace{D(V_g - V)}^{\text{KVL in } ①} + \overbrace{(1-D)(-V_g)}^{\text{KVL in } ②} \\ &= V_g(2D-1) - DV \quad (1) \end{aligned}$$


$$\begin{aligned} \langle i_c \rangle = 0 &= \overbrace{D\left(I - \frac{V}{R}\right)}^{\text{KCL in } ①} + \overbrace{(1-D)\left(-\frac{V}{R}\right)}^{\text{KCL in } ②} \\ &= -\frac{V}{R} + DI \quad (2) \end{aligned}$$

①

- circuit in config ①

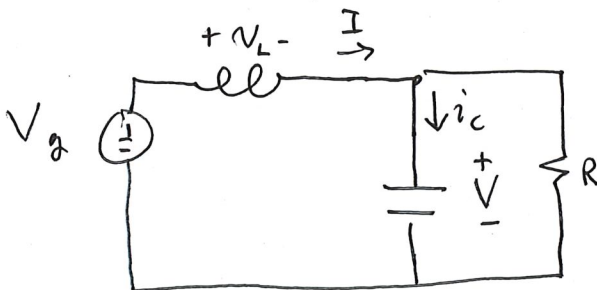

- circuit in config ②

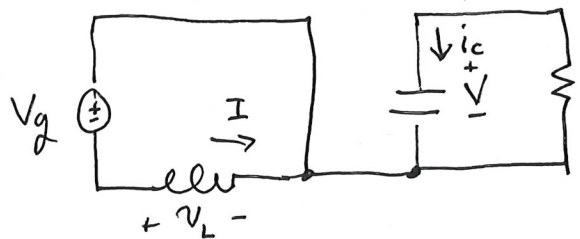

- (1)-(2) are 2 equations with 2 unknowns (V, I). Solve for V, I :

- Get V from (1)

$$V = V_g \frac{2D-1}{D} \quad (3)$$

- (3) \rightarrow (2) to get I

$$I = \frac{V}{DR} = \frac{V_g}{R} \frac{(2D-1)}{D^2} = I \quad (4)$$

C

10 Determine polarities of off sw voltages & on currents using solutions from [c].

→ sw a

sw a

$$\begin{aligned}
 V_a &= V_g - V = V_g - V_g \left(\frac{2D-1}{D} \right) \\
 &= V_g \left(1 - \frac{2D-1}{D} \right) = V_g \left(\frac{D-2D+1}{D} \right) \\
 &= V_g \left(\frac{1-D}{D} \right) \Rightarrow \boxed{V_a \text{ can be } \oplus \text{ only}}
 \end{aligned}$$

$\underbrace{V_g}_{\oplus \text{ only}} \underbrace{\left(\frac{1-D}{D} \right)}_{\oplus \text{ only for } 0 < D < 1}$

product of two \oplus #'s is also positive

sw a

$$i_a = I = \frac{V_g}{R} \frac{1}{D^2} (2D-1) \Rightarrow \boxed{i_a \text{ can be } \oplus \text{ or } \ominus, \text{ depending on } D}$$

$\underbrace{\frac{V_g}{R}}_{\oplus} \underbrace{\frac{1}{D^2}}_{\oplus} \underbrace{(2D-1)}_{\begin{matrix} \oplus \text{ for } D > 1/2 \\ \ominus \text{ for } 0 < D < 1/2 \end{matrix}}$

$\oplus \times \oplus \times (\oplus \text{ or } \ominus)$

$\rightarrow i_a \oplus \text{ for } D > 1/2$
 $i_a \ominus \text{ for } 0 < D < 1/2$

→ sw b is same as sw a

sw b

$$\Rightarrow \boxed{V_b \oplus \text{ only}}, \boxed{i_b \oplus \text{ or } \ominus}$$

- sw x

$$\begin{aligned}
 V_x &= V_g \Rightarrow \boxed{V_x \oplus \text{ only}} \\
 i_x &= -I \\
 &= -\frac{V_g}{R} \frac{1}{D^2} (2D-1) \Rightarrow \boxed{i_x \oplus \text{ or } \ominus}
 \end{aligned}$$

sw x


- sw y same as sw x

sw y

$$\Rightarrow \boxed{V_y \oplus \text{ only}}, \boxed{i_y \oplus \text{ or } \ominus}$$

look @ quadrants


sw a & sw b

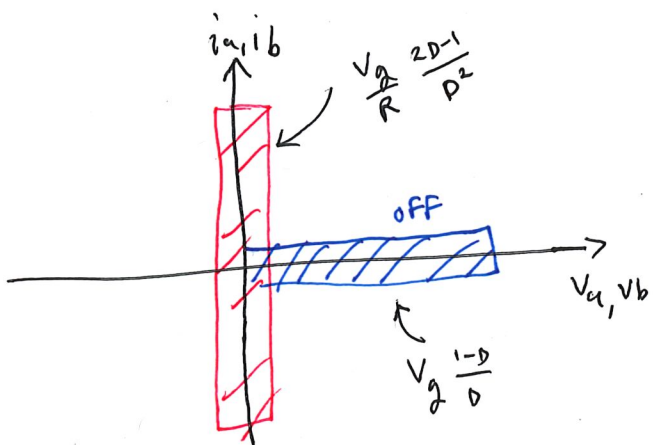

Two quadrant, current bidirectional

sw a & b are MOSFETs

sw x & sw y


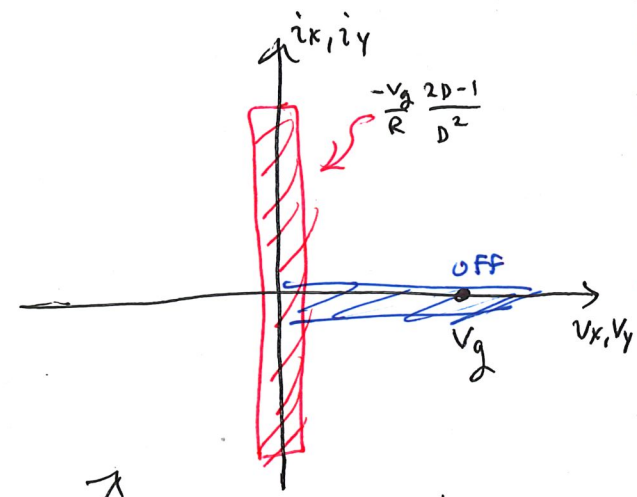


Two quadrant, current bidirectional

sw x, sw y also MOSFETs


Realization:

MOSFET =
sign convention

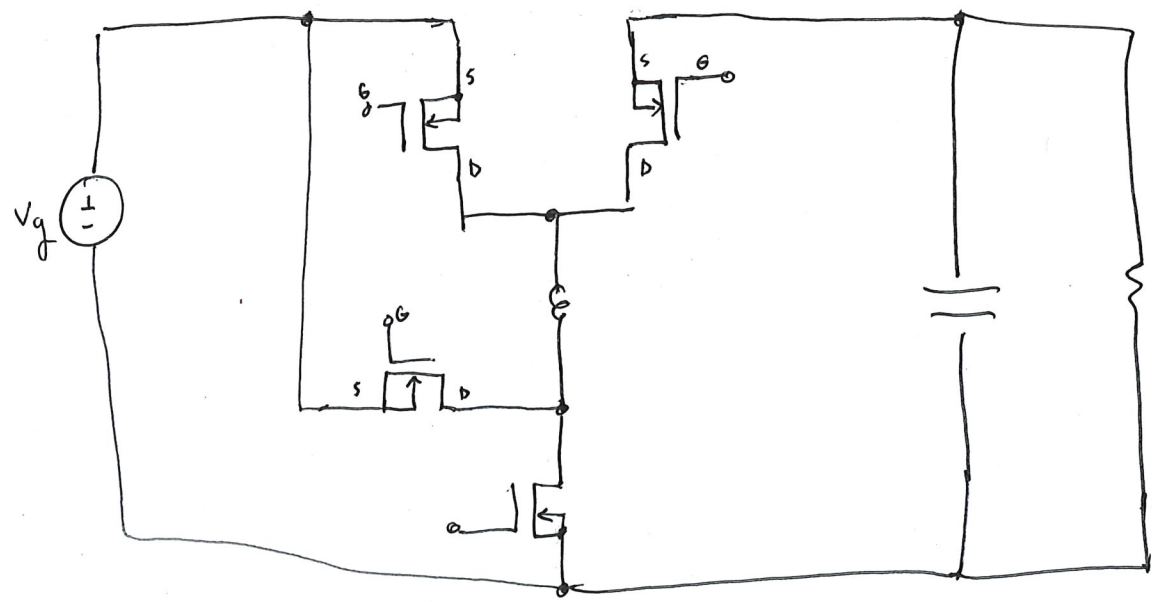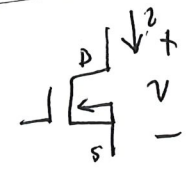

Problem #2

[A]

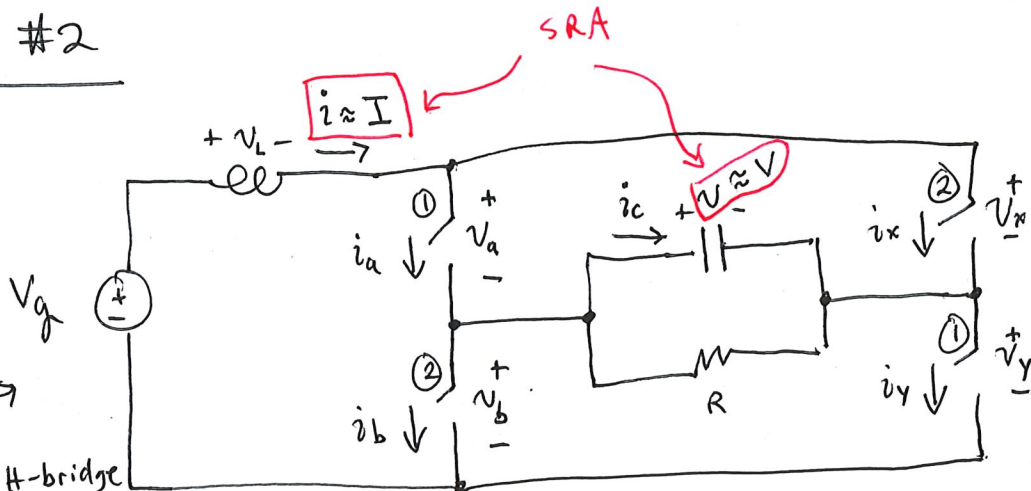

called a
"current source H-bridge
Inverter"

[B] Write sw v 's & i 's in terms of V_g, I, V .

off state sw voltages

$$v_a = -V$$

$$v_b = +V$$

$$v_x = +V$$

$$v_y = -V$$

on state sw currents

$$i_a = I$$

$$i_b = I$$

$$i_x = I$$

$$i_y = I$$

[C] Apply voltsecond & charge balance ... similar to ~~HW2~~ HW2 problem #1.

$$\begin{aligned} \langle v_L \rangle = 0 &= D(V_g - V) + (1-D)(V_g + V) \\ &= V_g + V(1-2D) \end{aligned} \quad (1)$$

$$\begin{aligned} \langle i_c \rangle = 0 &= D\left(I - \frac{V}{R}\right) + (1-D)\left(-I - \frac{V}{R}\right) \\ &= -\frac{V}{R} + I(2D-1) \end{aligned} \quad (2)$$

• solve for V, I .

• Rearrange (2)

$$\rightarrow I = \frac{V}{R} \frac{1}{2D-1} \quad (3)$$

• Put (3) \rightarrow (1) to get

$$V = \frac{-V_g}{1-2D} = \boxed{V_g \frac{1}{2D-1} = V} \quad (4)$$

• (4) \rightarrow (3) g.ves

$$\boxed{I = \frac{V_g}{R} \frac{1}{(2D-1)^2}} \quad (5)$$

C

D: Look at sw v's & i's in **B** using solution in **C**

sw a $\left\{ \begin{aligned} v_a = -V &= -V_g \frac{1}{2D-1} \Rightarrow v_a \text{ can be } \oplus \text{ or } \ominus \\ &\quad \underbrace{\oplus \ominus}_{\substack{\oplus \text{ for } D > 1/2 \\ \ominus \text{ for } 0 < D < 1/2}} \end{aligned} \right.$

$i_a = I = \frac{V_g}{R} \frac{1}{(2D-1)^2} \Rightarrow i_a \oplus \text{ only}$
 $\underbrace{\oplus}_{\substack{\oplus \text{ only b/c} \\ \text{denominator} \\ \text{is squared}}}$

sw Y $\left\{ \begin{aligned} &\bullet \text{ sw Y is same} \\ &\quad \text{as sw a} \end{aligned} \right.$




$v_y \oplus \text{ or } \ominus$
 $i_y \oplus \text{ only}$

sw b


$$\begin{aligned}
 & \left\{ \begin{aligned} v_b &= +V = \underbrace{V_g}_{\oplus} \underbrace{\frac{1}{2D-1}}_{\oplus \text{ or } \ominus} \Rightarrow v_b \oplus \text{ or } \ominus \\ i_b &= \text{same} \dots \Rightarrow i_a \oplus \text{ only} \end{aligned} \right.
 \end{aligned}$$

all switches experience same polarities

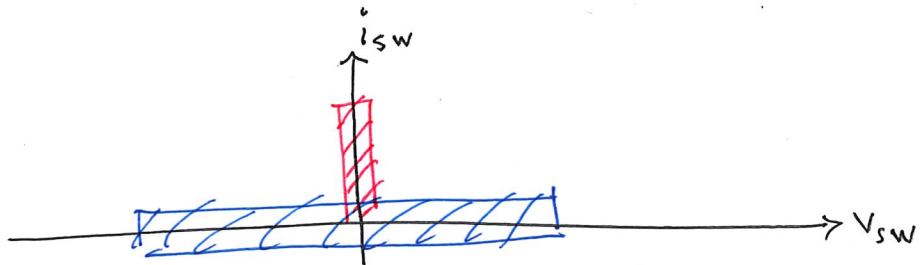


2 quadrant, voltage bidirectional

all are series diode & IGBT (or MOSFET)

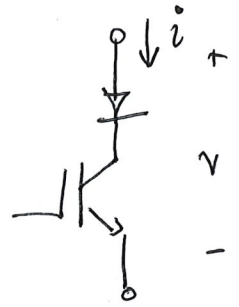


Realization:

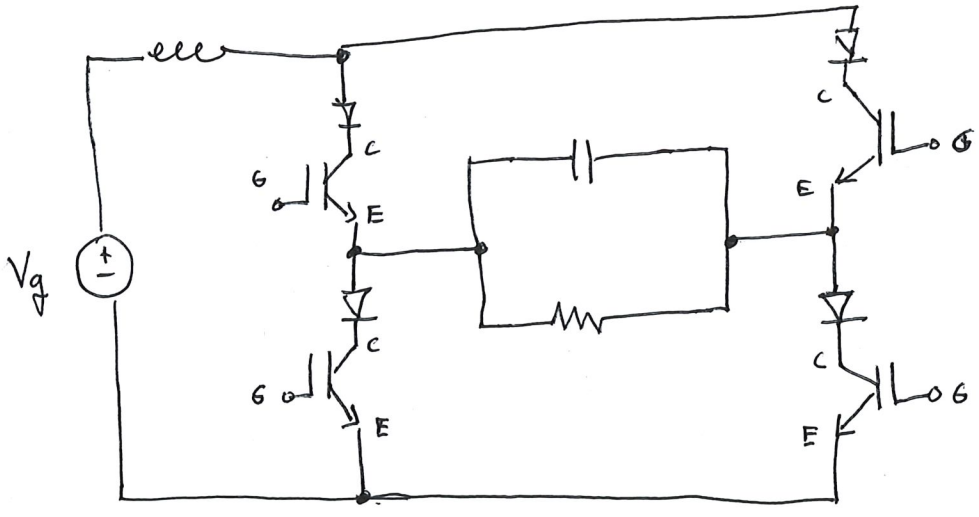

Problem #3

[A] already done in prompt... just need to define v 's & i 's in circuit & switches.

Use "SRA"

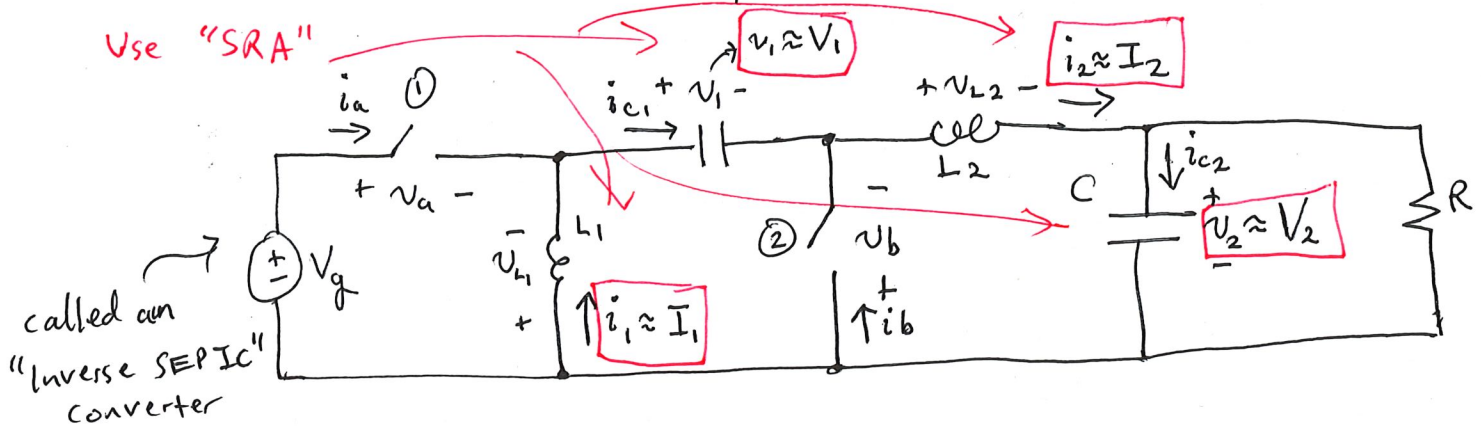

[B] Express v_a, i_a, v_b, i_b in terms of I_1, I_2, V_1, V_2

off-state sw voltages

$$v_a = V_g - V_1$$

$$v_b = -(V_g - V_1) = V_1 - V_g$$

on-state sw currents

$$i_a = I_2 - I_1$$

$$i_b = I_2 - I_1$$

[C] Solve for I_1, I_2, V_1, V_2

$$\begin{aligned} \langle v_{L1} \rangle &= 0 = D \underbrace{(-V_g)}_{* \text{ KVL } ①} + (1-D) \underbrace{(-V_1)}_{* \text{ KVL } ②} \\ &= -D V_g - V_1 D' \quad \text{let } D' = 1-D \end{aligned} \quad (1)$$

$$\begin{aligned} \langle v_{L2} \rangle &= 0 = D \underbrace{(V_g - V_1 - V_2)}_{* \text{ KVL } ①} + (1-D) \underbrace{(-V_2)}_{* \text{ KVL } ②} \\ &= D(V_g - V_1) - V_2 \end{aligned} \quad (2)$$

$$\langle i_{C1} \rangle = 0 = D \underbrace{(I_2)}_{* \text{ KCL } ①} + (1-D) \underbrace{(I_1)}_{* \text{ KCL } ②} \quad (3)$$

$$\langle i_{C2} \rangle = 0 = I_2 - \frac{V_2}{R} \quad (4)$$

* KCL same for ① & ②

Helpful Note: To get quantities marked with (*), redraw ckt for both switch configurations. Then carefully look @ KVL & KCL for configurations ① & ②. I skipped this step since I am more experienced. I suggest you not skip this step.

We now have 4 equations (1)-(4) & 4 unknowns (I_1, I_2, V_1, V_2). Next solve system of equations w/ algebra

(1) gives

$$\boxed{V_1 = -\frac{D}{D'} V_g} \quad \checkmark \quad (5)$$

(5) \rightarrow (2) gives

*from (2) directly substitute (5)

$$V_2 = D(V_g - \overset{\nwarrow}{V_1})$$

$$= D(V_g + \frac{D}{D'} V_g)$$

$$= DV_g(1 + \frac{D}{D'}) = DV_g(\frac{D' + D}{D'})$$

$$= \boxed{\frac{D}{D'} V_g = V_2} \quad \checkmark \quad (6)$$

Rearrange (4) then substitute (6)

$$I_2 = \frac{V_2}{R} = \boxed{\frac{DV_g}{D'R}} = I_2 \quad \checkmark \quad (7)$$

Rearrange (3) then substitute (7)

$$I_1 = -\frac{D}{D'} I_2 = \boxed{-\frac{D^2}{D'^2} \frac{V_g}{R}} = I_1 \quad \checkmark \quad (8)$$

c

D Look @ polarities for v_a, i_a, v_b, i_b .

Re-examine sw v's & currents we started with and substitute solutions in (5)-(8).

{ sw
a

- $$v_a = V_g - V_1 = V_g + \frac{D}{D'} V_g$$

$$= V_g \left(1 + \frac{D}{D'}\right) = V_g \left(\frac{D' + D}{D'}\right)$$

$$= \frac{V_g}{D'} \rightarrow \boxed{v_a \oplus \text{ only}}$$

since $V_g \neq D'$ both \oplus only

{ sw
b

- $$i_a = I_2 - I_1 = I_2 + \frac{D}{D'} I_2$$

$$= I_2 \left(1 + \frac{D}{D'}\right) = \frac{I_2}{D'}$$

$$= \frac{D}{D'^2} \frac{V_g}{R} \rightarrow \boxed{i_a \oplus \text{ only}}$$


since V_g, R, D, D' all \oplus only
- $$v_b = V_1 - V_g = -v_a = -\frac{V_g}{D'} \rightarrow \boxed{v_b \ominus \text{ only}}$$
- $$i_b = \dots \text{ same as } i_a = \frac{D}{D'^2} \frac{V_g}{R} \rightarrow \boxed{i_b \oplus \text{ only}}$$

$1 - \cancel{D'} + \cancel{D}$

D

[E]

look @ quadrants & pick devices

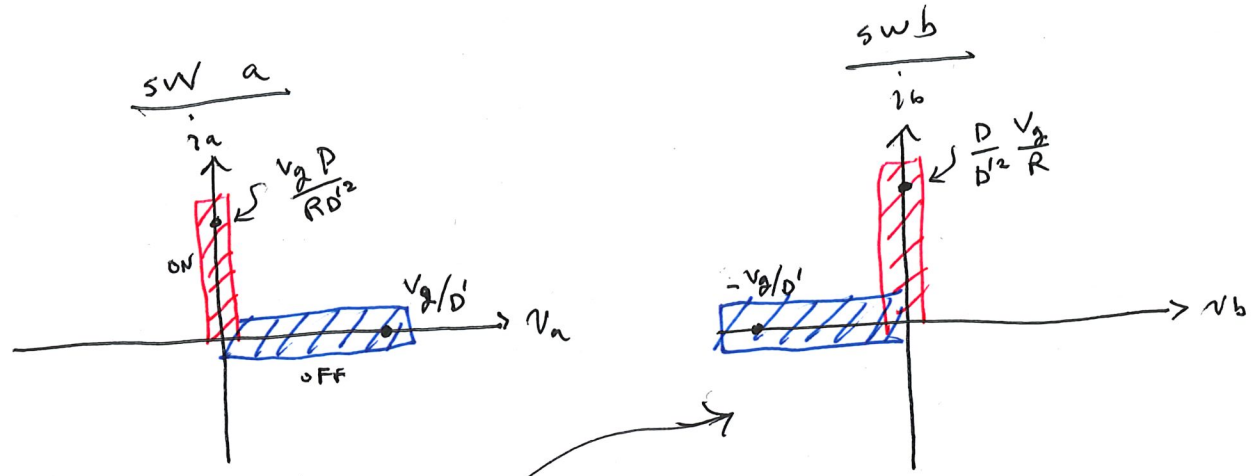

Both are "single quadrant" devices

- sw a = MosFET or IGBT
- sw b = Diode

Realization below ↴

