

Lecture # 11, 10/25/2021

- Last Time

- Overview of lab PWM chip & gate driver
- Tiny bit of CHM, devices

- Lab discussion

- Loose ends on bootstrap design

UC27712 datasheet gives good design tips

Need to pick C_{boot} , R_{boot}

Look at Eq (1) - (2) for C_{boot}

$$Q_{total} = Q_g + \frac{I_{QES}}{f_{sw}}$$

• gate charge on MOSFET

• This value is in MOSFET datasheet

≈ 0
can ignore this

Look @ eq (5) for R_{boot}

helps limit current flow into C_{boot}

$$\text{pick } R_{boot} \geq \frac{V_{DD} - V_{D100\%}}{I_{BOOT,PK}}$$


12V supply voltage

$\approx 5A$ diode datasheet

diode drop

\approx a few Ohms

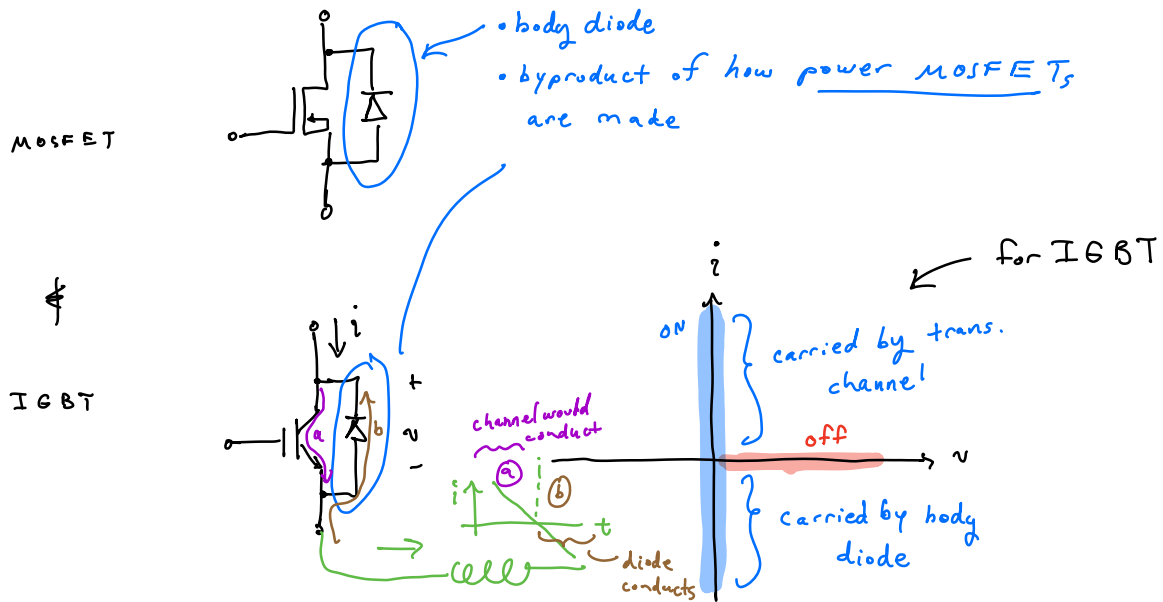- Switches w/ Intrinsic "anti-parallel" body diodes




Recap of devices & where they are used

- controlled {
- MOSFET \rightarrow usually voltage below 600V, (Si)
"low power" \rightarrow Watts to kW,
 f_s up to MHz
 - IGBT \rightarrow up to several kV
"moderate to high power"
 \hookrightarrow up to 100's of kW
 f_s up to 10's of kHz
- uncontrolled {
- Diodes \rightarrow ubiquitous across all applications

- only turn on is controlled {
- Gate turn off (SCR, thyristor) devices
 - High power, up to MW
 - $f_s \approx 100$'s of Hz, down to 10's of Hz



— Converter Examples

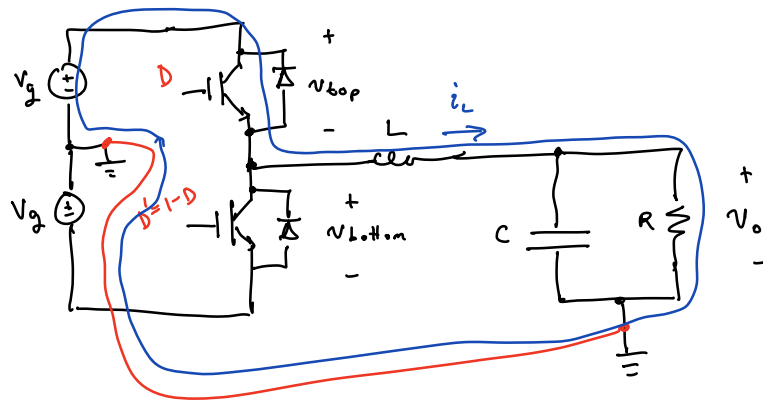- Basic "voltage source inverter" ... single phase



In SS, can show that

$$V_o = (2D - 1)V_g$$

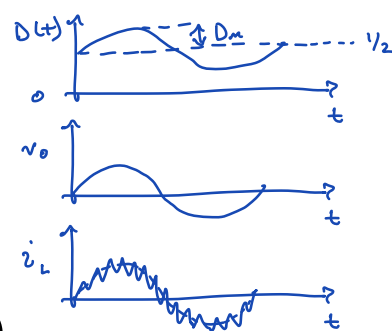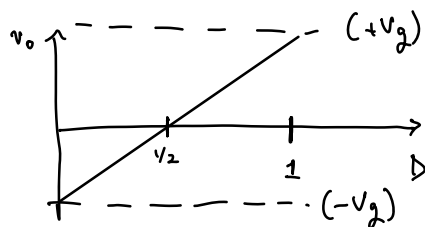

Can get a sinusoidal output!

pick $D(t) = \frac{1}{2} + D_m \sin(\omega t)$

$$\rightarrow -\frac{1}{2} \leq D_m \leq \frac{1}{2}$$

$$i_L \approx \frac{v_o}{R} = (2D-1) \frac{V_g}{R}$$

as D varies between 0 & 1

can get both \oplus & \ominus i_L values


\Rightarrow need bidirectional conducting devices



• Look @ voltage across each sw.

\hookrightarrow only need to block \oplus voltage

\Rightarrow imply either IGBT (w/ body diode) or MOSFET will work.

- Ideal 4 quadrant sw can be made with heroic efforts. Very specialized. See book for more info.

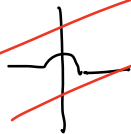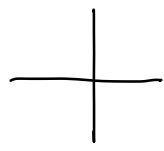~~ = old school~~

 = no connection,  = connection

Lecture #12 10/27/21

Last time

- Switches w/ body diodes
- Inverter example (half bridge)
- Started sw. loss example


Today

- Switching loss
- Device Modeling

Logistics

- No lecture Friday → Will post a make-up video.


— Switching losses & Buck example

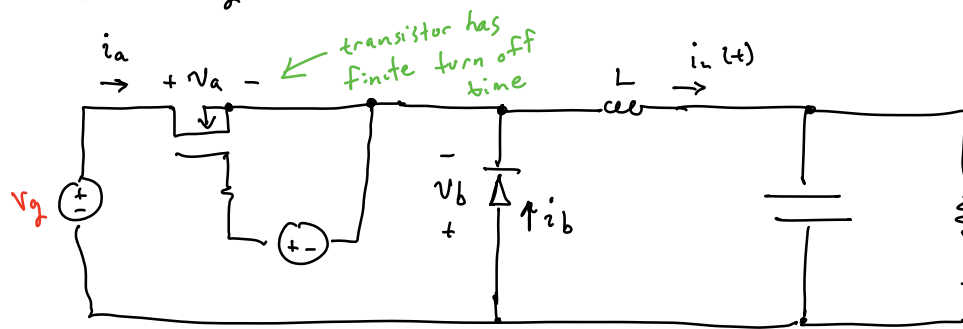

* All devices take finite time to turn on/off.

Causes "switching loss" during transitions.

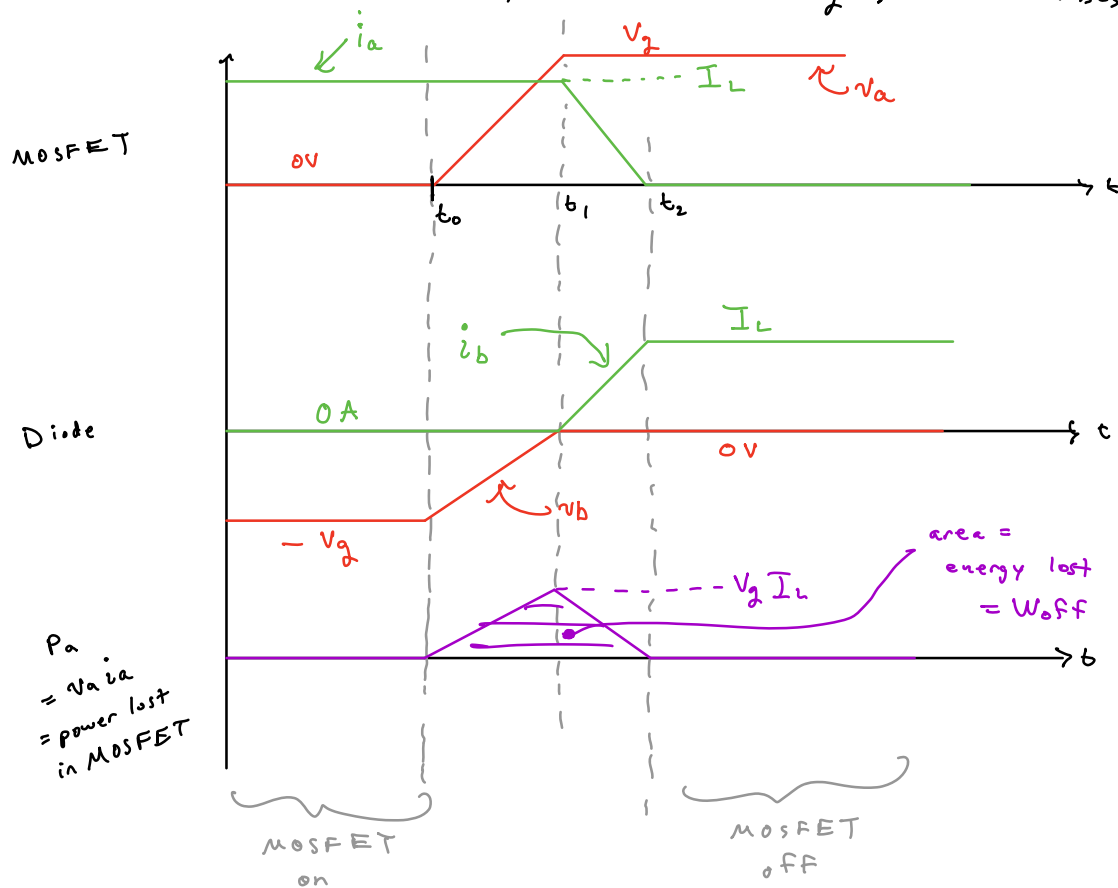- In example assume, ideal diode. Study MOSFET losses.



- This thing isn't lost in one transition.
... but we have switching.

$$P_{sw} = \frac{1}{T_s} \int_0^{T_s} P_a(t) dt = (W_{on} + W_{off}) \frac{1}{T_s}$$
$$= (W_{on} + W_{off}) f_s$$