

Lecture # 27    12/6/21

- Lab discussion

- ↳ Get  $\mathcal{N}$  w/ 24 V input, 48 (or so) V output

- ↳ Configure meters to give avg/filtered readout.
    - ↳ Use beefy banana cables (esp @ input).
    - ↳ Can "double-up" wires on input side for higher  $\mathcal{N}$ .

- Today

- ↳ Ch 6 continued
  - ↳ Transformer-based converters

- ↳ Flyback converter


- HW8, one problem only

## — Transformer Isolation (6.3 in book)

why?

- ▷ Gives isolation for safety
- ▷ Push up  $f_s$  to get small/cheap xfmr.
- ▷ Turns ratio can give very large conversion ratio
- ▷ Multiple inputs/outputs w/ extra windings.

## — Transformer analysis basics

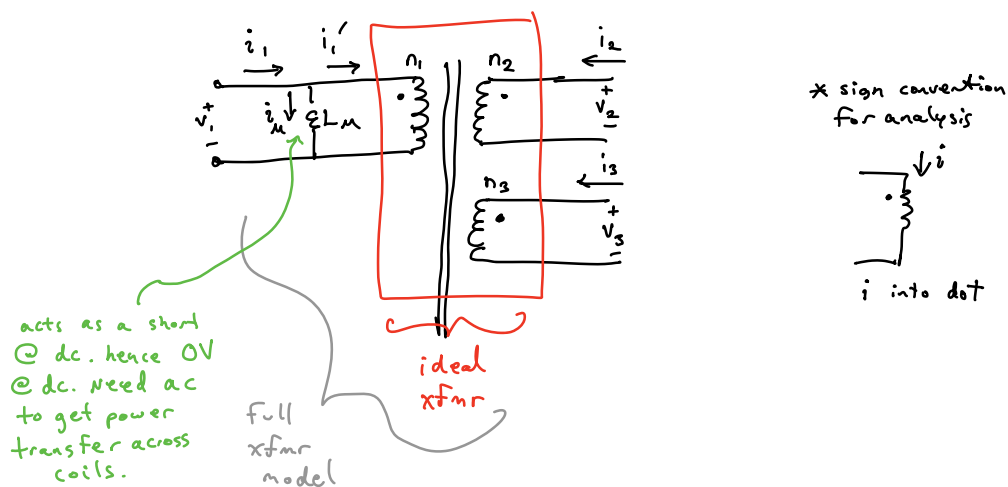

Equiv model w/ 2 components

- $L_M$  = magnetizing inductance
- Ideal xfmr.

• Golden eqn for ideal xfmr gives

$$\frac{v_1}{n_1} = \frac{v_2}{n_2} = \frac{v_3}{n_3} = \dots \quad (1)$$

Ideal xfmr cannot absorb power

$$\Rightarrow P_{in} = P_{out}$$

implies

$$0 = v_1 i_1' + v_2 i_2 + v_3 i_3$$

$$\text{use (1) to get } v_2 = \frac{n_2}{n_1} v_1 \text{ \& } v_3 = \frac{n_3}{n_1} v_1$$


$$= \cancel{v_1} i_1' + \frac{n_2}{n_1} \cancel{v_1} i_2 + \frac{n_3}{n_1} \cancel{v_1} i_3 = 0$$

$$\Rightarrow \boxed{n_1 i_1' + n_2 i_2 + n_3 i_3 = 0} \quad \begin{array}{l} \text{KCL-like eqn} \\ \text{for xfmr} \end{array} \quad (2)$$



— Flyback Conv.


Start w/ buck-boost

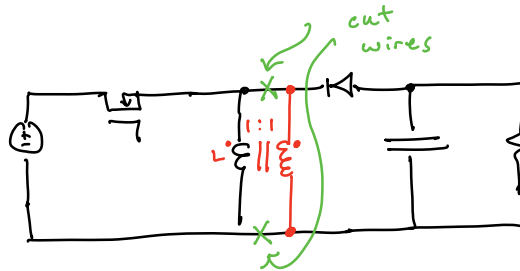

• = step 1


• = step 2

separate halves

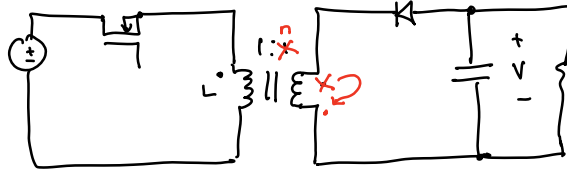


- Generalize to  $1:n$  turns
- Invert polarity of 2nd coil to get  $\oplus$  voltage  $V$ .
- Move sw to "low side" to simplify drive ckt.

"The flyback"

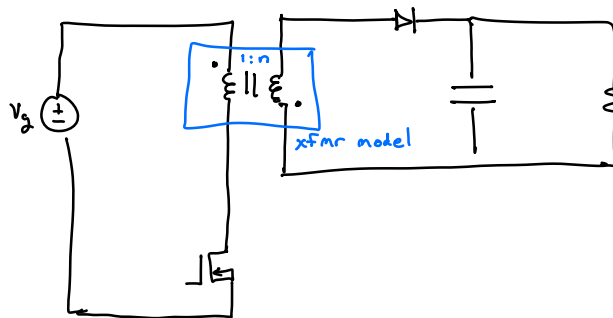

- Modeling for analysis. Add xfmr model

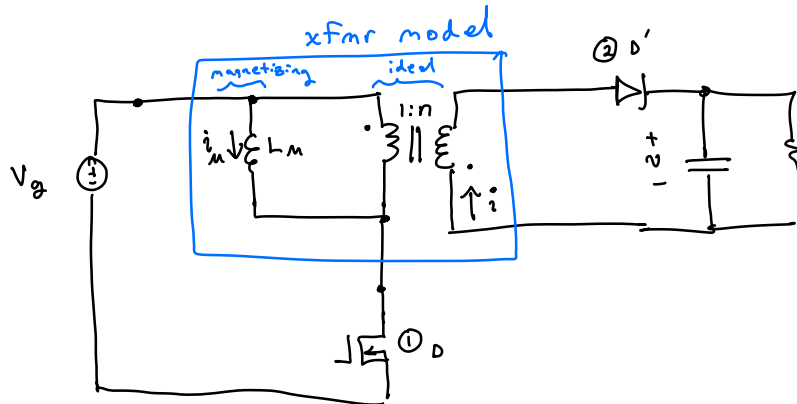


- $L_m$  behaves like a "typical" inductor. In steady state, can use SRA

$$i_m \approx I_m$$

$$v \approx V$$

- Analyze config ① & ②


- For ①

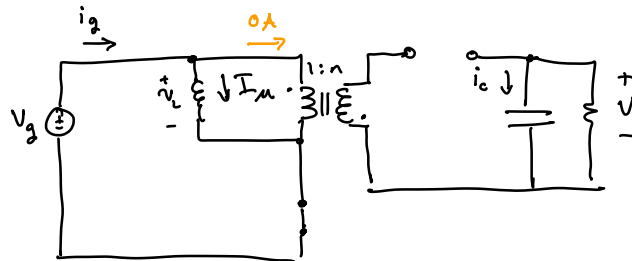

$$v_L = V_g, \quad i_c = -\frac{V}{R}$$

$$i_2 = i_m \approx I_m$$

- For ②

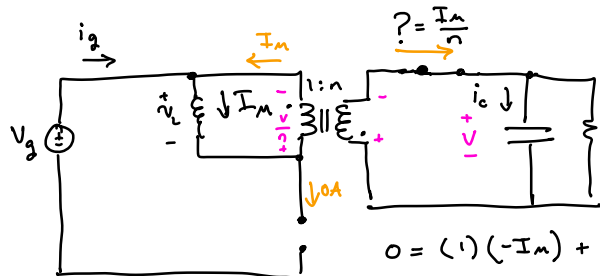

$$\frac{?}{n_1} = -\frac{V}{n_2}$$

$$\rightarrow ? = -V \frac{n_1}{n_2} = -V \frac{1}{n}$$

$$0 = (1)(-I_m) + n(?)$$

$$\Rightarrow ? = \frac{I_m}{n}$$

$$v_L = -\frac{V}{n}, \quad i_c = \frac{I_m}{n} - \frac{V}{R}$$

$$i_g = 0$$

Apply v-sec balance & Q balance

$$\bullet \langle v_L \rangle = 0 = D(V_g) + D'(-\frac{V}{n}) \quad (1)$$

$$(1) \text{ gives } M = \frac{V}{V_g}$$

$$\hookrightarrow \frac{V}{n} D' = D V_g$$

$$\hookrightarrow M = \frac{V}{V_g} = n \frac{D}{D'} = \boxed{n \frac{D}{1-D} = M}$$


like buck boost!  
but w/ n turns  
& no ⊖ sign.

$$\bullet \langle i_c \rangle = 0 = D(-\frac{V}{R}) + D'(\frac{I_m}{n} - \frac{V}{R})$$

can solve for  $I_m$

$$I_m = \frac{nV}{D'R} \quad \& \quad I_g = \langle i_g \rangle = D I_m$$

get equiv ckt

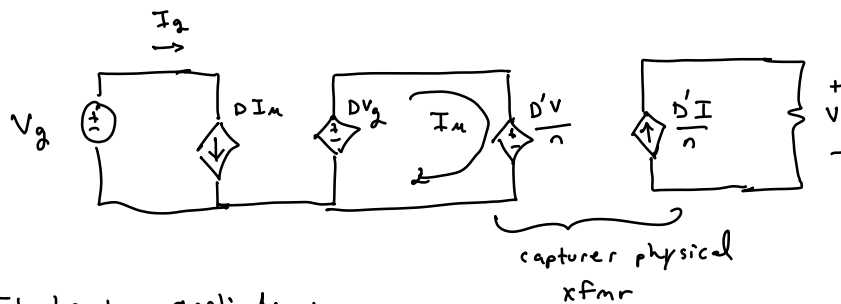

- Fly back application:

Phone charger

