


Lecture #17 11/10/21

Today: Ch 5 on DCM (today only) } read chapter efficiently over next few days


Look ahead: Inductor Design

- Discontinuous Conduction Mode (DCM) - Ch 5


Buck example

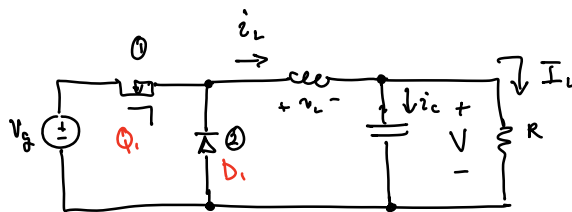

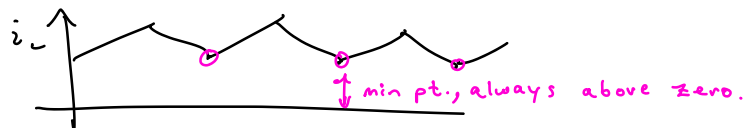All analysis so far is for "Continuous Conduction Mode" (CCM)



@ Boundary, we see

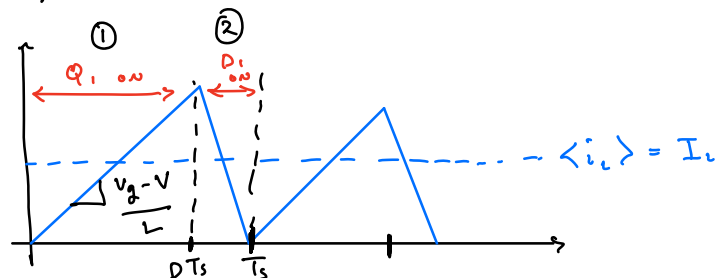

$$\text{know } v_L \approx L \frac{2 \Delta i}{\Delta t}$$

→ look @ config ①

$$\Rightarrow V_g - V = L \frac{2\Delta i}{DT_s}$$

solve for Δi

$$\Delta i = \frac{(V_g - V)DT_s}{2L} \quad (1)$$

Recall, can use V-sec balance to derive $M = \frac{V}{V_g} = D$
underbrace
ideal buck

$$\Rightarrow V = DV_g \quad (2)$$

(2) \rightarrow (1) gives

$$\begin{aligned} \Delta i &= \frac{(V_g - DV_g)DT_s}{2L} \\ &= \frac{V_g(1-D)DT_s}{2L} \quad (3) \end{aligned}$$

Look @ load

$$\begin{aligned} I_L &= \frac{V}{R} \quad \leftarrow \text{due to charge balance} \\ &= \frac{DV_g}{R} \quad (4) \end{aligned}$$

DCM occurs if

$$\begin{array}{ccc} I_L & < & \Delta i_L \\ \uparrow & & \uparrow \\ \text{use (4)} & & \text{use (3)} \end{array}$$

\Downarrow

$$\frac{\cancel{DV_g}}{R} < \frac{\cancel{V_g}(1-D)\cancel{DT_s}}{2L}$$

load dc comp.
 Δi_L ripple size

Obtain DCM boundary equⁿ:

$$\text{DCM occurs if: } \frac{1}{R} < \frac{(1-D)T_s}{2L} \quad (6) \quad \text{for buck}$$

call R_{crit} when

$$\frac{1}{R_{crit}} = \frac{(1-D)T_s}{2L}$$

$$\hookrightarrow R_{crit} = \frac{2L}{D'T_s} \quad (7)$$

Look closer @ (6) & rearrange it to get


$$\frac{2L}{RT_s} < D' \quad (8)$$

physics
"K"


control side
 $K_{crit}(D)$

\hookrightarrow also know range D lies in
(between 0 & 1 are possible)

- Crossing DCM boundary

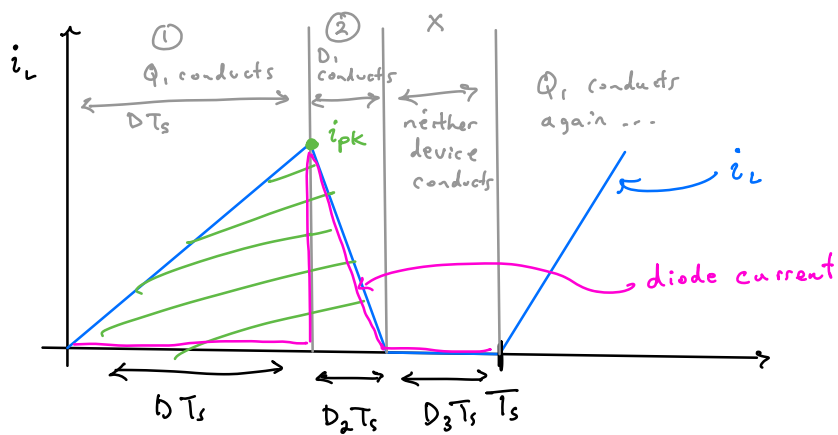

Now Get 3 regions / ckt's

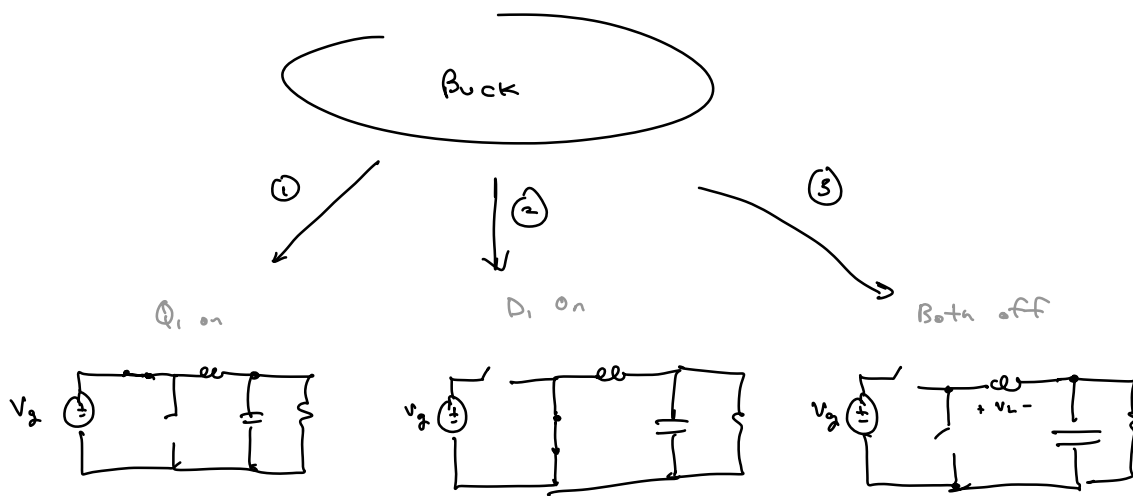

Cautions

→ ~~$i_L \approx I_D$~~ SRA for i_L no longer is true

→ $v \approx V$ ✓ SRA still okay for cap.

When does DCM happen?

→ "light load" → large R , less power

→ inductor intentionally designed for large ripple


- Look @ v-sec balance
 - can get smaller/cheaper inductor
 - facilitate soft switches

$$\langle v_L \rangle = 0 = \overbrace{D(V_g - V)}^{(1)} + \overbrace{D_2(-V)}^{(2)} + \overbrace{D_3(0)}^{(3)} \quad (9)$$

* Note
 $D + D_2 + D_3 = 1$

→ Extra unknown... need 3rd eqn.
Will have 2 charge balance eqns

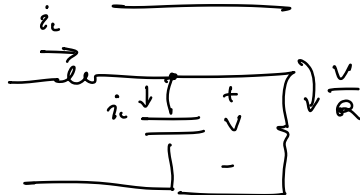- Charge balance on load side using KCL analysis



KCL sides

$$i_L(t) = i_c(t) + V/R$$

↓ avg both sides

$$\underbrace{\langle i_L \rangle}_{I_L} = \cancel{\langle i_c \rangle} + \frac{V}{R}$$

must be zero b/c s.s.

$$\Rightarrow \boxed{I_L = \frac{V}{R}} \quad (10)$$

- Compute $\langle i_c \rangle$ using integral of i_L waveform

$$\underbrace{\langle i_c \rangle}_{I_L} = \frac{1}{T_s} \int_0^{T_s} \underbrace{i_L(t) dt}_{\text{area of } \triangle}$$

$$\begin{aligned} &= \cancel{\frac{1}{T_s}} \frac{1}{2} i_{pk} (D + D_2) \cancel{T_s} \\ &= I_L \end{aligned} \quad (11)$$

equal

Last step: Do algebra to eliminate D_2 ... then can get V 's & I 's

Solve it. (9) gives

$$0 = D(V_g - V) + D_2(-V)$$

$$\Rightarrow \boxed{D_2 = D \frac{V_g - V}{V}} \quad (12)$$

Equate (10) & (11)

$$\begin{aligned}
 \frac{V}{R} &= \frac{1}{2} \frac{DT_s}{L} (V_g - V) (D + D_2) \\
 &\quad \text{ipk. From } \Delta I_L \text{ eqn when } Q_1 \text{ on} \quad \uparrow \text{ use (12)} \\
 &= \frac{1}{2} \frac{DT_s}{L} (V_g - V) \left(D + D \frac{V_g - V}{V} \right) \\
 &= \frac{1}{2} \frac{D^2 T_s}{L} (V_g - V) \left(\frac{V + V_g - V}{V} \right) \\
 &= \frac{1}{2} \frac{D^2 T_s}{L} (V_g - V) \left(\frac{V_g}{V} \right) \\
 &\quad \underbrace{\hspace{10em}}_{\text{RHS}}
 \end{aligned}$$

$$= \underbrace{\frac{V}{R}}_{\text{LHS}}$$

x by $\frac{R}{V_g}$

$$\underbrace{\frac{V}{V_g}}_{\text{LHS}} = D^2 \frac{RT_s}{2L} (V_g - V) \frac{1}{V} = D^2 \underbrace{\frac{RT_s}{2L}}_{\text{call this } K^{-1}} \left(\frac{V_g}{V} - 1 \right)$$

from earlier, see (8)

↔
↓ rewrite

$$\frac{V}{V_g} - \frac{D^2 V_g}{K} \frac{1}{V} + \frac{D^2}{K} = 0$$

want $M = \frac{V}{V_g}$

x by $\frac{V}{V_g}$

get quadratic form

$$\left(\frac{v}{v_g}\right)^2 + \frac{D^2}{k} \left(\frac{v}{v_g}\right) - \frac{D^2}{k} = 0$$

↑
apply quadratic eqn to
set $M = \frac{v}{v_g}$


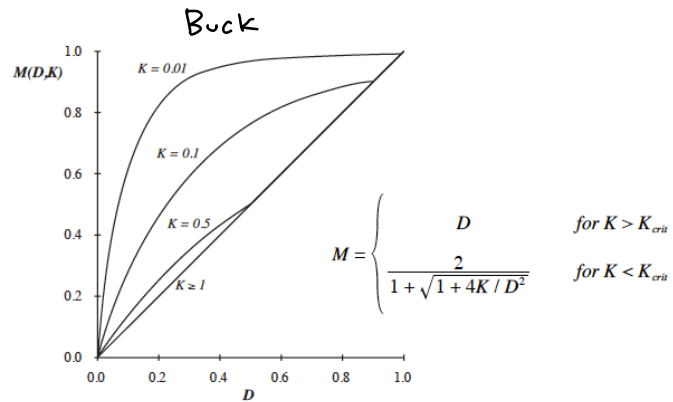


Table 5.2. Summary of CCM-DCM characteristics for the buck, boost, and buck-boost converters

Converter	$K_{crit}(D)$	DCM $M(D,K)$	DCM $D_2(D,K)$	CCM $M(D)$
Buck	$(1-D)$	$\frac{2}{1 + \sqrt{1 + 4K/D^2}}$	$\frac{K}{D} M(D,K)$	D
Boost	$D(1-D)^2$	$\frac{2}{1 + \sqrt{1 + 4D^2/K}}$	$\frac{K}{D} M(D,K)$	$\frac{1}{1-D}$
Buck-boost	$(1-D)^2$	$-\frac{D}{\sqrt{K}}$	\sqrt{K}	$-\frac{D}{1-D}$

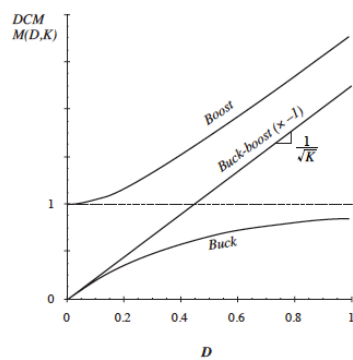with $K = 2L / RT_s$, DCM occurs for $K < K_{crit}$.



- DCM buck and boost characteristics are asymptotic to $M = 1$ and to the DCM buck-boost characteristic
- DCM buck-boost characteristic is linear
- CCM and DCM characteristics intersect at mode boundary. Actual M follows characteristic having larger magnitude
- DCM boost characteristic is nearly linear

