

Lecture # 26 , 12/3/21

Last time:

↳ Finished magnetics & transformers (ch 10) to Sunday night 1159pm.

□ HW7 deadline extended

Today:


↳ Converter structures, Ch 6

Reading Assignment


↳ Read Ch 6 over next 1 week.

- Patterns/Rules that Govern most converter topologies


• Main idea

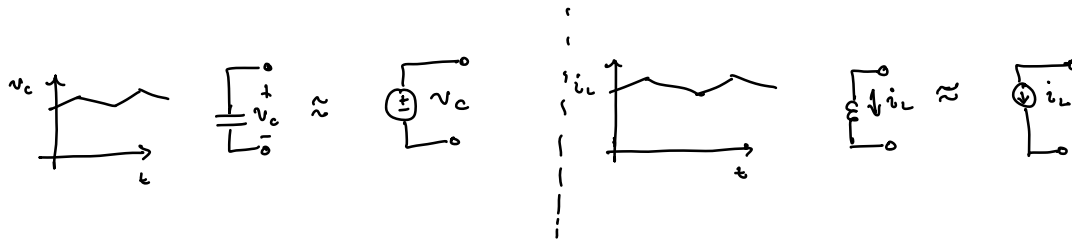

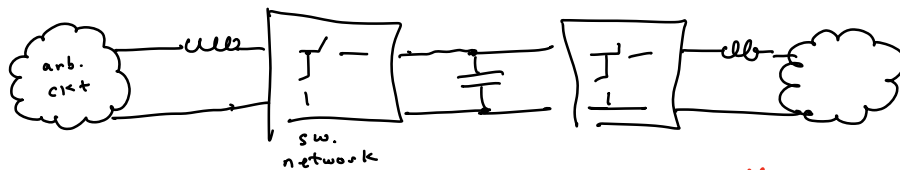Converters generally built by cascading alternating
L's (\approx current source) & C's (\approx voltage source)




Why?

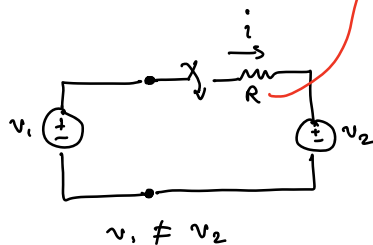

$\rightarrow R$ is very small, $R \rightarrow 0$

i will be very large b/c
differing v source voltages

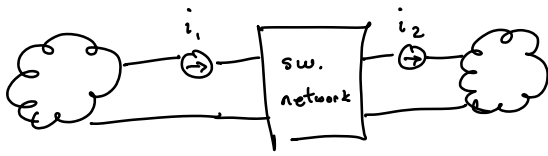
* don't connect to dissimilar voltages
in parallel.



$$i_1 \neq i_2$$

$$i \neq 0 @ t=0$$

ex:

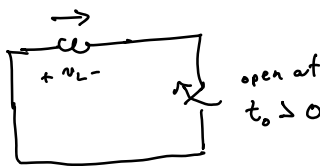

* don't connect 2 mismatched currents in series


$$v_L = L \frac{di}{dt}$$

$L \rightarrow$ goes to $\infty @ t_0$

$$\Rightarrow v_L \rightarrow \infty @ t_0$$

- Circuit Inversions


• Buck is simplest, start here

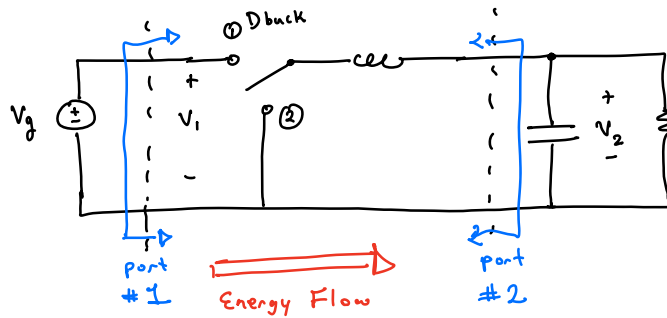

Know $V_2 = V_1 D_{buck}$, $D_{buck} \rightarrow$ position ① duty

$$M(D_{buck}) = \frac{V_2}{V_1} = D_{buck}$$

• Swap input/output ckt elements

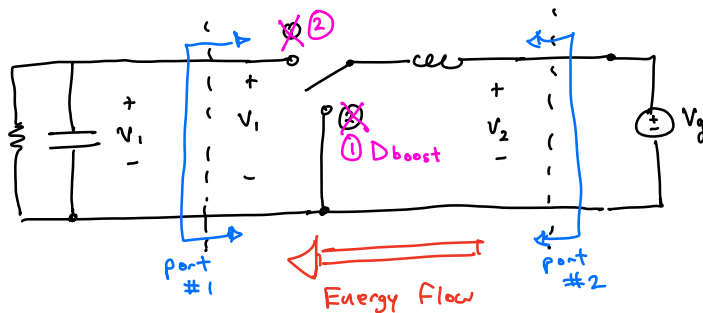

D_{boost} is new ① position duty


It's a boost!

Boost is a buck w/ input/output external elements swapped
& duties swapped.

$$D_{\text{boost}} = 1 - D_{\text{buck}} = D'_{\text{buck}}$$


- Cascaded Converters

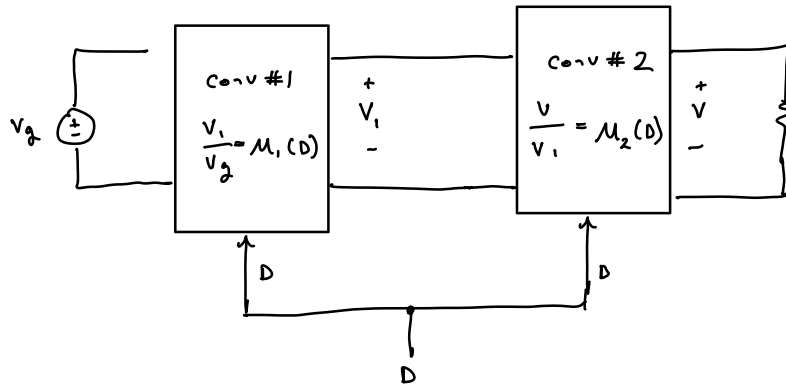* Build more complex akts with multiple cascaded converters



$$\frac{V}{V_g} = M_1(D) M_2(D)$$

Example: Buck + Boost

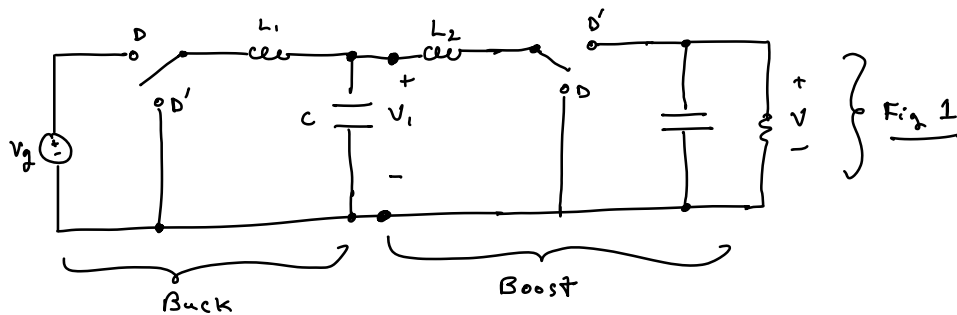

$$M_1(D) = \frac{V_1}{V_g} = D \quad M_2(D) = \frac{V}{V_1} = \frac{1}{1-D}$$

multiply


$$\frac{V}{V_g} = M_1(D) M_2(D) = \frac{D}{1-D} \quad \left\{ \begin{array}{l} \text{"non-inverting"} \\ \text{buck-boost"} \end{array} \right.$$

↓ abstract analysis to show "hiding" buck boost

* Redraw Fig 1 to recover classic buck-boost

Step 1: Simplify filter


↳ Remove intermediate cap & combine L's

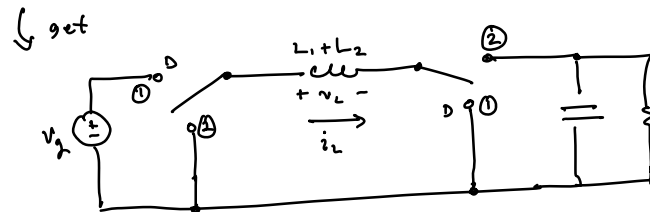

config ①



config ②

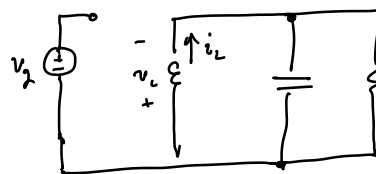

modify ② ckt to obtain basic buck-boost. Get rid of redundant switches


redraw

stays on top now




Use ① & ② to get classic buck boost

↳

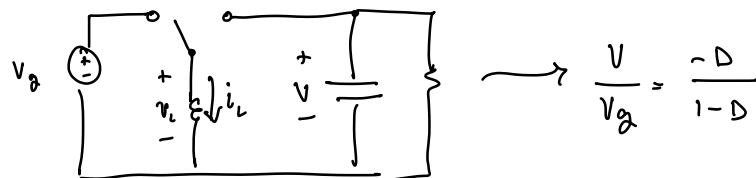

- Differential Connections

* Enables generation of ac waveforms.

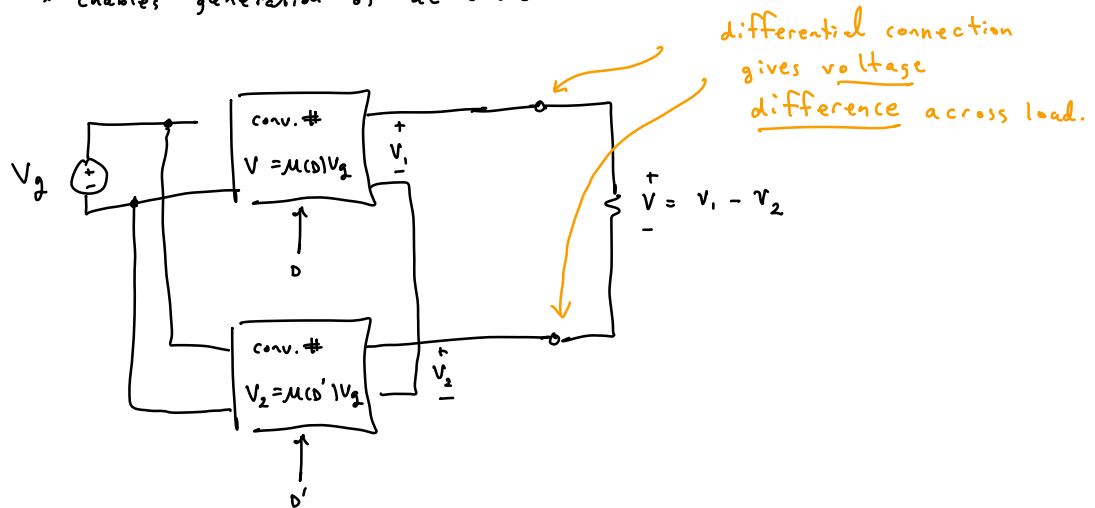

even if V_1 & V_2 are each \oplus , the difference $V_1 - V_2$ can be negative by manipulating V_1 & V_2 .

\Rightarrow allows us to produce an ac waveform.